

Q.1	(A) Select the correct option :		12
	i)	(b) inductance	
	ii)	(a) Hay's	
	iii)	(a) 40 %	
	iv)	(c) 0.5	
	v)	(d) all of the above	
	vi)	(b) are zero	
Q.2	(B) Answer in one sentence :		03
	i)	Since the balancing condition of Wien's bridge depends on the angular frequency, therefore it's source must be a pure sinusoidal?	
	ii)	PIV (peak inverse voltage) rating of a diode is the maximum voltage applied to the diode without damaging it.	
	iii)	Electric potential is potential energy per unit charge.	
	(C) Fill in the blanks		05
	i)	Phasor	
	ii)	Q-factor or Q value	
	iii)	Infinite	
	iv)	A	
	v)	Constant	
Q.2	(A) Attempt any one		08
	i)	Circuit diagram of series C-R circuit-----(2) Finding the phasor voltages-----(2) Obtaining the impedance of the circuit-----(2) Phasor Diagram-----(2)	
	ii)	Explanation of AC bridge-----(2) Obtaining the conditions required to balance AC bridge-----(4) Diagram of Maxwell's LC bridge-----(2)	
	(B) Attempt any one		08
	i)	Circuit diagram of series L-C-R combination-----(2) Derivation for impedance of the circuit-----(3) Expression for phase difference between the current and the voltage---(1) Phasor diagrams for voltage in LCR circuit-----(2)	
	ii)	Circuit diagram and explanation of Wein's bridge-----(3) Obtaining balance condition for Wein's bridge-----(4) Formula for angular frequency-----(1)	

	(C) Attempt any one	04
	i)	$V_{max} = V_{cc} = 15V, \omega = 100\pi, R = 5\Omega, L = 10mH$ Reactance of Inductor $X_L = 2\pi f L = \omega L$ } → ② $\therefore X_L = 100\pi \times 10 \times 10^{-3} \Omega$ $X_L = 3.14 \Omega$ Impedance of the circuit $ Z^* = \sqrt{R^2 + X_L^2}$ → ① $\therefore Z^* = 5.9 \Omega$ $I_{rms} = \frac{V_{rms}}{ Z^* } = \frac{V_{max}}{\sqrt{2} Z^* } = \frac{15}{\sqrt{2} \times 5.9} = \underline{\underline{1.80A}}$ → ①
	ii)	$R_2 = 2.2k\Omega, R_4 = 1k\Omega, C_3 = 0.1\mu F$ Balance condition of de Sauty's bridge is } → ① $\frac{C_1}{C_3} = \frac{R_4}{R_2}$ $\therefore C_1 = \frac{R_4 \times C_3}{R_2} = \frac{1}{2.2} \times 0.1 \times 10^{-6} = 0.045 \times 10^{-6} F$ } → ② $\therefore C_1 = 0.045 \mu F$ The value of other capacitance needed to balance bridge is $0.045 \mu F$ → ①
Q.3	(A) Attempt any one	08
	i)	Diagram of a bridge full wave rectifier ----- (2) Explanation during positive half cycle ----- (3) Explanation during negative half cycle ----- (3)
	ii)	Electronic adder explanation----- (2) Full adder logical circuit with explanation----- (3) Verifying its truth table----- (3)
	(B) Attempt any one	08
	i)	Statement of reciprocity theorem----- (1) Explanation with the help of network circuit----- (2) Finding the value of I_{L1} ----- (2) Finding the value of I_{L2} ----- (2) Conclusion----- (1)
	ii)	Explanation of zener diode----- (2) Circuit diagram for zener diode as voltage regulator----- (2) Discussing the circuit for input voltage greater than or less than zener voltage ----- (4)
	(C) Attempt any one	04

	i)	$R_{th} = \frac{R_1 R_2}{R_1 + R_2} + R_3 = \frac{10 \times 5}{10+5} + 8 = \underline{11.33 \Omega} \rightarrow \textcircled{1}$ <p>for V_{th},</p> $I = \frac{V}{R_{th} + R_2} = \frac{20}{15} = 1.33 \text{ A}$ $\therefore V_{th} = I R_2 = 1.33 \times 5 = \underline{6.67 \text{ V}}$ <p>\therefore Thevenin's equivalent circuit is</p>
	ii)	$V_{in} = 50 \text{ V}, \text{ Series resistance } R = 1 \text{ k}\Omega, \text{ load resistance } = 2.2 \text{ k}\Omega$ $V_z = 25 \text{ V}$ <p>Voltage across series resistance R,</p> $V_R = V_{in} - V_z = 50 - 25 = \underline{25 \text{ V}}$ <p>Current through series resistance R is</p> $I_R = \frac{V_R}{R} = \frac{25 \text{ V}}{1 \text{ k}\Omega} = \underline{25 \text{ mA}}$ <p>$\therefore V_z = V_L = \underline{25 \text{ V}}$</p> $\therefore I_L = \frac{V_L}{R_L} = \frac{25 \text{ V}}{2.2 \text{ k}\Omega} = \underline{11.36 \text{ mA}}$ <p>we have,</p> $I_R = I_z + I_L$ $\therefore I_z = I_R - I_L = 25 - 11.36 = \underline{13.64 \text{ mA}}$
Q.4	(A)	Attempt any one
	i)	Expression for discrete charge distribution-----(2) Explanation of linear charge distribution-----(2) Explanation of surface charge distribution-----(2) Explanation of volume charge distribution-----(2)
	ii)	Construction of Helmholtz coil with diagram-----(2) Obtaining the magnetic field produced by it-----(2) Finding its value at midpoint of the line joining the centres----(2) Explaining the magnetic field with the help of graph-----(2)
	(B)	Attempt any one
	i)	Assumption of point charges distribution ----- (2) Finding the work done to bring the charges-----(4) Conclusion-----(2)
	ii)	Explaining the solenoid-----(2) Obtaining the magnetic field of current carrying solenoid-----(2) Proving the value at the end is half the field at a point well inside-----(2) Plot of the magnetic field along the axis of solenoid-----(2)

	(C)	Attempt any one	04
	i)	<p>Let $q_0 = 1\text{C}$, $q_1 = 2\text{uC}$, $q_2 = 3\text{uC}$, $q_3 = 5\text{uC}$</p> $x_1 = 2\text{cm}$, $x_2 = 3\text{cm}$, $x_3 = 5\text{cm}$	①
		using superposition principle,	
		$F = \frac{q_0}{4\pi\epsilon_0} \left[\frac{q_1}{r_1^2} + \frac{q_2}{r_2^2} + \frac{q_3}{r_3^2} \right] \rightarrow ①$ $= 9 \times 10^9 \times 1 \times \left[\frac{2}{4^2} + \frac{3}{9^2} + \frac{5}{25^2} \right] \times 10^{-6} \rightarrow ①$ $\boxed{F = 9.27 \times 10^7 \text{ N}} \rightarrow ①$	
	ii)	<p>for straight long conductor carrying current,</p> $B = \frac{\mu_0 I}{2\pi x}$ <p>Here, $I = 12\text{A}$, $x = 25\text{cm} = 25 \times 10^{-2}\text{m}$</p> $\therefore B = \frac{\mu_0 \times 2I}{4\pi x} = 10^{-7} \times \frac{2 \times 12}{25 \times 10^{-2}} = 0.96 \times 10^{-5} \text{ wb}$ $\boxed{B = 0.96 \times 10^{-5} \text{ wb.}}$	②
Q.5		Attempt any four	20
	i)	Statement of Superposition theorem----- (2) Basic steps for solving a network circuit----- (3)	
	ii)	$Y = A \cdot B + B \cdot C (B+C)$	
		---(5)	
	iii)	Importance of capacitor as a filter----- (2) Explanation with the help of graph----- (3)	
	iv)	Explanation of EX-OR gate----- (2) It's construction using basic gates----- (3)	

	v)	Discussion of electric field-----(2) Obtaining expression in terms of force and charge-----(3)	
	vi)	Statement of Biot-Savarts law-----(2) It's explanation-----(3)	
