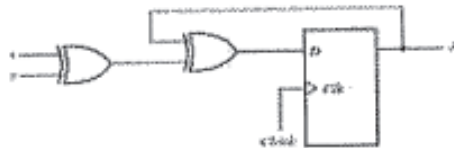


- N.B. :** (1) Question No. 1 is **compulsory**.  
 (2) **Solve** any **three** questions from remaining **five** questions.  
 (3) Draw neat **diagrams** and assume suitable **data** wherever **necessary**. Justify your **assumptions**.

1. (a) Explain Shift register and its applications. 5  
 (b) Explain drawback of synchronous counter. 5  
 (c) Draw truth table and circuit of Half Adder. 5  
 (d) What do you mean by noise margin ? What is its value in TTL and CMOS family ? 5
2. (a) Simplify following function and realize using NOR gate 10  

$$F = \prod M(1, 2, 4, 7, 11, 13) d(9, 15)$$
  
 (b) Design Mod 5 asynchronous counter and explain glitch problem. 10
3. (a) Design and explain 8 bit binary added using IC 7483. 10  
 (b) Analyze the sequential state machine shown in figure. Write the state table and state diagram for the same : 10



4. (a) Design a circuit with PLA to implement the following functions : 10  

$$F1 = \sum m(1, 2, 3, 6, 9, 11)$$
  

$$F2 = \sum m(2, 12, 13)$$
  

$$F2 = \sum m(1, 2, 8, 12, 13)$$
  
 (b) Draw logic diagram of mod-8 binary counter. Sketch the resulting state variable output. 10
5. (a) Design Moore sequence detector to detect sequence . . . . 101 . . . using D FF. 10  
 (b) Draw a circuit diagram of CMOS inverter and explain its operation. Draw its transfer characteristics. 10
6. Write short notes on any **three** of the following :— 20
  - (a) K-map
  - (b) Mealy and Moore sequential machine
  - (c) Noise Margin
  - (d) XC 9500 CPLD family.