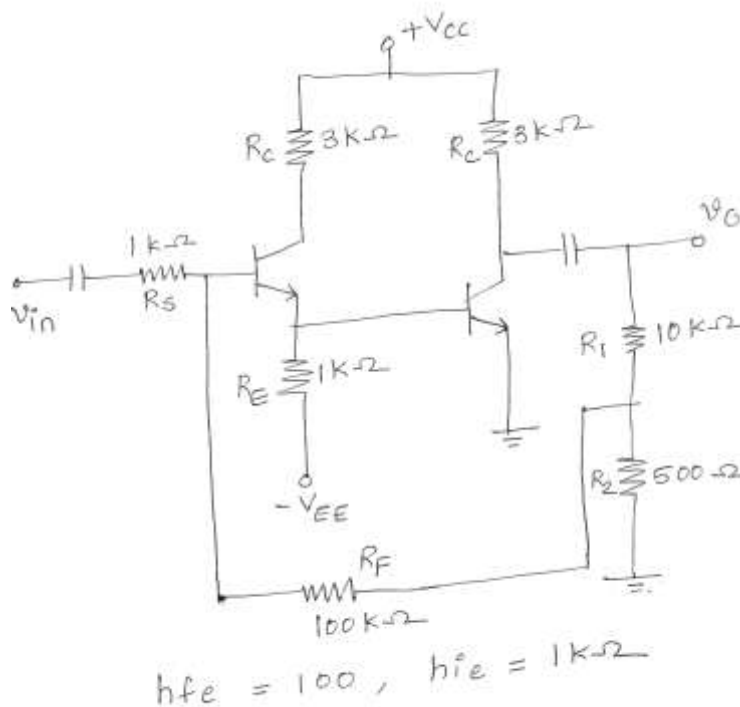


Please check whether you have got the right question paper.

- N.B:
1. Question no one is compulsory.
 2. Attempt any three questions out of remaining five questions.
 3. All questions carry equal marks.

- Q.1 a) Discuss LOG amplifier using op-amp with neat circuit diagram. Derive expression for output and state disadvantages. 5
- b) Compare current series and current shunt types of negative feedback. 5
- c) Explain working of precision full wave rectifier using op-amp. 5
- d) For power BJT the thermal resistance parameters are as follows. 5
- $$\theta_{\text{dev-case}} = 3 \text{ }^{\circ}\text{C/W} \quad \theta_{\text{case-sink}} = 0.7 \text{ }^{\circ}\text{C/W}$$
- $$\theta_{\text{case-amb}} = 72 \text{ }^{\circ}\text{C/W} \quad T_{\text{amb}} = 40^{\circ} \text{C}$$
- $$\theta_{\text{sink-amb}} = 5 \text{ }^{\circ}\text{C/W} \quad T_{\text{j max}} = 180^{\circ} \text{C}$$
- Evaluate the maximum power dissipation in transistor with and without heat sink.
- Q.2 a) Derive the equations for frequency of oscillations and conditions for colpitt's oscillator with neat circuit diagram. 10
- Discuss its disadvantage and method to overcome it.
- b) Design transformer coupled class A power amplifier to provide 9 W output to 6Ω load. 10
- Q.3 a) Derive equation for gain of three op-amp instrumentation amplifier and design it for variable gain from 1 to 1000. 10
- b) Evaluate A_d, A_c and CMRR for DIUO differential amplifier 10
- Given = supply = $\pm 20\text{V}$, $R_c = 4.7 \text{ k}\Omega$
 $R_E = 1.5 \text{ k}\Omega$, $R_S = 750 \Omega$, $\beta = 150$
 Discuss need of swamping resistors.
- Q.4 a) Discuss shortcomings of ideal integrator and suggest solution for the same in detail. 7
- Draw frequency response for both the cases and develop output equation.
- b) Evaluate A_{v_f} and R_{inf} for the following circuit. 13



- Q.5 a) Discuss class- B push- pull power amplifier with neat diagram and current wave forms 10
Derive equations for efficiency and figures of merit. Explain advantages and disadvantages.
- b) Design R.C phase shift oscillator for $f = 10\text{ KHz}$. 5
- c) Explain working of clamper circuit using op-amp. Draw input output wave form. 5
- Q.6 Write short notes on (any four) 20
- Characteristics of negative feedback
 - Class AB push. Pull power amplifier
 - Current mirror circuit
 - Peak detector
 - Schmitt trigger.

DBEC DATA SHEET

Transistor type	P _{den} max @ 25°C Watts	I _{cm} max @ 25°C Amps	V _{ce} (volts) d.c.	V _{ceo} (Volts) d.c.	V _{ceo} (Sus) Volts d.c.	V _{ces} (Sus) Volts d.c.	V _{ces} (Sus) Volts d.c.	V _{ceo} (Sus) Volts d.c.	V _{ces} (Sus) Volts d.c.	D.C. current		Signal	h _{FE} max.	V _{et} max.		
										min	max.					
2N3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8
2N3055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5
ECM149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2
ECM100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9
2N525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9

BFW 11—JFET MUTUAL CHARACTERISTICS

Transistor type	h _{ie}	h _{oe}	h _{re}	o _{je}
BC 147A	2.7 K Ω	18 μ Ω	1.5 × 10 ⁻⁴	0.4°C/mw
2N 525 (PNP)	1.4 K Ω	25 μ Ω	3.2 × 10 ⁻⁴	—
BC 147B	4.5 K Ω	30 μ Ω	2 × 10 ⁻⁴	0.4°C/mw

N-Channel JFET

Type	V _{DS} max. Volts	V _{GS} max. Volts	V _{GS} max. Volts	P _d max. @25°C	I _{DS} max. mA	T _J max. °C	r _{DS}	-V _P Volts	r _g	Derate above 25°C
2N3822	50	50	50	300 mW	2 mA	175°C	3000 μΩ	6	50 KΩ	2 mW/°C
BFW 11 (typical)	30	30	30	300 mW	7 mA	200°C	5000 μΩ	2.5	50 KΩ	—

UJT type	P _d max. @25°C	I _e max. peak pulse current	V _{max} Volts max.	V _{max} Volts	T _J max. °C	η	R _{th} KΩ	Max. I _P μA
2N2646	300mW	50mA	30	35	125°C	0.56	4.7	9.1