

- Instructions:** 1) Question No. 1 is compulsory.  
 2) Answer **any three** from **remaining five**.  
 3) Assume data where ever needed.

- 1 Answer any four**
- a) State and prove Demorgans theorem. **5**
- b) Explain in brief CMRR, slew rate. **5**
- c) Convert following **5**  
 (i) 101101 to gray code  
 (ii)  $(CD8.4)_{16}$  to octal
- d) Convert SR to JK flip flop. **5**
- e) Explain in brief types of registers. **5**
- 2** a) Explain 555 timer working as astable multivibrator. **10**
- b) Explain first order low pass filter. Design a low pass filter at a cut off frequency of 1kHz with a pass band gain of 2. Also plot the frequency response curve. Assume  $C=0.01\mu F$ . **10**
- 3** a) Design a mod-5 synchronous counter using JK flip flop without lockout. **10**
- b) Minimize the expression using K map and implement using NAND gates only. **10**  

$$F = \Sigma(0,5,9,12,13,14,15) + d(1,2,3,4)$$
- 4** a) Explain successive approximation type ADC. **10**
- b) Explain TTL logic families. **10**
- 5** a) Implement following expression using (i) 8:1 Mux (ii) 4:1 Mux **10**  
 $F(A,B,C) = \Sigma(0,2,5,6,7)$
- b) Explain ideal and practical differentiator. **10**
- 6** a) Design and implement 3bit gray to binary code converter. **10**
- b) Explain Schmitt trigger with necessary waveforms. **10**

-----