

**[Time: Three Hours]****[ Marks:80]**

Please check whether you have got the right question paper.

- N.B: 1. Question no 1. Is compulsory.  
2. Attempt any 3 questions from remaining.  
3. Assume suitable data wherever necessary.

**Q.1** Attempt any **Four** of following.**[20]**

- a) Discuss Power MOSFET structure, working and characteristics with neat labeled diagrams.
- b) Explain Block Diagram of VCO.
- c) Explain the different types of analog switches.
- d) Compare AC and DC motors. Give suitable examples for each.
- e) Explain the generalized impedance convertors and give a few examples.
- f) Explain block diagram of PLL and list application of PLL.

**Q.2**

- a) Design a voltage regulator using IC 723 to meet the following specifications:-  
 $V_o = 5V, I_o = 100mA, V_{in} = 15 \pm 20V, I_{sc} = 150mA \text{ & } V_{sense} = 0.7V$
- b) Explain working of UJT as a Relaxation Oscillator and derive its frequency.
- c) Explain working and construction of a basic stepper motor.

**[05]****[07]****[08]****Q.3**

- a) Compare Active and Passive filters. Explain low pass KRC filter and derive the equation for Q.
- b) Explain Lock range, Capture range and pull in time related to PLL.
- c) Explain missing pulse detector using timer IC 555.

**[10]****[05]****[05]****Q.4**

- a) Draw and explain the two transistor model of SCR.
- b) Design an Instrumentation Amplifier using AD620 for gain of 650 and explain its applications.
- c) Design a timer for Duty cycle 40% for  $T_{on} = 0.8ms$ . Draw corresponding waveforms across output and capacitor.

**[08]****[06]****[06]****Q.5**

- a) Explain the functional block diagram of IC8038.
- b) Design a 2nd order Butterworth high pass filter for  $f = 1.5 \text{ KHz}$  and also plot its frequency response.
- c) Sketch the functional block diagram of IC555 timer and explain its working principle. Also explain use of pin number 2 and pin number 5 in detail.

**[05]****[05]****[10]****Q.6** Attempt any **Four** of following:-**[20]**

- a) Explain FSK using IC 555
- b) Short note on Switching Mode Power Supply
- c) Short note on :Opto -Isolators and Opto -Couples
- d) Draw Symbol, structure and characteristics of DIAC and TRIAC.
- e) Draw Frequency response of Butterworth, Chebyshev and Elliptical filters and compare them.

\*\*\*\*\*