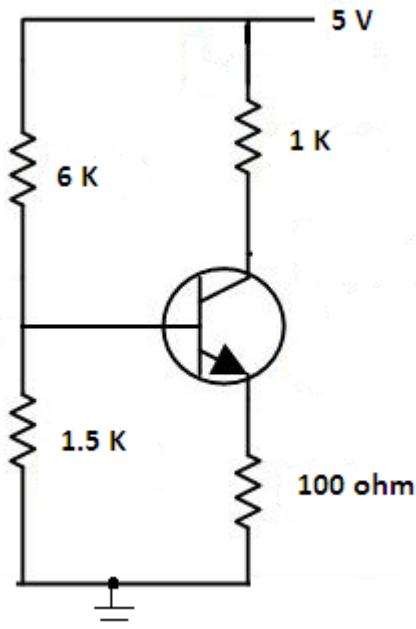


(3 Hours)

Maximum Marks 80


- N.B: (1) Question No.1 is compulsory.
 (2) Solve any three out of remaining question.
 (3) Assume suitable data if necessary.

Que-1	Solve any Four	Marks
a	What happens when pn junction diode is made forward bias, explain considering any suitable application.	5
b	Explain how CC configuration of BJT gives voltage gain less than 1	5
c	Explain with the help of construction that MOSFET gives more Input resistance than JFET	5
d	What is varactor Diode, also state its applications.	5
e	Compare C, L and LC filters.	5
Que-2a	Draw Energy band diagram of pn junction diode under i) Zero Bias ii) Forward bias and iii) Reverse Bias	10
Que-2b	For the given circuit find Steady State DC Parameters I_{CQ} and V_{CEQ} Given $\beta = 100$ and $V_{BE} = 0.7 \text{ V}$, also state in which region the circuit is working.	10



Que-3a For the given MOSFET amplifier , Determine IDq, VGSq and VDS.

10

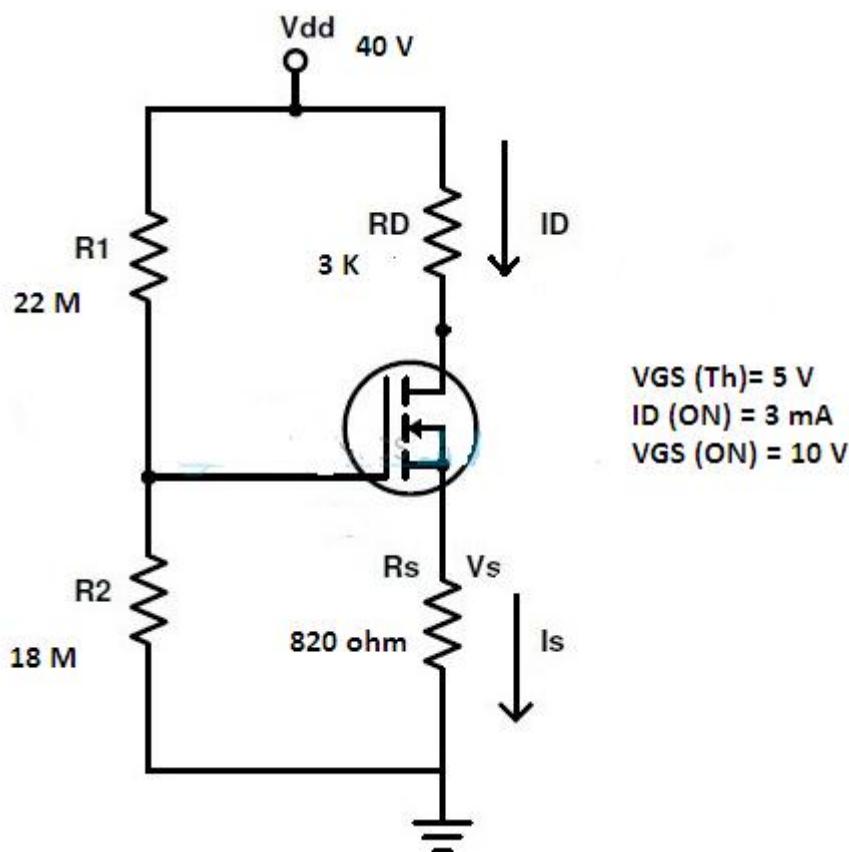

Que-3b Explain working principle, characteristics and applications of Photodiode.

10

Que-4a What is the need of Filters, Explain L filter circuit?

10

Que-4b For the voltage divider biased BJT amplifier without bypass capacitor circuit derive equation of Input resistance, Voltage gain, current gain and output resistance.

10

Que-5a Design Single Stage CE amplifier for the given specifications

Av ≥ 100 , S = 10, Vo = 3 V, fL = 20 Hz, use transistor BC 147 BUse coupling and bypass capacitor as C1 = C2 = 10 μF and CE = 100 μF .

15

Que-5b What is Clamping circuit, explain with neat Input and output waveforms for negative Clamping circuit.

05

Que-6a For the voltage divider biased E MOSFET circuit derive equation of Input Resistance, Voltage gain and output resistance.

10

Que-6b Derive equation of Input resistance, Current gain and Voltage gain for CC amplifier.

10

DBEC DATA SHEET

Transistor type	Pdmax @ 25°C Watts	I _{cm} @ 25°C Amps	V _{ce0} volts d.c.	V _{ca0} (S _W) volts d.c.	V _{ce0} (S _W) volts d.c.	D.C. current typ. max.	T _i °C max.	Signal h _{ie} min. typ. max.	V _{ce} max.	θ _{ce} °C/W	Derate above 25°C W/°C	
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	1.5
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	75	1.5
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	1.2
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	0.9
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	2.0
2N 5225(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	4.5
Transistor type												
BC 147A	2.7 KΩ	18μ A	1.5 × 10 ⁻⁴	0.4°C/mW	—	—	—	—	—	—	—	—
2N 525 (PNP)	1.4 KΩ	2.5μ A	3.2 × 10 ⁻⁴	0.4°C/mW	—	—	—	—	—	—	—	—
BC 147B	4.5 KΩ	30μ A	2 × 10 ⁻⁴	0.4°C/mW	—	—	—	—	—	—	—	—
ECN 100	50 Ω	—	—	—	—	—	—	—	—	—	—	—
ECN 149	15 Ω	—	—	—	—	—	—	—	—	—	—	—
ECN 055	12 Ω	—	—	—	—	—	—	—	—	—	—	—
2N 3055	6 Ω	—	—	—	—	—	—	—	—	—	—	—
N-Channel JFET												
Type	V _{ds} max. Volts	V _{ds} max. Volts	V _{ds} max. Volts	P _d max. @25°C	T _i max.	I _{ds}	I _{ds}	θ _{ds} (typical)	-V _f Volts	r ₄	Derate above 25°C	
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ A	6	50 kΩ	2 mW/°C	0.59°C/mW	
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μ A	2.5	50 kΩ	—	0.59°C/mW	