

(3 Hours)

[Total Marks:80]

- N.B.** (1) Question no.1 is compulsory.  
 (2) Attempt any three from the rest.  
 (3) Make any suitable assumption wherever required.
- Q.1** Answer any four.
- |     |  |    |
|-----|--|----|
| (a) | Explain drift current and diffusion current                          | 5M |
| (b) | Explain DC load line in common emitter BJT                           | 5M |
| (c) | Explain why FET is free from thermal runaway.                        | 5M |
| (d) | Explain the re model of BJT.   | 5M |
| (e) | Explain the sufficient and necessary conditions for the oscillation. | 5M |
- Q.2**
- |     |   |     |
|-----|---|-----|
| (a) | Explain the input and output characteristics of CE BJT amplifier. | 10M |
| (b) | Explain different biasing techniques in BJT                       | 10M |
- Q.3**
- |     |   |     |
|-----|---|-----|
| (a) | Write the working principle of enhancement and depletion type of MOSFET.  | 10M |
| (b) | Draw the circuit diagram of bridge rectifier with LC filter with all the waveforms and derive the expression for ripple factor. | 10M |
- Q.4**
- |     |  |     |
|-----|--|-----|
| (a) | Draw the circuit diagram of current series feedback amplifier and derive the expression for input and output impedance and voltage gain with feedback. | 10M |
| (b) | Explain the working principle of the following semiconductor devices   | 10M |
|     | i. PIN diode   |     |
|     | ii. FET  |     |
|     | iii. L-C tank circuit  |     |
|     | iv. Schottky diode   |     |
- Q.5**
- |     |  |     |
|-----|--|-----|
| (a) | Draw the circuit diagram of collpitt's oscillator and explain the working. Derive the expression for the frequency of oscillation. | 10M |
| (b) | explain the modeling of CE BJT in h- parameter and hence derive the expression for voltage gain                                    | 10M |
- Q.6** Write short note on any THREE of the following. 20M
- |     |  |
|-----|--|
| (a) | UJT relaxation oscillator.                       |
| (b) | Zener diode as voltage regulator                 |
| (c) | Two port network                                 |
| (d) | Input output and transfer characteristics of FET |

-----