


Time: 3Hrs



00054369
Marks:-100


<p>N.B : (1) All questions are compulsory. (2) Figures to the right indicate maximum marks. (3) Use of non-programmable calculators is permitted. (4) Symbols used have their usual meaning</p>		
Q1.	A) Select correct answer.	(12)
	1 b) conservative	
	2 b) $\rho d\rho d\theta dz$	
	3 b) unfaithful amplification	
	4 b) is reduced	
	5 d) 60°	
	6 c) 1	
	B) Answer in one sentence.	(03)
	1 $h_1 = 1, h_2 = r, h_3 = r\sin\theta$	
	2 The ideal value of stability factor is 1	
	3 Slew rate is the rate of change of close loop output voltage per unit time.	
	C) Fill in the Blanks.	(5)
	1 $d\vec{s} = dx dy \hat{k}$	
	2 $\nabla \times \vec{A} = 0$	
	3 not fall below 1V	
	4 6	
	5 decreases.	
Q2.	A) Attempt any one.	(8)
	1 Statement & explanation-2 Problem solving- 6	
	2 Problem solving- 8	
	B) Attempt any one.	(8)
	1 	
	2 Spherical co-ordinate system----2 marks Derivations of unit vectors ----6 marks	
	C) Attempt any one.	(4)

	1		
	2	$\vec{F} = 2xy^2 \hat{i} + 3xy \hat{j}$ Path - O(0,0) to P(1,1) described by equation $y = x^2$. $W = \frac{46}{30}$ units	
Q3.	A)	Attempt any one.	(8)
	1	Circuit diagram and description (3 Marks) Circuit Analysis (Deriving I_C and V_{CE}) (3 Marks) Discussion of circuit stabilisation (2 marks)	
	2	Stability factor (2 marks) Input resistance (2 marks) output resistance (2 marks) Bandwidth (2 marks)	
	B)	Attempt any one	(8)
	1	Circuit diagram and description (3 Marks) Circuit Analysis (Deriving I_C and V_{CE}) (3 Marks) Discussion of circuit stabilisation (2 marks)	
	2	Circuit diagram (2 marks) Identifying different sections (4 marks) Phase inversion in CE amplifier (2 marks)	
	C)	Attempt any one	(4)

1		<p>For a silicon transistor,</p> $V_{BE} = 0.7 \text{ V}$ $I_B = \frac{I_C}{\beta} = 1/100 = 0.01 \text{ mA} \quad (1 \text{ mark})$ <p>Now $V_{CE} = V_{BE} + V_{CR}$ or $2 = 0.7 + V_{CB}$ $\therefore V_{CB} = 2 - 0.7 = 1.3 \text{ V} \quad (2 \text{ marks})$ $\therefore R_B = \frac{V_{CB}}{I_B} = \frac{1.3 \text{ V}}{0.01 \text{ mA}} = 130 \text{ k}\Omega \quad (1 \text{ mark})$</p>	
2		Bandwidth diagram (1 marks) Explanation (3 marks)	
Q4.	A)	Attempt any one UNIT III	(8)
1		Diagram (03)+working(04)+frequency(01)	
$f = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$			
2		Definition(01)+diagram (02)working(02)+derivation(03) The op-amp circuit where output voltage is proportional to the integral of the input.	
$V_o = \frac{-1}{RC} \int V_i dt$			
B)		Attempt any one.	(8)
1		Definition(01)+diagram(03)+working(04) The electronic circuit that generates periodic waveforms / alternating signals at the output terminal with only dc supply as input.	


9

00054369

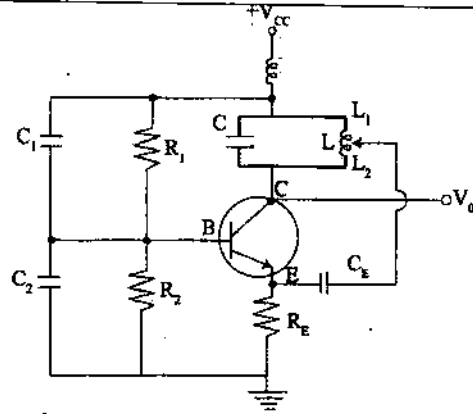

$$f = \frac{1}{2\pi\sqrt{LC}} \quad \text{or} \quad \frac{1}{2\pi\sqrt{(L_T)C}} \quad L_T = L_1 + L_2 + 2M$$

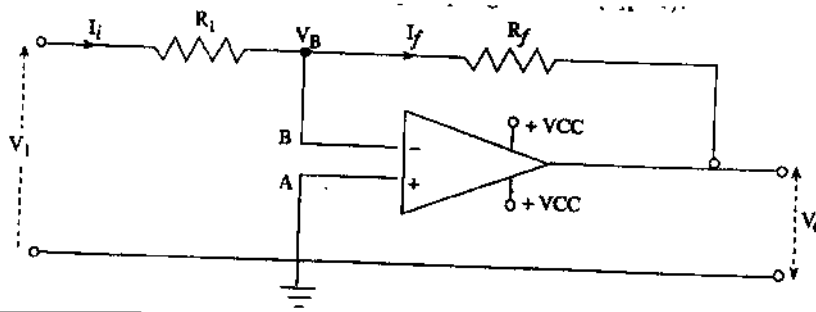
2 Definition(02)+diagram(02)+derivation(04)



C) Attempt any one.

(4)

1 Diagram(02)+working(02)

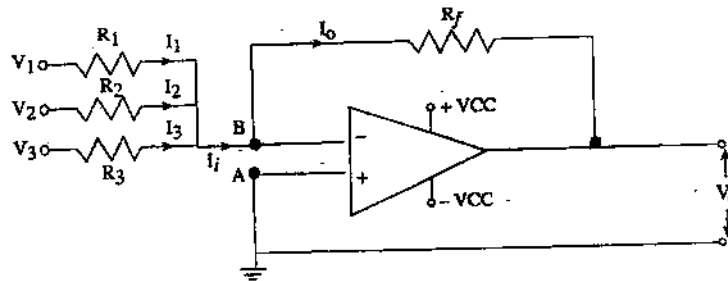

$$R_1 = R_2 = R_3 = R \text{ and } R_f = R/3$$

2 $R_i = 10K\Omega$, $R_f = 22K\Omega$

$$\text{Gain} = \frac{-R_f}{R_i} = -2.2 \quad \text{-----2 marks}$$

$$\text{For } V_i = 150\text{mV}, V_o = 0.33\text{V} \quad \text{-----1 mark}$$

$$\text{For } V_i = -3\text{V}, V_o = 6.6\text{V} \quad \text{-----1 mark}$$

Q5. Attempt any Four.

(20)

1 Divergence theorem statement (2 marks)

Explanation with examples of positive, negative divergence (3 marks)

2			
3		Draw DC load line ($V_{CE} = 15\text{ V}$, $I_C = 0$ & $V_{CE} = 0$, $I_C = 5\text{ mA}$) (3 marks) Operating point $V_{CE} = 8.55\text{ V}$, $I_C = 2.15\text{ mA}$ (2 marks)	
4		(i) the voltage gain with feedback = 8 (1 mark) (ii) the input resistance with feedback = 5 K Ω (2 mark) (iii) the output resistance with feedback = 10 K Ω (2 mark)	
5		For a typical transistorized Colpitt's oscillator $C_1 = 0.05\mu\text{F}$, $C_2 = 0.5\mu\text{F}$ and $L = 200\text{ mH}$. $\beta = \frac{C_1}{C_2} = 0.1$ -----1 mark $A_v = 1/\beta = 10$ -----1 mark $C_T = \frac{C_1 C_2}{C_1 + C_2} = 0.045\mu\text{F}$ -----1 mark $F = \frac{1}{2\pi\sqrt{L C_T}} = 1678\text{ Hz}$ -----2 marks	
6		$V_1 = 2\text{ V}$, $V_2 = 2.5\text{ V}$ and $V_3 = 3.2\text{ V}$ $R_1 = 2\text{ K}\Omega$, $R_2 = 1.5\text{ K}\Omega$, $R_3 = 1.8\text{ K}\Omega$ and $R_F = 2\text{ K}\Omega$ $V_o = -R_F \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$ -----1 marks $V_o = -8.89\text{ V}$ -----2 marks If $V_o = -10\text{ V}$, $R_F = 2025\text{ K}\Omega$ -----2 marks	