

Q-1 A Select the correct options

12 marks
(2 marks each)

- (i) (c) purely resistive
- (ii) (a) $\frac{E_0}{\sqrt{2}}$
- (iii) (d) equal to the load
- (iv) (c) voltage regulator
- (v) (c) A
- (vi) (a) -30 V/m

B

(i) Superposition Theorem (1 mark)

In a network with two or more sources, the current or voltage for any component is the algebraic sum of the effects produced by each source acting separately. (Network should consist of bilateral and linear components only)

(ii) Wien's Bridge determines frequency of the source (1 mark)

(iii) Electric field at any pt. is the measure of force $\vec{F}$ on a test charge q_0 . (1 mark)

$$\vec{E}(r) = \lim_{q_0 \rightarrow 0} \frac{\vec{F}}{q_0}$$

The unit of $\vec{E}$ is N/C or V/m

(C) Fill in the blanks

5 marks
(1 mark each)

- (i) equal
- (ii) zero
- (iii) conservative field
- (iv) infinite
- (v) interchanged

Q-2 A

(i) Circuit Diagram of series LR circuit

1 mark


Derivation for

$i = I_0 \sin(\omega t - \theta)$ using complex numbers

5 marks.


Phasor. $V = ZI$

1 mark

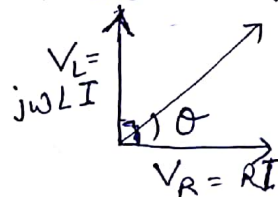

$|I|$ = rms current flowing thro' the circuit
 $\frac{V}{Z} = I = |I| e^{-j\theta}$

(ii) circuit diagram

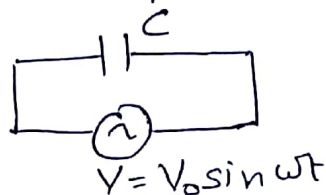


1 mark

$$i(t) = \omega C V_0 \sin(\omega t + \pi/2)$$

— 2 marks

phasor

— 1 mark

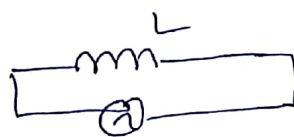

$$i(t) = i_0 \sin \omega t$$

— 1 mark

$$V(t) = \omega L I_0 \sin(\omega t + \pi/2)$$

Voltage across inductor leads the current — 2 marks
phasor — 1 mark


(2)

B

(i) Circuit Diagram of Maxwell's
L/C bridge

2 marks

Derivation for

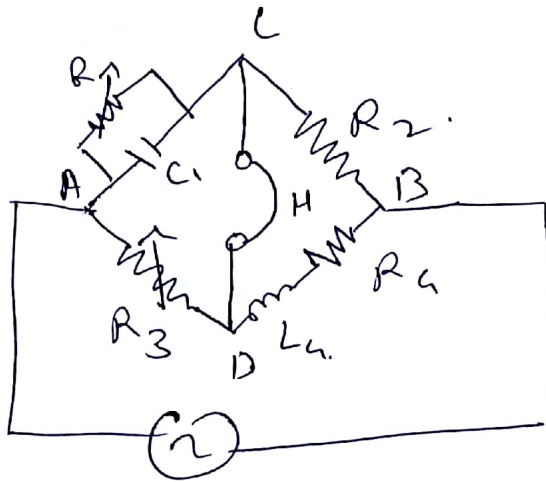

Derivation for

6 marks

$$R_4 = \frac{R_2 R_3}{R_1}$$

$$L_4 = R_2 R_3 C_1$$

(ii) Circuit Diagram

— 1 mark.

Derivation for


$$Z = |Z| e^{i\alpha} = R + j(\omega L - \frac{1}{\omega C})$$

where $|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$

$$\tan \alpha = \frac{(\omega L - \frac{1}{\omega C})}{R}$$

— 5 marks

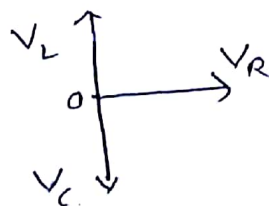Phasor for Resonance condition $\omega L = \frac{1}{\omega C}$




— 2 marks.

③

(c)

(i)

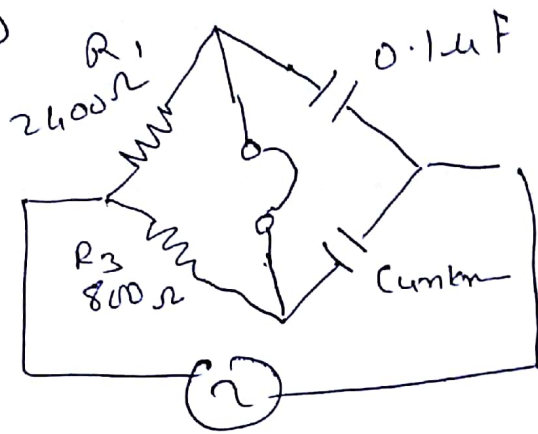

4 marks

At balance

$$Z_1 = Z_2$$

$$Z_2 = Z_4$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$R_1 \left(-\frac{j}{\omega C_x} \right) = \left(-\frac{j}{\omega C_2} \right) \times R_4$$

$$\therefore C_x = \frac{R_1}{R_4} C_2$$

$$= \frac{2400}{800} \times 0.1 \mu F$$

$$C_x = 0.3 \mu F$$

$$ii) \quad \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f = 112533 \text{ Hz}$$

- 4 marks

Q-3 A


(i) Statement of maximum power transfer theorem

2 marks

(ii) Proof of the theorem

6 marks

(ii)

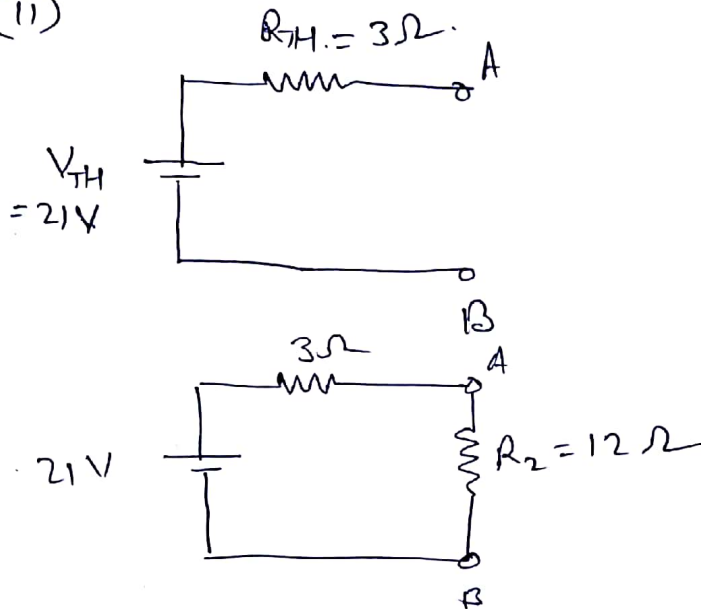

$$V_{R2} = 16.8 V$$

$$I_{R2} = 1.4 A$$

B

(i) Circuit diagram of Bridge rectifier.

Bridge

2 marks.

Working of the bridge rectifier
input & output waveforms

4 marks

2 marks.

(ii) Answer why NOR & NAND are universal gates.

2 marks.

Using NAND gates construct other gates

3 marks

Using NOR gates construct other gates

3 marks

(5)

(C) (i) Without Zener voltage across $1\text{ k}\Omega$ resistor will be

$$V_R = 1\text{ k}\Omega \times \frac{18\text{ V}}{1.27 \times 10^3}$$

$$= 14.2 \text{ V. volts}$$

This is greater than Zener breakdown voltage of 10 volts $\therefore$ Zener will go in the breakdown state. - 2 marks

Maximum current that can pass thr' Zener

$$P = 1\text{ W}$$


$$250\text{ mW} = 10\text{ volts} \times I$$

$$\therefore \underline{I = 25\text{ mA}}$$

- 2 marks

(ii) Circuit Diagram of +ve clamper

- 2 marks

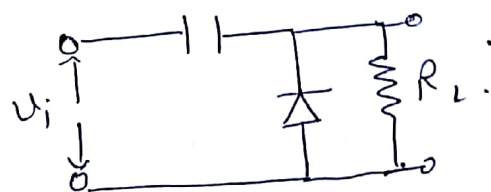

Voltage levels at the output

- 2 marks

$$0\text{ V} - 16\text{ V}$$

Q-4 A

(i) Derivation with figure of potential energy of pt-charge distribution, - 6 marks

Potential energy of pt-charge distribution,


$$W = \frac{1}{2} \sum_{i=1}^N \sum_{j=1}^N \frac{q_i q_j}{4\pi\epsilon_0 r_{ij}}, \quad i \neq j$$

$$W = \frac{1}{2} \sum_{i=1}^N q_i V(r_i) \quad \text{where}$$

$$V(r_i) = \sum_{j=1}^N \frac{q_j}{4\pi\epsilon_0 r_{ij}}$$

(ii)

8 marks.

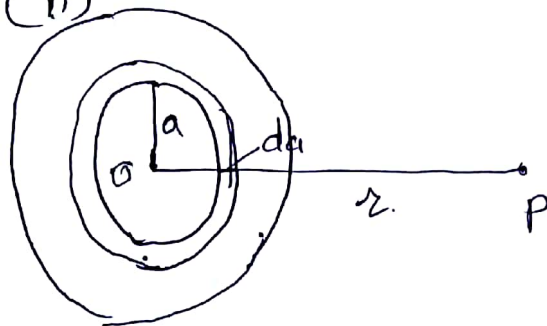

$$\sigma = \frac{q}{\pi R^2} \quad \because R \text{ radius of the disc}$$

$$V = \frac{2q}{(4\pi\epsilon_0) R^2} \left[\sqrt{R^2 + z^2} - z \right]$$

B

(i) magnetic field produced by solenoid.

Figure

- 3 marks

Derivation

5 marks

$$B = \frac{\mu_0 N I}{2L} (\cos \theta_1 + \cos \theta_2)$$

For very long solenoid

$$B = \frac{\mu_0 (N/L) I}{2}$$

(7)

(ii) Figure -


2 marks

Derivation

5 marks

$$B = \frac{\mu_0 I}{4\pi a} (\sin \theta_1 + \sin \theta_2)$$

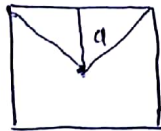at center of the square,
 B due current I carrying square



$$B = \frac{\mu_0 I}{4\pi a}$$

$$B = \frac{4 \mu_0 I}{4\pi a} (\sin \theta_1 + \sin \theta_2)$$

$$= \frac{4 \mu_0 I}{4\pi a} (2 \times \sin 45^\circ)$$

$$B = 1.41 \frac{\mu_0 I}{\pi a}$$

- 2 marks.

(c)(i)

$$B = \mu_0 n I$$

$$n = \frac{2000}{0.5}, \quad I = ?$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ N/A}^2$$

$$B = 0.01 \text{ T}$$

$$I = 1.99 \text{ A} \approx 2 \text{ A}$$

(8)

(ii)

$$\begin{aligned} V_B - V_A &= \frac{500 \text{ mJ}}{Q} \\ &= \frac{500 \times 10^{-3} \text{ J}}{0.1 \text{ C}} \\ &= 5000 \times 10^{-3} \text{ Volts} \\ &= 5 \text{ volt.} \end{aligned}$$

Q-5

(i) Definition of Q factor - 2 marks

Q factor is voltage magnification.
It is defined as a ratio of p.d. across the inductance or capacitance to the applied emf at resonance.

$$Q = \frac{V_L}{V} = \frac{\omega L}{R}$$

Derivation of - 2 marks

$$Q = \frac{\omega_0 L}{R}$$

Significance

1 mark

(ii) Statement of De Morgan's

2 marks

any theorem

Circuit equivalent &

3 marks

Truth table

iii) Circuit diagram of the filter circuit

- 1 mark


Action of capacitor with the waveforms

4 marks

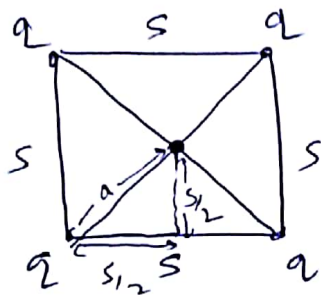(iv) Total work done

- 4 marks

$$W = \frac{1}{4\pi\epsilon_0} \frac{4\sqrt{2} q Q}{s}$$



Potential at the center due to 4 charges 'q' $V = \frac{1}{4\pi\epsilon_0} \frac{4q}{a}$

$$a^2 = \frac{s^2}{4} + \frac{s^2}{4}$$

$$a^2 = \frac{2s^2}{4}$$

$$a = \frac{\sqrt{2} s}{2} = \frac{s}{\sqrt{2}}$$

$$\therefore V = \frac{1}{4\pi\epsilon_0} \frac{4q}{s/\sqrt{2}}$$

$$\therefore W = \frac{1}{4\pi\epsilon_0} \frac{4qQ}{s/\sqrt{2}} = \frac{\sqrt{2}}{4\pi\epsilon_0} \frac{4qQ}{s}$$

(10)

v) Magnetic field at the center of current carrying square loop.

$$B = \frac{4 \times \mu_0 I}{4\pi a} (\sin \theta_1 + \sin \theta_2)$$

$$= \frac{4 \times \mu_0 I}{4\pi a} (2 \sin 45^\circ)$$

$$= \frac{4 \times \mu_0 I}{4\pi a} 2 \times 0.707$$

$$= \frac{1.41 \mu_0 I}{\pi a}$$

(vi) $\overline{V^2} = \frac{\int_0^T V^2 dt}{\int_0^T dt}$

$$\overline{V^2} = \frac{1}{T} \int_0^T V_0^2 \sin^2 \omega t dt$$

$$= \frac{V_0^2}{T} \int_0^T \left(\frac{1 - \cos 2\omega t}{2} \right) dt$$

$$= \frac{V_0^2}{2T} \left[T - \frac{\sin 2\omega t}{\omega} \right]_0^T$$

$$\overline{V^2} = \frac{V_0^2}{2}$$

$$V_{rms} = \sqrt{\overline{V^2}} = \frac{V_0}{\sqrt{2}}$$

- 2 marks

$$V_{av} \text{ for full cycle} = 0$$

- 1 mark

$$V_{av} \text{ for half cycle} = \frac{\int_0^{T/2} V dt}{\int_0^{T/2} dt}$$

- 2 marks

$$= \frac{2 V_0}{\pi}$$

(11)