

Q.P. Code : **10018**

(3 Hours)

[Total Marks : 60

- Note:** 1) Attempt all questions.
2) Figure to the right indicates Full mark.
3) Use of Non-programmable calculator is allowed.

1. Attempt **any two**-

- a) What are temperature transducers? Describe any one of them. 6
- b) Give a brief account of a common anode seven segment display. 6
- c) What is a LVDT? Describe the construction and the working principal. 6

2. Attempt **any two**-

- a) Draw the block diagram of a single trace CRO. Explain the function of the time base generator. 6
- b) Describe the digital to analog conversion using weighted resistor. 6
- c) Write a note on transistorised voltmeter. 6

3. Attempt **any two**-

- a) With the help of block diagram explain working of instrumentation amplifier as light intensity meter. 6
- b) Draw neat circuit diagram of negative clipper with help of waveforms explain its working. 6
- c) What is band pass filter? Draw frequency response of a band pass filter, define Q factor calculate centre frequency if $f_H=2500\text{Hz}$. and $f_L=1800\text{Hz}$. 6

4. Attempt **any two**-

- a) With help of neat diagram explain working of boost regulator using Max 631. 6
- b) Draw block diagram of fixed output voltage regulator with short circuit protection. Explain how the circuit works. 6
- c) Design a negative voltage regulator using LM 337 for input voltage is equal to -20 volts and $V_{ref} = -1.24$ volts. Draw circuit diagram for design values. 6

5. Attempt **any four** -

- a) What is a load cell? 3
- b) Draw the circuit diagram for a seven segment display. 3
- c) What is a sweep generator. 3
- d) Draw the circuit diagram and frequency response of wide band pass filter. 3
- e) What are characteristics of linear IC voltage regulator. 3
- f) What is role of diodes in positive adjustable voltage regulator using LM 317. 3

381C8C5EE3389FCC0E1CC138DC341011