

Q.P. Code : **10029**

(3 Hours)

[Total Marks :100]

- Note:** 1) Figures to the right indicate full marks.
2) All questions are compulsory.
3) Neat diagrams should be drawn whenever necessary.
4) Use of non-programmable calculators/log tables is allowed.
5) Symbols have their usual meaning unless otherwise stated.

1. a) Attempt **any TWO**:
 - i) Discuss the phenomenon of thermionic emission in metals. Obtain Richardson -Dushman equation for the emission current density. **10**
 - ii) State the salient features of superconductivity. Explain how the superconducting transition temperature varies with magnetic field. **10**
 - iii) Discuss Kronig Penney model for the motion of an electron in a periodic potential. Explain the formation of energy bands on the basis of this model. **10**
2. Attempt **any TWO**:
 - i) What is ferromagnetism? Discuss Weiss field theory of Ferromagnetism. Deduce Curie Weiss law. **10**
 - ii) Obtain an expression for concentration of electrons in an intrinsic semiconductor. **10**
 - iii) Set up the continuity equation for the charge carriers in an extrinsic semiconductor. **10**
3. Attempt **any TWO**:
 - i) Draw the circuit of a transistorized monostable multivibrator. Explain its working with the help of different waveforms. **10**
 - ii) Sketch the basic structure of an n-channel JFET. Explain the working along with characteristic curves. **10**
 - iii) Explain the use of SCR as full wave rectifier. Derive the equation for its output voltage **10**
4. Attempt **any TWO**:
 - i) With the help of schematic diagram, explain how 555 timer can be used as an astable multivibrator. **10**
 - ii) Explain how OPAMP can be used in a log amplifier. Derive the relation between the output and the input. **10**
 - iii) Explain the working of TTL NAND gate **10**

[TURN OVER]

Con. 1094-17.

5. Attempt **any FOUR**:

- i) Explain collision time and relaxation time of free electrons in metals. 5
 - ii) Write a note on Type I superconductors. 5
 - iii) State any two applications of Hall Effect. 5
 - iv) Write a note on optocouplers. 5
 - v) Explain the following terms used for a DIFF amplifier : input bias current, input offset voltage and CMRR 5
 - vi) Explain different types of registers. 5
-