

- Paper solution -

Subject - EDC (SE/electrical/SEM-III/DEC-17)

Q.P. Code - 23921.



(1)

Q.1. (a) Construction of JFET.


(5M)

Constructional circuit diag of n & p channel JFET with symbols - 3M.

Explanation - 2M.

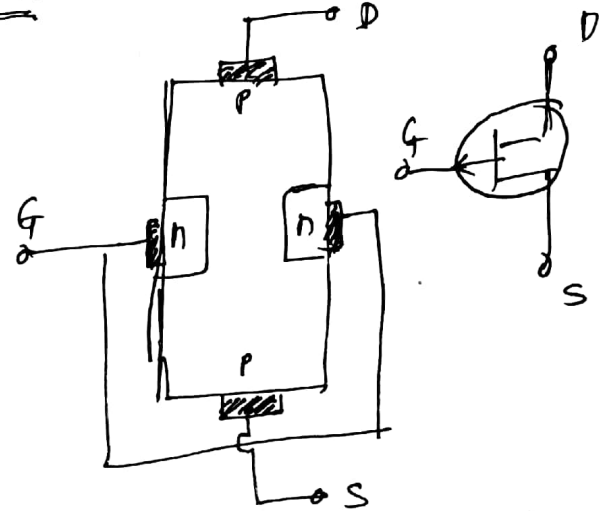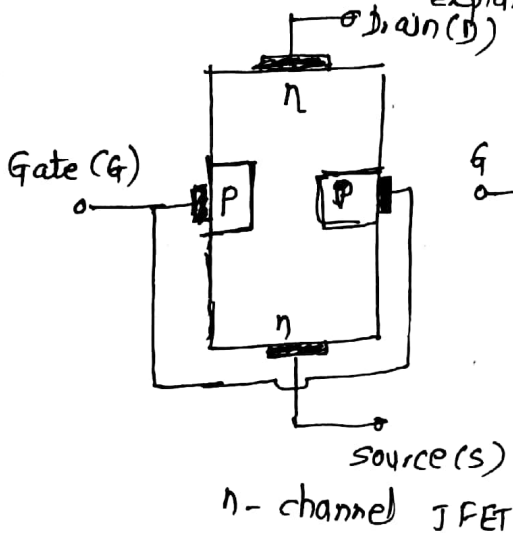

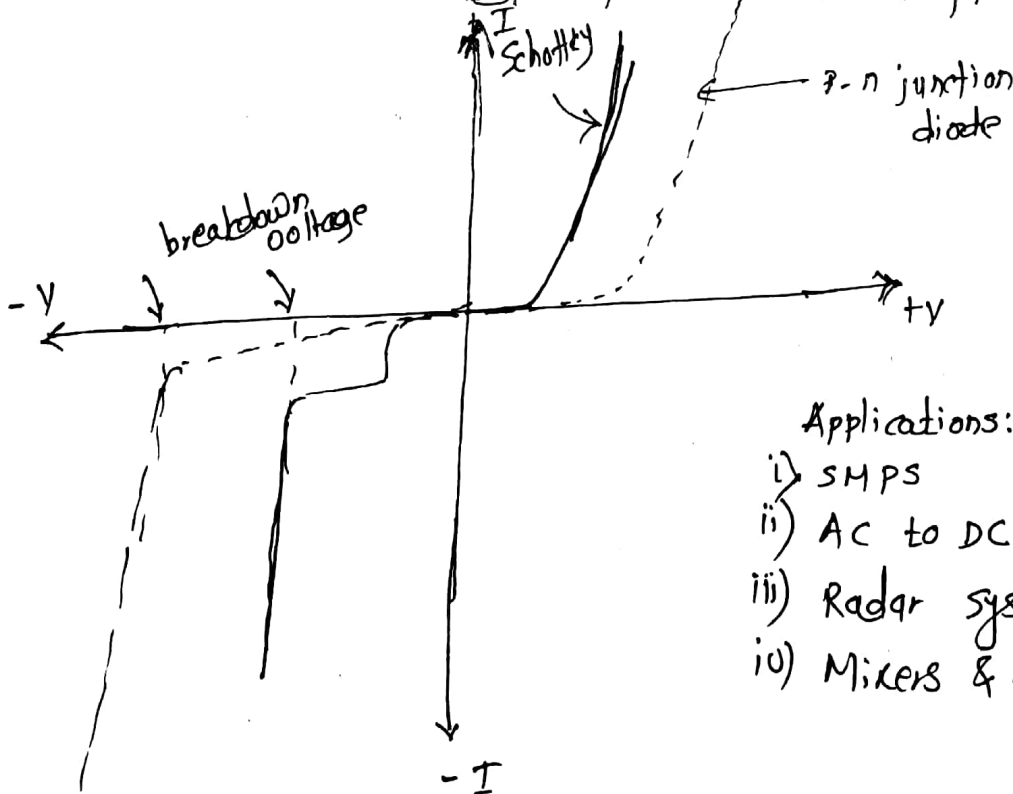(b) V-I chs:- 2M Explanation - 1M & applications - 2M. (5M)




Applications:-

- i) SMPS
- ii) AC to DC converters.
- iii) Radar systems.
- iv) Mixers & detectors in comm' sys.

(c) h-parameter Model of BJT.


(5M)

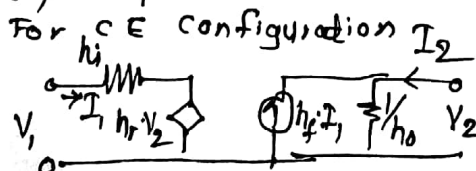


- diag. - 2M.
- defining parameters - 2M
- explanation - 1M.

(d) Darlington pair configuration

(2)

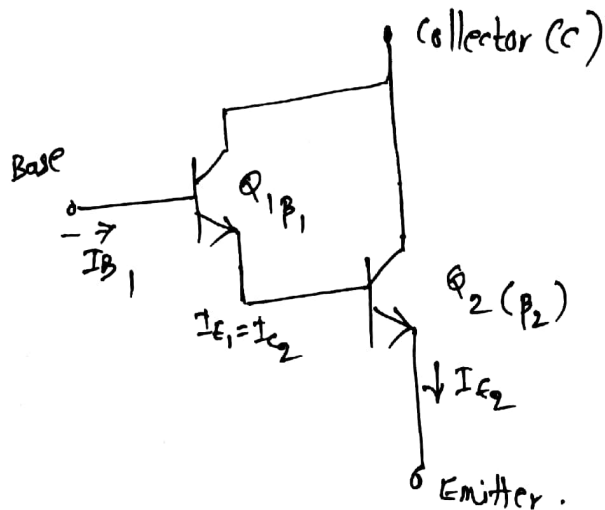

Darlington connection

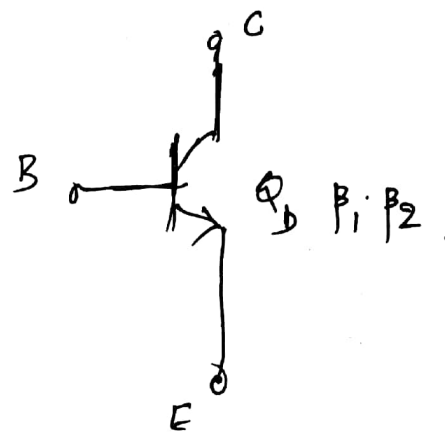

Equivalent darlington transistor.

Diag. - 2M. Explanation - 1M.

Why to use in BJT - 2M.

(e) Hartley Oscillator.

(5M)

Given: $L_1 = 0.5 \text{ mH}$, $L_2 = 0.5 \text{ mH}$, $C = 100 \text{ pF}$.

$$f_0 = \frac{1}{2\pi \sqrt{L_{eq} \cdot C}} \quad \text{where } L_{eq} = L_1 + L_2$$

$$\therefore f_0 = \frac{1}{2\pi \sqrt{1 \times 10^{-3} \times 100 \times 10^{-12}}}$$

$$= \underline{503.292 \text{ KHz.}}$$

Correct solution 5M.

(f) Advantages of -ve f/b.

(5M)

- Any 5 advantages with mathematical expression

e.g. B.W. Increases then

$$\frac{A_v}{f} = \frac{A_v}{(1 + A \cdot \beta)} \quad \text{B.W.}_f = \text{B.W.} \times (1 + A \cdot \beta)$$

Que.2 (a) Various types of -ve f/b amplifiers

(10M) (5)



Parameter i) Voltage series ii) Current series iii) Voltage shunt iv) Current shunt

- I] Block Diagram - 2M.
 II] Feedback gain - 2M.
 III] Bandwidth - 2M.
 IV] Noise - 1M
 v) Freqⁿ distortion - 1M.
 vi) stability - 1M
 vii) Amplifier type - 1M.

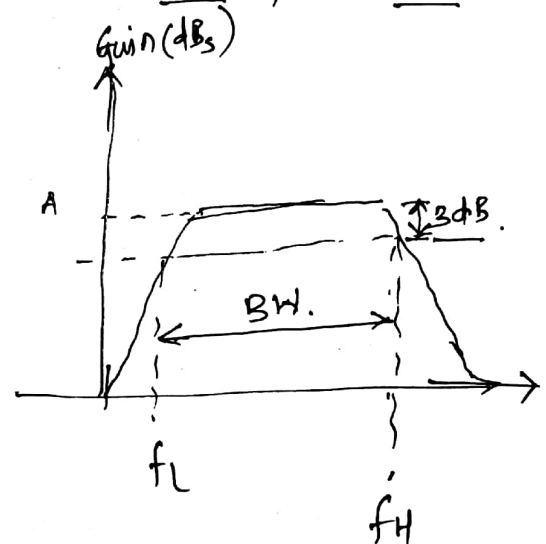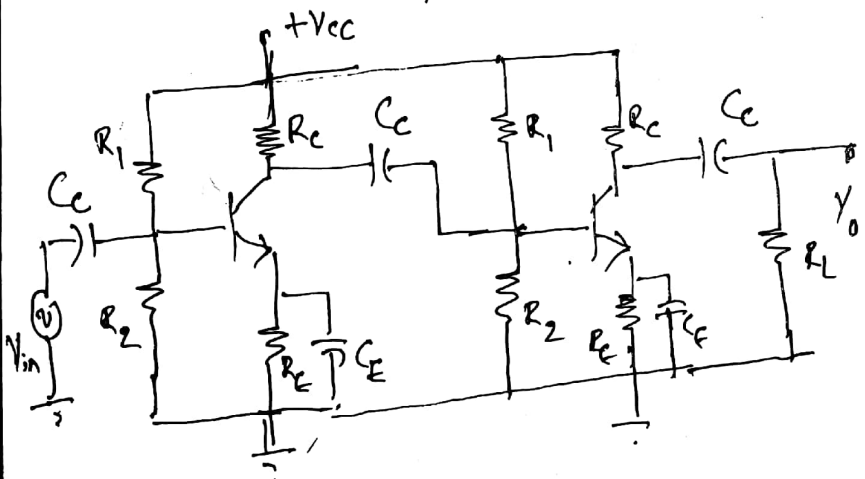
(b) Multistage RC coupled transistor Amplifier.

(10M)

- Diag. - 3M, Explanation - 3M Freqⁿ Response diag. 2M explanation 2M.



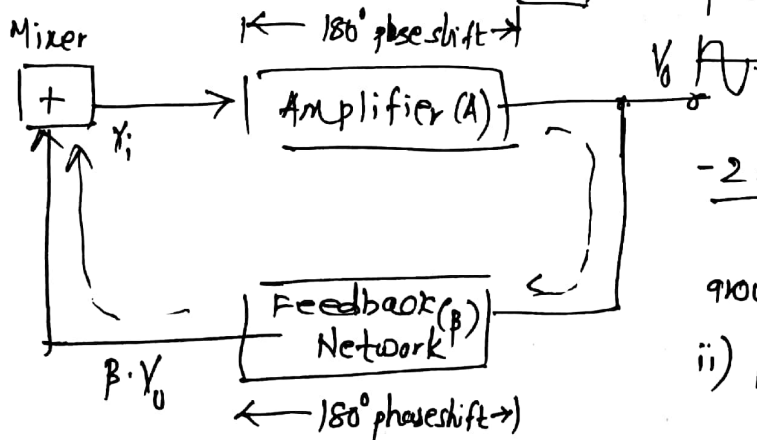Que.3 (a) Barkhausen's Criteria - 4M RC - phase shift oscillator - 6M.



- 2 conditions

- i) Total phase shift around loop either 0° or 360°
 ii) $|A \cdot \beta| \geq 1$

R-C - phase shift oscillator either using BJT or FET.

(b). Comparison betⁿ C, LC & CLC filters.

(10M) (4)

Parameters - Diag. - 2M.

Expression for ripple factor - 2M.

Surge current thro' diode - 2M.

switchover for - 1M.

Voltage regulation - 1M.


Place of filter - 1M.

Appn - 1M or any other suitable point

Que. (4) - (a) Various biasing techniques used in BJT.

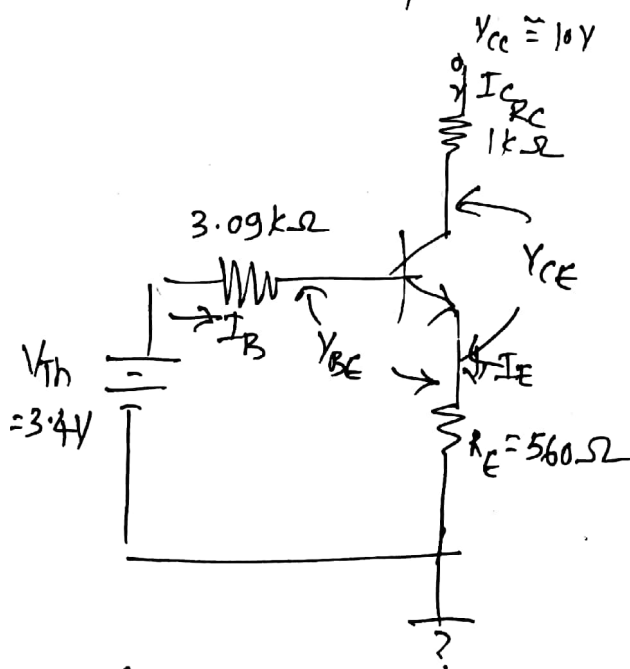i) Fixed Bias ii) Emitter to Base bias & iii) Voltage divider or potential divider or self bias. - 2M.

Thevenin's equivalent ckt. with $R_{Th} = 3.09 k\Omega$ & $V_{Th} = 3.4V$ - 3M.



$$\left. \begin{aligned} I_{BQ} &= 45.35 \mu A \\ I_{CQ} &= 4.53 mA \\ I_{EQ} &= 4.575 mA \\ V_{CEQ} &= 2.9V \end{aligned} \right\} 5M.$$

(b) D-Type MOSFET.

(10M)

constⁿ diag. - 2M. Explanation - 1M.

Working with explanation and i/p & o/p chs - 7M.

Q.5. (a) complete AC analysis using either h-parameter or r_e Model - 10M. ^(10M) (5)

Expressions for. $A_I, A_{IS}, R_i, R_i', R_o, R_o', A_v, A_{v_s}$

(b) Differentiate JFET & MOSFET

Parameters - symbol - 1M.

Constn - 2M.

I/p Impedance - 2M.

biasing Methods used - 2M.

I/p & o/p cbs - 3M. or any other suitable point.

Que. 6 (a) UJT Relaxation oscillator.

ckt. diag. & waveforms - 5M.

Explanation - 5M.

(b) Thermal stabilization - 5M, compensation techniques - 5M.

(c) Concept of DC Load Line.

Mathematical expression for CE configuration - 5M.

Diagram - 2M.

Explanation - 3M.