

- MODEL ANSWER -
 SUBJECT:- Electronic Devices & Circuits.
 SE (Electrical / SEM-III / CBCGS / REV-2016 / MAY-2018.

Que. 1:- (a) Drift Current

Proper explanation (with fig.) - $2\frac{1}{2}$ M.

Diffusion Current

Proper explanation - $2\frac{1}{2}$ M.

(b) Concept of DC Load Line in CE configuration.

- Fig of CE Amp^r & with proper detail

diag. of DC Load line - $2\frac{1}{2}$ M.

- Mathematical Expressions with explanation $2\frac{1}{2}$ M.

(c) since FET is unipolar device thermal runaway doesn't exist. 2 M. for constⁿ details of FET & 3M for explanation.

(d) r_e Model of BJT

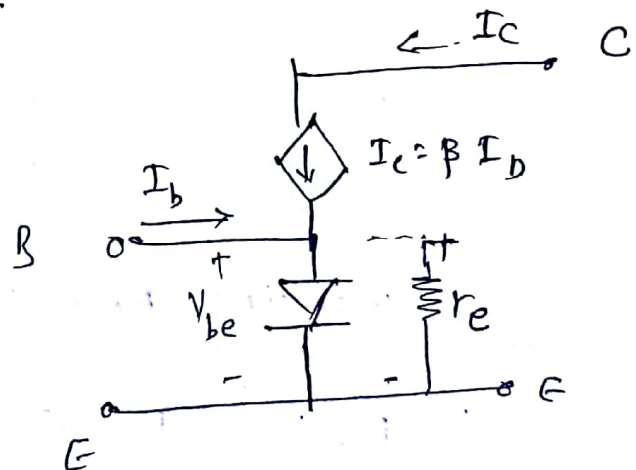
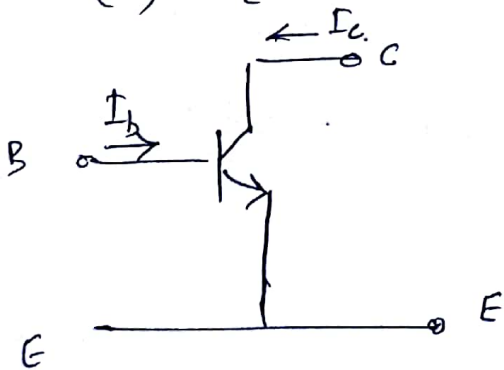


Fig. - 3M, explanation - 2M.

(e) Barkhausen's Criteria. 2 conditions. with figs.

- Fig. - 2M, explanation - 3M.

Que. (2):- (a) I/p ch^s - Fig. with BJT in CE configuration.

O/p ch^s - Fig. \rightarrow 5M.

Explanation - 5M.

Que. 2 (b) Different biasing techniques.

- Mentioning all biasing techniques - 2M.

- Any biasing method (preferably potential divider biasing) Fig. - 4M.

Explanation - 4M.

Que. 3 (a) Working principle with Fig. Enhancement type MOSFET. 5M.
" " " Depletion " " 5M.

Que. 3 (b) Proper circuit diagram of bridge rectifier with LC Filter & Waveforms - 5M.

Explanation: - 5M.

Que. 4 (a) Detail Block diag. of current series feedback amp^r. - ~~4~~ 2½ M.

Expression for Z_p Impedance - $2\frac{1}{2} M$

" " o/p " - $2\frac{1}{2} M$

" " voltage gain - $2\frac{1}{2} M$.

Que. 4 (b) - Working principle of

I] P-N Diode - 1M

II] FET - 3M

III] L-C Tank circuit - 3M

IV] Schottky Diode - 3M.

Que. 5 (a) Circuit diag of Colpitt Oscill^r - $2\frac{1}{2} M$

Working principle: - $2\frac{1}{2} M$.

Expression for freqⁿ of oscillation with explanation - 5M.

Que. 5(b). BJT as CE Amp^r - ckt. diag. - 2M.

h-parameter model fig. - 3M.

Expression for voltage gain with details - 5M.

Que. 6(a) UJT Relaxation Oscillation

Fig. & Waveforms - 4M.

Explanation - 3M.

(b) Zener Diode as voltage regulator.

Fig. with Zener ch^s - 4M.

Explanation - 3M.

(c) Two port network.

Fig. - 3M.

Any detail (with h parameter or r_e model)
Explanation - 3M.

(d) I/p ch^s - 3M

O/p ch^s - 3M.