

Marks distribution -

Q.1 - a - Circuit diagram - 2M

Explanation - 3M

b - Structural diagram - 2M
Operation - 3M

c - Diagram - 1M
Explanation - 4M

d - 1 Mark for each Comparison

e - Circuit diagram - 2M
Explanation - 1M
wave forms - 3M

Q.2 - a - Structure characteristics - 5M
Static char. - 5M

b - circuit diagram - 2M
Explanation - 3M
input & output waveforms - 3M
Formulas / derivation / Application - 2M

Q.3 a - circuit diagram - 3M
Working - 2M
wave form - 3M

b - circuit diagram - 2M
Calculation - 2M
working - 2M
waveforms - 4M

Q-4 - a - Multiple PWM - 5M
Sinusoidal PWM - 5M

b - Average output voltage - 2.5M

ΔV_c - 2.5M

ΔI - 2.5M

critical L & C - 2.5M

Q-5 - a - * Unidirectional

→ circuit diagram - 1.5M

→ working - 1.5M

→ waveforms - 2M

* Bidirectional

→ circuit diagram - 1.5M

→ working - 1.5M

→ waveforms - 2M

b - * class E [5M], class D [5M]

circuit diagram - 1.5M

working - 1.5M

waveforms - 2M

Q-6 - a - efficiency - 3.5M

Form Factor - 3.5M

Power factor - 3M

b - 5M

c - circuit diagram - 1.5M

working - 1.5M

waveforms - 2M

Q.4- b- $V_s = 14V$, $\alpha = 0.25$, $f = 25\text{KHz}$, $L = 160\mu\text{H}$
 $C = 200\mu\text{F}$, $I_o = 1.25\text{A}$

$V_s \rightarrow$ Source Voltage, $\alpha \rightarrow$ duty cycle
 $f \rightarrow$ frequency, $L \rightarrow$ inductor, $C \rightarrow$ Capacitor
 $I_o \rightarrow$ Average load current

(i) Average output voltage (V_o)

$$V_o = -V_s \cdot \frac{\alpha}{1-\alpha} = -14 \times \frac{0.25}{(1-0.25)}$$

$$V_o = -4.66\text{V}$$

(ii) Peak to peak output voltage ripple (ΔV_c)

$$\Delta V_c = \frac{I_o \cdot \alpha}{f \cdot C} = \frac{1.25 \times 0.25}{20 \times 10^3 \times 160 \times 10^{-6}}$$

$$\Delta V_c = 0.077\text{V}$$

(iii) Peak to peak ripple current of inductor (ΔI)

$$\Delta I = \frac{V_s \cdot \alpha}{f \cdot L} = \frac{14 \times 0.25}{25 \times 10^3 \times 160 \times 10^{-6}}$$

$$\Delta I = 0.87\text{A}$$

(iv) critical value of L and C

$$\text{Load resistance (R)} \Rightarrow R = \frac{V_o}{I_o} = \frac{4.66}{1.25}$$

$$R = 3.73\Omega$$

$$L = \frac{\alpha(1-\alpha)R}{2f} = \frac{0.25(1-0.25)3.73}{2 \times 25 \times 10^3}$$

$$L = 13.9\mu\text{H}$$

$$C = \frac{\alpha}{2fR} = \frac{0.25}{2 \times 25 \times 10^3 \times 3.73} \Rightarrow C = 1.34\mu\text{F}$$

Q.6 - (a) $V_s = 230 \text{ V}$, $f = 50 \text{ Hz}$, $R = 10 \Omega$, $\alpha = 45^\circ$

$V_s \rightarrow$ Source Voltage, $f \rightarrow$ frequency

$R \rightarrow$ Load Resistance, $\alpha \rightarrow$ Firing Angle

(i) Rectification efficiency (η)

$$\eta = \frac{\text{Output power}}{\text{Input power}} = \frac{V_o \cdot I_o}{V_{on} \cdot I_{on}}$$

$$\therefore V_o = \frac{2V_m}{\pi} \cos \alpha = \frac{2\sqrt{2} \times 230}{\pi} \cos 45^\circ = 146.42 \text{ V}$$

$$I_o = \frac{V_o}{R} = \frac{146.42}{10} = 14.64 \text{ A}$$

$$V_{on} = V_s = 230 \text{ V}$$

$$I_{on} = I_o = 14.64 \text{ A}$$

$$\eta = \frac{146.42 \times 14.64}{230 \times 14.64} = 0.6366 = 63.66 \%$$

(ii) Form Factor (FF)

$$FF = \frac{V_{on}}{V_o} = \frac{230}{146.42} = 1.57$$

(iii) Input Power Factor (PF)

$$PF = \text{CDF (current distortion factor)} \times \text{DF (input distortion factor)}$$

$$= \frac{2\sqrt{2}}{\pi} \cos \alpha = \frac{2\sqrt{2}}{\pi} \cos 45^\circ$$

$$PF = 0.63$$