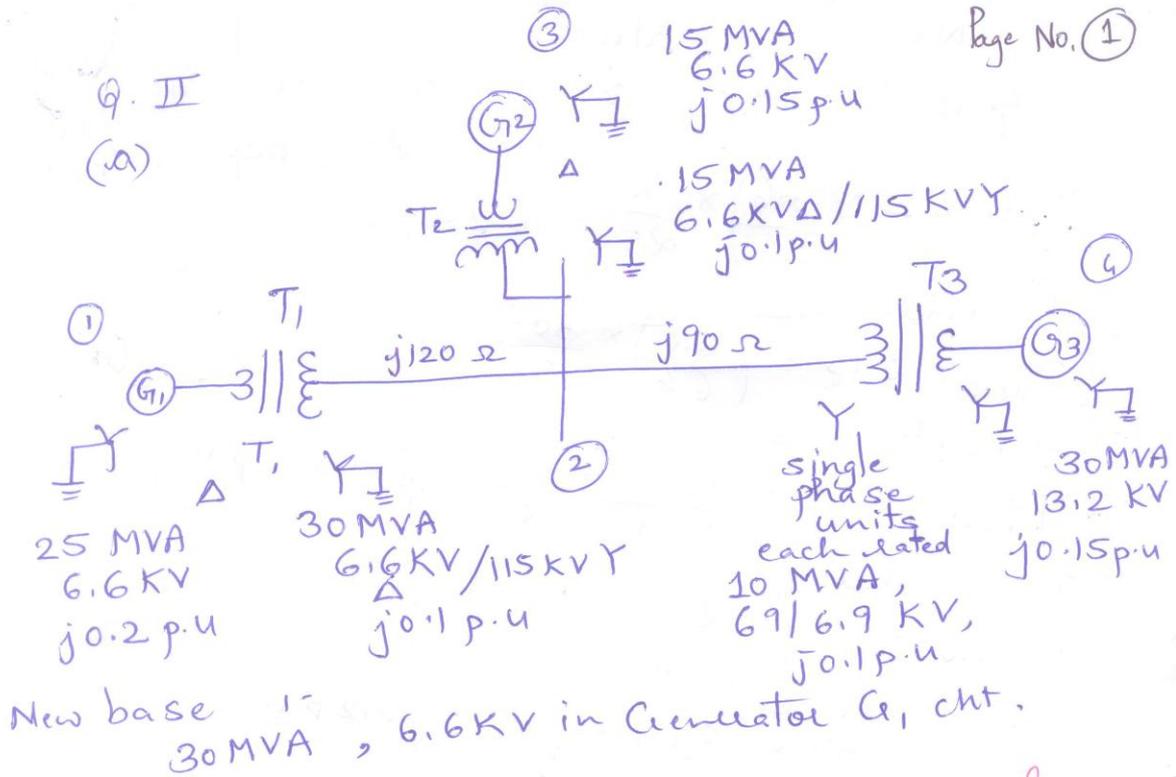


Q. II
(a)



Solution - Base power = 30 MVA

Base voltages in 4 sections

Section ① generator G₁
Base volt. = 6.6 KV

Section ②, ~~generator G₂~~ Transmission line
Base volt. = 115 KV

Section ③ generator G₂
Base volt. = 6.6 KV

Section ④ generator G₃

Transformer 3, 3-φ transformer 30 MVA,
line volt. ratio. $\frac{\sqrt{3} \times 69}{\sqrt{3} \times 6.9}$
119.508 / 11.9508 KV

Base volt. for section ④, (n = ?)
 $\frac{115}{n} = \frac{119.508}{11.9508}$ n = 11.5 KV

New p.u. values.

(1) generator G_1 , $Z_{pu\ new} = Z_{pu\ old} \left(\frac{Base\ KV\ old}{Base\ KV\ new} \right)^2 \frac{Base\ MVA\ new}{Base\ MVA\ old}$

$$X_{pu\ new} = 0.2 \times \left(\frac{6.6}{6.6} \right)^2 \times \frac{30}{25} = j0.24\ p.u.$$

(2) generator G_2

$$X_{pu\ new} = 0.15 \times \left(\frac{6.6}{6.6} \right)^2 \times \frac{30}{15} = j0.3\ p.u.$$

(3) generator G_3

$$X_{pu\ new} = 0.15 \times \left(\frac{13.2}{11.5} \right)^2 \times \frac{30}{30} = j0.1976\ p.u.$$

(4) Transformer T_1

$$X_{pu\ new} = 0.1 \times \left(\frac{6.6}{6.6} \right)^2 \times \frac{30}{30} = j0.1\ p.u.$$

(5) Transformer T_2

$$X_{pu\ new} = 0.1 \times \left(\frac{6.6}{6.6} \right)^2 \times \frac{30}{15} = j0.2\ p.u.$$

(6) Transformer T_3

$$X_{pu\ new} = 0.1 \times \left(\frac{119.508}{115} \right)^2 \times \frac{30}{30} = j0.1079\ p.u.$$


(7) Base impedance for transmission lines

$$Z_{base} = \frac{(Base\ KV)^2}{Base\ MVA} = \frac{(115)^2}{30} = 440.83\ \Omega$$

$$X_{pu\ line\ 1} = \frac{j120}{440.83} = j0.272\ p.u.$$

$$X_{pu\ line\ 2} = \frac{j90}{440.83} = j0.204\ p.u.$$

p.u. impedance diagram

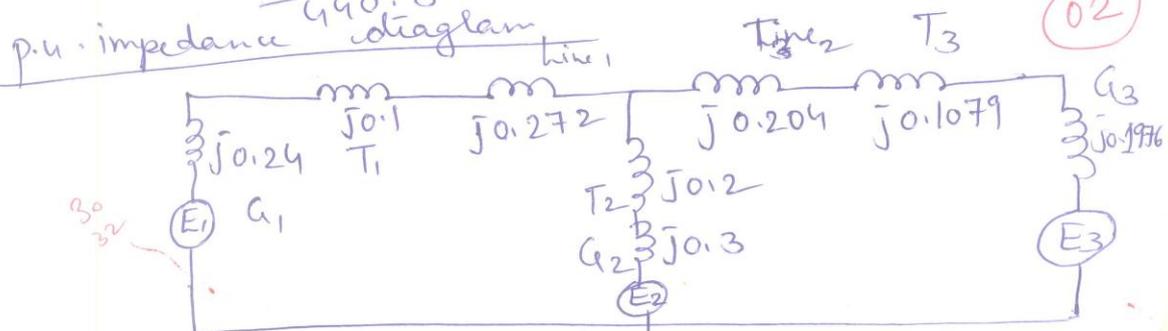

06

02

Q. III (b) 3- ϕ , 66 kV, 50 Hz $R = 9.6 \Omega$
 $L = 0.097 \text{ H}$, $C = 0.765 \mu\text{F}$ per phase

$P_L = 24 \text{ MVA}$, $V_L = 66 \text{ kV (line)}$ $\cos \phi_L = 0.8$
 Nominal T₆ ckt. = $209.95 \angle -36.87^\circ \text{ P.f.}$

$V \cdot R^n = 9$
 $\gamma = 9$ $I_L = \frac{24 \times 10^6}{\sqrt{3} \times 66 \times 10^3} = 209.95 \angle -36.87^\circ \text{ P.f.}$
 $X = 2\pi \times 50 \times 0.097 = 30.47 \Omega/\text{ph}$ (14.7%
93.6%)

$Y = j\omega C = 2\pi \times 50 \times 0.765 \times 10^{-6} \angle 90^\circ$
 $= 2.403 \times 10^{-4} \angle 90^\circ \text{ S/ph}$

$Z = R + jX_L = 9.6 + j30.47$

$V_L = \frac{66 \times 10^3}{\sqrt{3}} = 38.105 \times 10^3 \text{ V (phase voltage)}$
 $= 31.94 \angle 72.51 \Omega/\text{ph}$

$A = D = 1 + \frac{ZY}{2} = 1 + \frac{31.94 \angle 72.51 \times 2.403 \times 10^{-4} \angle 90^\circ}{2}$
 $= 0.996 \angle 0.066^\circ$

$B = Z(1 + \frac{ZY}{2}) = 31.88 \angle 72.54$

$C = Y = 2.403 \times 10^{-4} \angle 90^\circ$
 $V_S = AV_L + BI_L = 0.996 \angle 0.066 \times 38.105 \times 10^3 \angle 0 + 31.88 \angle 72.54 \times 209.95 \angle -36.87^\circ$
 $= 43.57 \text{ kV} \angle 5.19^\circ$ (05)

$V_S(\text{line}) = \sqrt{3} \times 43.57 \text{ kV} = 75.47 \text{ kV}$
 $I_S = CV_L + DI_L = 2.40 \times 10^{-4} \times 38.105 \times 10^3 \angle 0 + 0.996 \angle 0.066 \times 209.95 \angle -36.87^\circ$
 $= 203.76 \angle -34.74^\circ$ (03)

$\cos \phi_S = \text{Sending end p.f.} = \cos(5.19 + 34.74) = 0.7669$

$V_L(\text{NL}) = \frac{|V_S|}{|A|} = \frac{75.47 \times 10^3}{0.996} = 75.77 \text{ kV}$

$\% \text{V.R.} = \frac{V_L(\text{NL}) - V_L(\text{FL})}{V_L(\text{FL})} \times 100 = \frac{75.77 - 66}{66} \times 100 = 14.81\%$ (01)

$\text{Trans. } \eta = \frac{\frac{P_L}{\cos \phi_L}}{\frac{\sqrt{3} V_S I_S \cos \phi_S}} = \frac{24 \times 10^6 \times 0.8}{\sqrt{3} \times 75.47 \times 10^3 \times 203.76 \times 0.7669} \times 100 = 93.88\%$ (01)

Q. IV (b)

Consider a string insulator with 3 units
 Capⁿ. from each unit to the tower is 12.5% of capⁿ. of each unit.

$K = 0.125$

$V_3 = 11 \text{ KV. (max value)}$

Applying KCL at 'A'

$i_2 = i_1 + i_1' \quad \therefore V_2 j\omega C = V_1 j\omega C + V_1 j\omega 0.125C$
 $V_2 = V_1 + 0.125 V_1 = 1.125 V_1$

Applying KCL at 'B'


$i_3 = i_2 + i_2' \quad \therefore V_3 j\omega C = V_2 j\omega C + (V_1 + V_2) \times j\omega 0.125C$

$V_3 = V_2 + (V_1 + V_2) \cdot 0.125$
 $= V_2 + V_1 \cdot 0.125 + V_2 \cdot 0.125$
 $= (1 + 0.125) V_2 + V_1 \cdot 0.125$
 $= 1.125 V_2 + V_1 \cdot 0.125 = (1.125)^2 V_1 + V_1 \cdot 0.125$
 $= 1.265 V_1 + V_1 \cdot 0.125$
 $V_3 = 1.39 V_1 \quad \therefore V_1 = \frac{11 \text{ KV}}{1.39} = 7.913 \text{ KV}$

Now, $V_3 = 11 \text{ KV}$

$V_2 = 1.125 \times 7.913$
 $= 8.902 \text{ KV}$

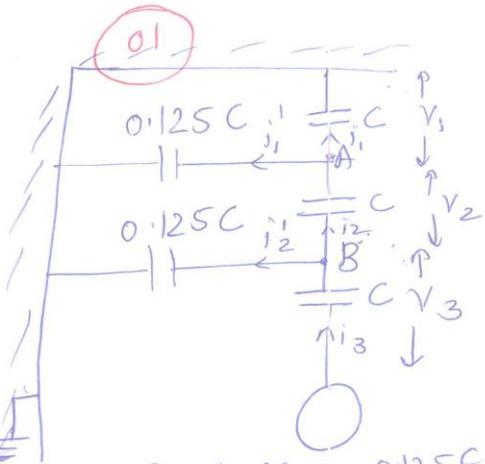∴ Max^m volt. across the string for which it can be used = $V_1 + V_2 + V_3$
 $= 7.913 + 8.902 + 11$
 $= \underline{27.815 \text{ KV (phase volt.)}}$




05

02

01

Q. (V)

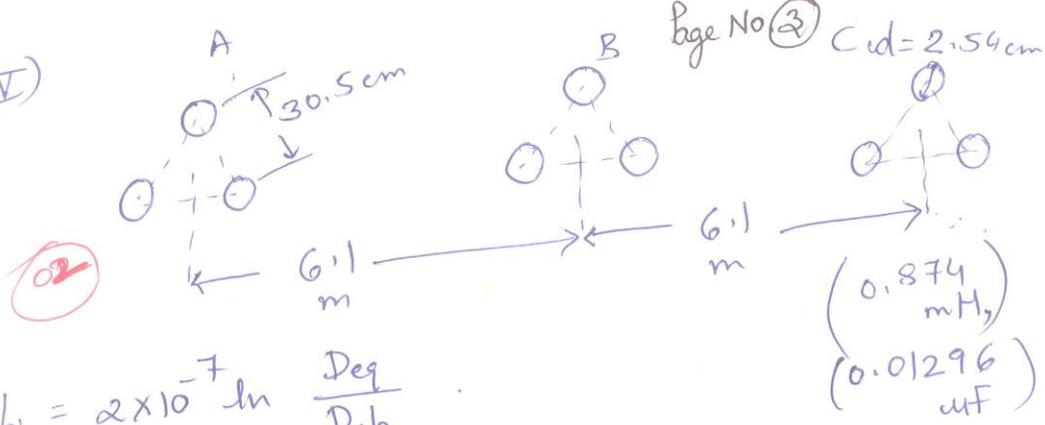

$$L = 2 \times 10^{-7} \ln \frac{D_{eq}}{D_{sb}}$$

* $D_{eq} = \sqrt[3]{D_{ab} D_{bc} D_{ca}}$
 (01) $= \sqrt[3]{6.1 \times 6.1 \times 12.2} = 7.685 \text{ m}$

(01) $D_{sb} = \sqrt[9]{(r' \times 30.5 \times 30.5)^3} = \sqrt[9]{0.7788 \times 1.27 \times 30.5 \times 30.5}$
 $= 9.726 \text{ cm} = 0.09726 \text{ m}$

(02) $L_{ph} = 2 \times 10^{-7} \ln \frac{7.685}{9.726 \times 10^{-2}} \text{ H/m}$
 $= 0.2 \times 4.3696 = 0.8739 \text{ mH/km/phase}$

(02) $C = \frac{2\pi \epsilon_0 F_{lm}}{\ln \left(\frac{D_{eq}}{D_{sb}} \right)} = \frac{2\pi \times 8.854 \times 10^{-12}}{\ln \left(\frac{7.685}{10.57 \times 10^{-2}} \right)}$

(01) $D_{sb} = \sqrt[3]{1.27 \times 30.5 \times 30.5} = 10.57 \text{ cm}$
 $= \frac{55.6 \times 10^{-12+9}}{4.286} \text{ uF/km}$

$= 12.972 \times 10^{-3}$
 $C_{ph} = \frac{0.012972 \text{ uF/km}}{\text{per phase}}$

(01) or find mutual GMD.
 * Since the distance between the subconductors per phase is very less as compared to the distance between the adjacent phases.