

Q.P code: 40093

Q1. a) $h_{21} = -h_{12}$ ← condition for reciprocity of h-parameters.

b) $L\{f(t)\} = L\{r(t-a)\}$
 $= \frac{e^{-as}}{s^2}$

c) no. of possible trees.

no. of nodes	no. of branches →			
	1	2	3	4
1	1	1	0	0
2	-1	0	1	1
3	0	-1	-1	-1


$$|A A^T| = \begin{vmatrix} 1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 1 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & 1 \end{vmatrix} = \begin{vmatrix} 1+1+0+0 & -1+0+0+0 \\ -1+0+0+0 & 1+0+1+1 \end{vmatrix} = \begin{vmatrix} 2 & -1 \\ -1 & 3 \end{vmatrix}$$

$$= 6 - (-1) = 7$$

∴ No. of possible trees = 7

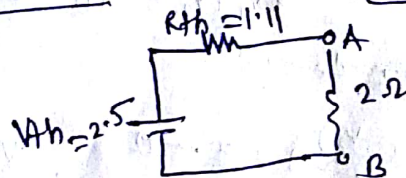d) Thevenin's equivalent network across A-B

$V_{th} = 2.5 \text{ Volts}$, $R_{th} = 1.11 \Omega$



$$I_{2\Omega} = \frac{V_{th}}{R_{th} + 2} = \frac{2.5}{1.11 + 2} = \frac{2.5}{3.11}$$

$I_{2\Omega} = 0.80 \text{ Amps}$

e) Explanation of super node concept


f)
$$\frac{V_1}{I_1} = \frac{s^4 + 2.5s^2 + 1}{s^3 + 1.5s} \Omega$$

$$\frac{V_2}{I_1} = \frac{1}{s^3 + (1.5)s} \Omega$$

Que 2

a) Superposition theorem.

Step 1: 1A source acting alone

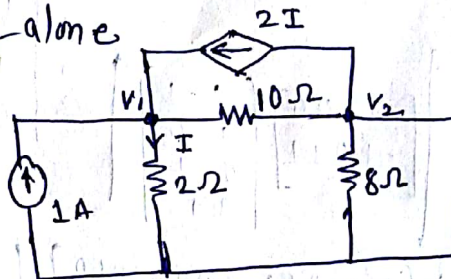

Kcl at node ①

$$-1 - 2I + I + \frac{V_1 - V_2}{10} = 0$$

$$-1 - 2\left(\frac{V_1}{2}\right) + \frac{V_1}{2} + \frac{V_1 - V_2}{10} = 0$$

$$-1 - V_1 + \frac{V_1}{2} + \frac{V_1 - V_2}{10} = 0$$

$$-10 - 10V_1 + 5V_1 + V_1 - V_2 = 0$$

$$-4V_1 - V_2 = 10$$

$$4V_1 + V_2 = -10 \quad \text{--- (1)}$$

Kcl at node ②

~~$$-\frac{V_1 - V_2}{10} + 2I = 0$$~~

~~$$-\frac{V_1}{10} + 2\left(\frac{V_1}{2}\right) = 0$$~~

~~$$-V_1 + 10V_1 = 0$$~~

~~$$9V_1 = 0$$~~

~~$$V_1 = 0$$~~

$$V_2 = 0$$

$$4V_1 = -10$$

$$V_1 = \frac{-10}{4}$$


$$V_1' = -2.5 \text{ volts.}$$

$$I_1' = \frac{V_1'}{2} = \frac{-2.5}{2}$$

$$I_1' = -1.25 \text{ Amps}$$

step 2: 2 volt source acting alone

Q P code: 40093
3/6

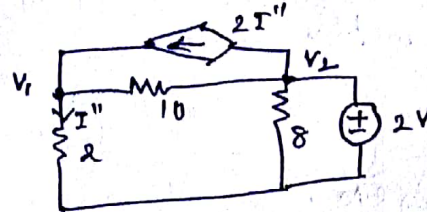

KCL at ①

$$-2I'' + I'' + \frac{V_1 - V_2}{10} = 0$$

$$V_2 = 2 \text{ volts.}$$

$$-2I'' + I'' + \frac{V_1 - 2}{10} = 0$$

$$-2I'' + I'' + \frac{2I'' - 2}{10} = 0$$

$$-20I'' + 2I'' - 2 = 0$$

$$-18I'' - 2 = 0$$

$$8I'' = -2$$

$$I'' = -2/8 = -0.25 \text{ Amps.}$$

step 3

current through 2 ohm resistor using superposition Th.

$$I = I' + I''$$

$$= -1.25 - 0.25$$


$$I = -1.50 \text{ Amps.}$$

b)

$$V_{th} = \frac{12}{5} = 2.4 \text{ volts.}$$

$$I_{sc} = 3 \text{ A}$$
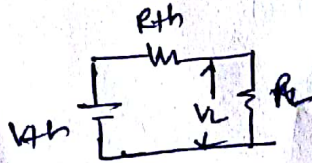
$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{8}{5} = 1.6 \Omega$$



$$V_L = \frac{1.6}{1.6 + 1.6} \times 2.4$$

$$= 1.2 \text{ volts.}$$

$$P_L = \frac{V_L^2}{R_L} = \frac{(1.2)^2}{1.6} = \frac{1.44}{1.6} = 0.9 \text{ watts.}$$

$$P_{max} = 0.9 \text{ watts.}$$

Que 3 a)

Reduced
incidence
matrix.

no. of nodes	no. of branches						
	1	2	3	4	5	6	7
A =	1	0	0	0	0	0	1
	2	-1	1	0	0	1	0
	3	0	-1	1	0	0	0
	4	0	0	-1	1	0	0
	5	0	0	0	-1	-1	-1

f. tie-set matrix

f. cut-set matrix

Q.P code: 40093 4/6

b) millman theorem.

$$R = \frac{1}{G} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{\frac{1}{4} + \frac{1}{2} + \frac{1}{1}} = \frac{1}{\frac{1+2+4}{4}} = \frac{4}{7}$$

$$V_m = \frac{\sum VG}{\sum G} = \frac{V_1 G_1 + V_2 G_2 + V_3 G_3}{G_1 + G_2 + G_3} = \frac{5 \times \frac{1}{4} + 0 \times \frac{1}{2} + 28 \times \frac{1}{1}}{\frac{1}{4} + \frac{1}{2} + \frac{1}{1}}$$

$$= \frac{5/4 + 28}{1/4 + 1/2 + 1} = \frac{5/4 + 28}{1.75} = \frac{5/4 + 28}{7/4} = \frac{5 + 112}{7} = \frac{117}{7}$$

$$\underline{V_2 = \frac{117}{7} \text{ volts.}}$$

$$= \frac{5 + 112}{7} = \frac{117}{7}$$

Q4 a)

$$i(t) = -10 e^{-0.5t} \text{ Amps. for } t > 0$$

$$V_c(t) = \frac{20}{3} (1 - e^{-0.5t}) \text{ volts. for } t > 0$$

b) $i_1(0^+) = 0.5 \text{ Amps.}$

$i_2(0^+) = 0.25 \text{ Amps.}$

$i_3(0^+) = 0 \text{ Amps.}$

Q5


9)

$$f(s) = 2s^4 + s^3 + 5s^2 + 3s + 4$$

Polynomial is Hurwitz.

b)
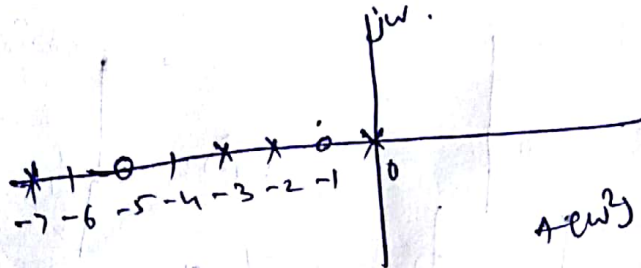
$$f(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$$



$$A(w^2) = s^4 - 35s^2 + 70 \Big|_{s=jw}$$

$$= w^4 + 35w^2 + 70$$

$A(w^2)$ is positive for all $w \geq 0$

$\therefore$ function is PRF

c)

4-parameter

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 8s^3 + 10s^2 + 8s + 3 & 8s^2 + 2s + 2 \\ 4s^3 + 4s^2 + 3s + 1 & 4s^2 + 1 \end{bmatrix}$$

$$Y = \begin{bmatrix} \frac{D}{B} & -\frac{\Delta T}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix} = \begin{bmatrix} \frac{4s^2 + 1}{8s^2 + 2s + 2} & \frac{-\Delta T}{8s^2 + 2s + 2} \\ \frac{-1}{8s^2 + 2s + 2} & \frac{8s^3 + 10s^2 + 8s + 3}{8s^2 + 2s + 2} \end{bmatrix}$$

$$\begin{aligned} \Delta T &= AD - BC \\ &= (8s^3 + 10s^2 + 8s + 3)(4s^2 + 1) - (8s^2 + 2s + 2)(4s^3 + 4s^2 + 3s + 1) \\ &= \end{aligned}$$


Q6. a)

$$Z(s) = \frac{s(s^2+4)}{(s^2+1)(s^2+9)}$$


Foster-I
Cauer-I

6/6

Foster-I

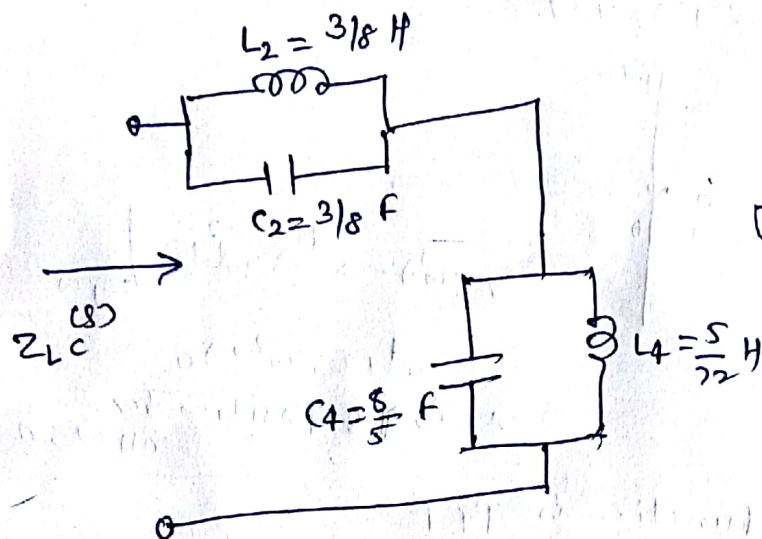

Cauer-I

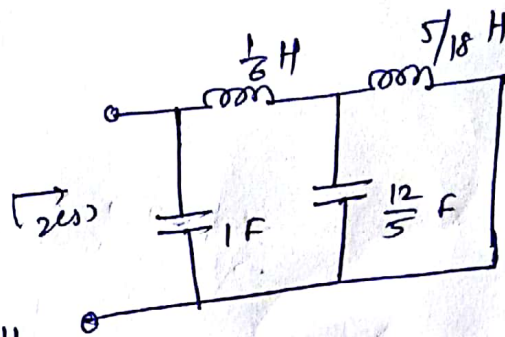

b)

$$\frac{V_2(s)}{V_1(s)} =$$

$$\frac{(s+1)(s+4)}{s^2+5s+6}$$

$$= \frac{(s+1)(s+4)}{(s+2)(s+3)}$$

