

- N.B. : (1) Question No. 1 is compulsory.
- (2) Solve any three questions from the remaining five
- (3) Figures to the right indicate full marks
- (4) Assume suitable data if necessary and mention the same in answer sheet.

(1)

Q.1	Attempt any 5 questions [20]
	<p>a) Compare ideal and practical opamp characteristics of ideal opamp</p> <ul style="list-style-type: none"> i) infinite voltage gain ii) infinite i/p impedance iii) zero o/p impedance iv) infinite BW v) No change in the characteristic features with changes in temperature vi) When equal voltages are applied at the 2 i/p terminals the o/p is zero. vii) Infinite slew rate <p>b) What is crossover distortion in power amplifier. How is it overcome?</p> <p>→ In class B power amplifier base current will not flow till i/p becomes equal to cut in voltage of transistor.</p> <p>→ Under this condition, sinusoidal i/p voltage will not produce sinusoidal o/p voltage.</p> <p>→ o/p voltage is distorted during cross over i.e. when one transistor is cutoff and other transistor is turned ON</p> <p>Remedy to overcome cross over distortion.</p> <p>→ Cross over distortion can be eliminated by making some changes in existing class B ckt.</p> <p>→ The change is that a small forward voltage is applied to each transistor to overcome its cut in voltage.</p> <p>→ Therefore the Q pt is shifted slightly above X axis and the operation is no more o class B but class AB operation.</p>

(2)

- c) Define differential and common mode gain and differential and common mode input impedance of differential amplifiers.

→ Differential gain : It is the gain with which the differential amplifier amplifies the differential S/g Vd. (Ideally Ac shud be ∞)

→ Common mode gain : It is the gain with which a practical diff amp amplifies the common mode S/g. (Ideally Ac shud be 0)

Differential mode input resistance is defined as the resistances between two input base terminals when a differential mode signal is applied.

Common mode input resistance is defined as the resistances between the common input terminals of differential amplifier operating in the common mode configuration.

- d) Draw the circuit diagram of Widlar current source and derive the relationship between output current and reference current.

→ In all current sources, I_o is approx equal to I_{REF} .

→ For basic 2 transistor current source if $I_o = 10\text{mA}$ and $V_{CC} = +5\text{V}$ and $V_{EE} = -5\text{V}$, then required value of R_1 is calculated as

$$R_1 = \frac{V_{CC} - V_{BE} + V_{EE}}{I_{REF}}$$


$$= \frac{5 - 0.7 + 5}{10\text{mA}} = 930\text{k}\Omega$$

→ A resistance of such large value is difficult to fabricate accurately on IC chip.

→ It requires large area as well. ∴ it is necessary to limit the value of resistor to a low $\text{k}\Omega$ range.

→ This requirement is satisfied by a special type of current source called as Widlar current source.

 → Fig. below shows ckt diagram of Widlar current source



- e) Draw high frequency hybrid pi equivalent of BJT and define the various components in the model.

Q

	<p>Components of a) Base-emitter b) Collector-emitter c) Base-collector hybrid pi eq.</p>	
	<p>f) Explain line regulation and load regulation of voltage regulator. Draw the line and load regulation characteristics of ideal and practical voltage regulator.</p> <p>→ The quality of IC regulator is often determined on the basis of three important parameters: line regulation, load regulation and ripple rejection.</p> <p>i) Line regulation : It is dependent on operating temperature of regulator. → Lesser line regulation implies better quality of an IC.</p> <p>→ It is defined as the change in the regulated o/p vltg due to change in unregulated i/p vltg over a specific range.</p> <p>ii) Load regulation : It describes change of o/p vltg over a specified load current. → For e.g: LM7815 has load regulation of 12mV for change of load current over a range from 5mA to 1.5A.</p>	
Q.2	<p>a) For the circuit shown in Fig. 2a find midband gain and corner frequencies.</p> <p>Fig.2a</p>	[10]
	<p>b) Determine unity gain bandwidth of N channel MOSFET with parameters $K_n = 0.25 \text{ mA/V}^2$, $V_{TN} = 1\text{V}$, $\lambda = 0$, $C_{gd} = 0.04 \text{ pF}$, $C_{gs} = 0.2 \text{ pF}$, $V_{GS} = 3\text{V}$. If a $10 \text{ k}\Omega$ load is connected to the output between drain and source determine the Miller capacitance and cut-off frequency.</p>	[10]
Q.3	<p>a) Draw circuit diagram of MOSFET based differential amplifier and derive the expression for differential gain, common mode gain and CMRR.</p> <p>b) For the circuit shown in Fig. 3b, find overall mid band voltage gain and</p>	[10]

(4)

capacitors C_{C1} and C_{C2} such that the 3 dB frequencies associated with each stage are equal. Assume BJT to have parameters $V_{BE(on)} = 0.7$ V, $\beta = 200$ and $V_A = \infty$

 


Fig. 3b

STEP 1: DC ANALYSIS

$$V_{TH} = V_{B1} = \frac{3k}{3k+55k} \times 5$$

$$V_{B1} = 1.802 \text{ V}$$

$$V_{B1} - V_{BE} - I_{E1}R_{E1} = 0$$

$$I_{E1} = \frac{V_{B1} - V_{BE}}{R_{E1}} = \frac{1.802 - 0.7}{1k}$$


$$I_{C1} \approx I_{E1} = 1.102 \text{ mA}$$

$$I_{C2} = I_{C1} = 1.102 \text{ mA}$$

$$\gamma\pi = \frac{\beta V_T}{I_C} = \frac{200 \times 26 \text{ mV}}{1.102 \text{ mA}} = 4.718 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{1.102}{26 \text{ mV}} = 42.38 \text{ mA/V}$$

STEP 2: HYBRID PI EQUIVALENT CKT.

 

STEP 3: ANALYSIS OF STAGE 2:

Effective load resistance $= R_{C2} = 3.5k$.

$$V_O = -g_m V_{\pi} \times R_{C2}$$

$$A_{V2} = \frac{-g_m \gamma\pi R_{C2}}{\gamma\pi + (\beta + 1) R_{E2}}$$

$$= \frac{42.38 \times 10^{-3} \times 4.718 \text{ k} \times 3.5 \text{ k}}{4.718 \text{ k} + 201 \times 1 \text{ k}}$$



ANALYSIS OF STAGE 1:

Effective load resistance on stage 1.

$$R_L = R_{C_1} \parallel R_{i_2} = 3.5k \parallel R_{i_2}$$

$$\begin{aligned} A_{V_1} &= \frac{-g_m r_\pi i_{f_1} R_L}{i_{f_1} (r_\pi + (\beta+1) R_E)} \\ &= \frac{-42.8m \times 4718k \times 2.932k}{4718k + 201 \times 1k} \\ &= 2.878 \end{aligned}$$

$$\begin{aligned} A_V &= A_{V_1} \times A_{V_2} \\ &= 2.878 \times 3.402 \\ &= 9.790 \end{aligned}$$

STEP 4: 3 dB frequencies associated with C_{C_1} & C_{C_2}

By time constant technique.

$$\tau_{S_1} = C_{C_1} \times (R_B \parallel r_i)$$

$$\tau_{S_1} = C_{C_1} \times (R_B \parallel (r_\pi + (\beta+1) R_E))$$

$$f_{L_1} = \frac{1}{2\pi C_{C_1} \times (R_B \parallel (r_\pi + (\beta+1) R_E))} \quad (1)$$

By time constant technique.

$$\tau_{S_2} = C_{C_2} \times [R_{C_1} + (R_B \parallel (r_\pi + (\beta+1) R_E))]$$

$$f_{L_2} = \frac{1}{2\pi C_{C_2} \times [R_{C_1} + (R_B \parallel (r_\pi + (\beta+1) R_E))]} \quad (2)$$

$$f_{L_1} = f_{L_2}$$

$$\frac{1}{2\pi C_{C_1} \times [R_B \parallel (r_\pi + (\beta+1) R_E)]} = \frac{1}{2\pi C_{C_2} \times [R_{C_1} + (R_B \parallel (r_\pi + (\beta+1) R_E))]}$$

$$C_{C_1} \times 18.082k = C_{C_2} (3.5k + 18.082k)$$

$$\frac{C_{C_1}}{C_{C_2}} = 1.193$$

Let $C_{C_1} = 10\text{ }\mu\text{F}$

$$C_{C_2} = 11.93\text{ }\mu\text{F}$$

- Q.4 a) Draw and explain current mirror circuit using MOSFET. For the circuit shown in Fig. 4a determine the value of I_{ref} and I_O . [10]

(6)

 


Fig.4a

- b) What are the ideal characteristics of opamp and also explain the effect of high frequency on OPAMP gain and phase. [5]

CHARACTERISTICS OF IDEAL OPAMP

Characteristics of ideal opamp


- i) infinite voltage gain
- ii) infinite input impedance
- iii) zero output impedance
- iv) infinite BW
- v) No change in the characteristic features with changes in temperature
- vi) When equal voltages are applied at the 2 input terminals the opamp is zero.
- vii) Infinite slew rate.
→ The gain of the opamp rolls off after a certain frequency is reached.
→ Obviously there must be a capacitive component in the equivalent circuit of the opamp since its reactance decreases as freq increases
→ Two major sources responsible for capacitive effects:
i) Physical characteristics of semiconductor devices
→ Opamps are made of BJT's & FET's which contain junction capacitors.
→ These junction capacitors are very small (pF range) and act as AC at low freq.
→ But they take finite values at higher frequencies. As freq increases, reactance of these capacitors decrease
ii) Capacitive effect due to internal construction of opamp.
→ In opamps a number of transistors as well as resistors and sometimes a capacitor are integrated on the same material called the substrate.
→ In fact the substrate acts as an insulator & helps to separate these components.

- c) Draw the circuit of V_{BE} multiplier biased class AB amplifier and explain [5]

(X)


the working and advantages of V_{BE} multiplier biased class AB amplifier.

 CLASS AB BIASING USING V_{BE} MULTIPLIER.
The ckt diagram is as shown below




- Q.5 a) Draw the circuit diagram of transformer coupled class A power amplifier. Also draw ac and dc loadlines for the same. Derive the expression for its power conversion efficiency. [10]

Circuit diagram

 

DC and AC Loadline

 

$$\therefore \eta_{max} = \frac{1}{2} = 50\%.$$


- b) Explain the working of basic differentiator with the help of input and output waveforms. Also derive the expression for the output voltage. What are the [10]

8


limitations of basic differentiator and how to overcome these limitations.

→ Differentiator as the name suggests performs the mathematical operation of differentiation i.e o/p v/f is the derivative of the i/p v/f. (rate of change of i/p v/tg).

 → Differentiator ckt can be constructed from a basic inverting amplifier if the i/p resistor R_1 is replaced by a capacitor C_1 as shown below



 
→ Thus the o/p v/tg V_o is equal to $R_F C_1$ times the negative instantaneous rate of change of i/p v/tg V_{in} with time.
Waveforms.



Q.6 Short notes on: (Attempt any four)

[20]

 
- a) Transistorised series regulator
- b) Power MOSFET




- c) Class AB power amplifier
- d) Active filters

Q

FIRST ORDER LOW PASS

 

FIRST ORDER HIGH PASS

 

→ Input resistor R_i & feedback resistor R_F are used to determine gain of filter in passband

e) Multistage amplifiers

MULTISTAGE AMPLIFIERS

- For many amplification purposes, a single transistor does not provide enough gain, so multiple ckt's or stages of amplification are needed.
- When an amplifier contains multiple stages the total gain is product of individual stage gains

$$G = G_1 \times G_2 \times G_3 \times \dots$$

$$\rightarrow \text{In dB } G(\text{dB}) = G_1(\text{dB}) + G_2(\text{dB}) + G_3(\text{dB}) + \dots$$

TYPES OF 2 STAGE CASCADeD AMPLIFIERS.

1. CE-CE cascade
2. CE - CC cascade
3. CC - CE cascade
4. CC - CC cascade (Darlington).
5. CE - CB cascade (Cascode).
6. CB - CC cascade
7. CC - CB cascade (emitter coupled pair)

Explain any one of the above.

