

Q. No.

EDC-1 Solution

Marks

Ques 1 (a)

Apply KVL to circuit

$$10 - V_D - I_D 1K = 0 \quad \text{--- (1)}$$

for I_{Dmax} let $V_D = 0$


$$\therefore 10 - 0 - I_{Dmax} 1K = 0$$

$$\therefore I_{Dmax} = \frac{10}{1K} = 10mA$$

for V_{Dmax} , let $I_D = 0$

$$\therefore 10 - V_{Dmax} - 0 = 0$$

$$\therefore V_{Dmax} = 10V$$

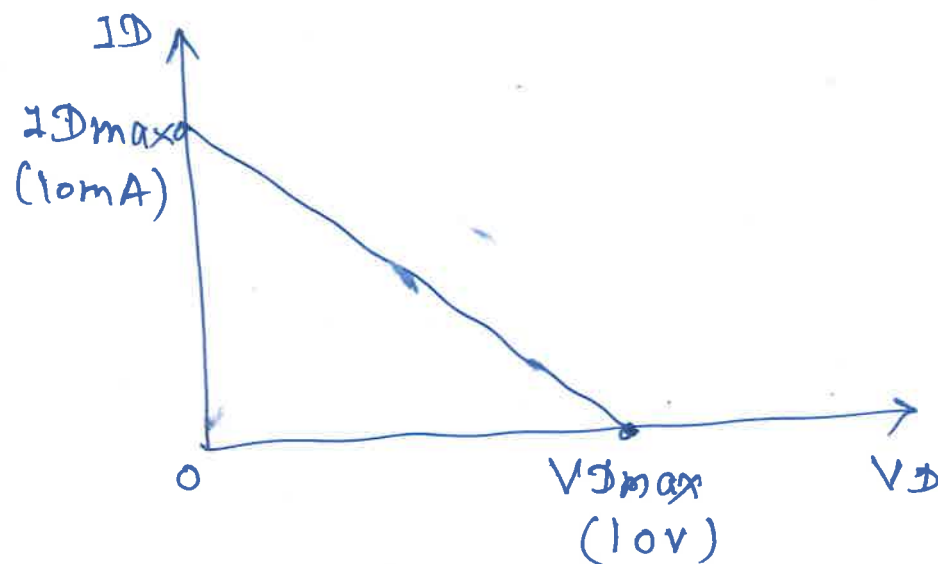

Q. No.

Marks

(Que 2 b)

$$V_{th} = \frac{R_2 V_{CC}}{R_1 + R_2} = 3 \text{ V}$$

$$R_{th} = R_1 \parallel R_2 = 12.95 \text{ k}\Omega$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E} = \frac{3 - 0.7}{12.95 \text{ k} + (101 \times 1.2 \text{ k})}$$

$$= 17.15 \mu\text{A}$$

$$\therefore I_{CQ} = \beta I_{BQ} = 1.71 \text{ mA}$$

$$r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{26 \text{ mV} \times 100}{1.71 \text{ mA}} = 1.516 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = 85.96 \text{ mA/V}$$

$$\text{let } r_o = \infty$$

$$R_i = r_{\pi} = 1.516 \text{ k}\Omega$$

$$R_i' = R_{th} \parallel R_i = 1.35 \text{ k}\Omega$$

$$A_v = \frac{-g_m V_{th} R_C}{V_{th}} = -g_m R_C = -257.20$$

$$R_o = \infty$$

$$R_o' = R_C = 3.9 \text{ k}\Omega$$

$$A_v \text{ with } R_L, \quad A_v = -g_m (R_C \parallel R_L) = -185$$

$$A_i = -\beta = -100$$

Q. No.

Que 3 a)

$$K = \frac{I_D(ON)}{[V_{GS(ON)} - V_{GS(th)}]^2}$$

$$= 0.55 \text{ mA/V}^2$$

$$V_{GS} = 9.7 - 0.75 I_{DQ}$$

$$I_{DQ} = K [V_{GS} - V_{GS(th)}]^2$$

Solving

$$I_{DQ} = 4.96 \text{ mA}$$

V_{DSQ}

$$V_{DSQ} = V_{DD} - I_D (R_D + R_S)$$

$$= 24 - 4.96 \text{ mA} (2.2 \text{ k} + 0.75 \text{ k})$$

$$\underline{V_{DSQ} = 9.36 \text{ V}}$$

Que 4 b)

$$I_B = 32.11 \mu\text{A}$$

$$I_C = \beta I_B = 3.21 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = 10.33 \text{ V}$$

$$V_C = 13.58 \text{ V}$$

$$V_E = 3.24 \text{ V}$$

Q. No.

(Que 6a)

From DC Analysis.

$$V_{GSQ} = V_G - I_D R_S$$

$$V_{GSQ} = 5 - 1.2 I_{DQ}$$

$$I_{DQ} = K (V_{GSQ} - V_T)^2$$

Solving

$$I_{DQ} = 1.11 \text{ mA}$$

$$\therefore V_{GSQ} = 4.66 \text{ V}$$

$$\therefore g_m = 2K (V_{GSQ} - V_T)$$

$$= 1.33 \text{ mA/V}$$

AC Analysis:

$$\underline{R_i = R_1 \parallel R_2 = 8 \text{ M}\Omega}$$

$$A_v = -g_m (r_d \parallel R_D)$$

$$\underline{A_v = -4.05}$$

$$R_o = r_d \parallel R_D$$

$$\underline{R_o = 3.04 \text{ k}\Omega}$$