

**Subject: Signal Conditioning Circuit Design  
SE (Instrumentation) (CBCGS)**


- N. B. 1) Question No. 1 is **compulsory (Any Four)**.  
 2) Answer any **3** questions from the remaining **5** questions.  
 3) Assume suitable data wherever necessary.

- Q1 (a) Write a short note on zero crossing detector. **20**  
 (b) Describe the term loading effect with suitable example.  
 (c) The resistors in a bridge are given by  $R_1=R_2=R_3=120\ \Omega$  and  $R_4 = 121\ \Omega$ . If the supply voltage is 10V. Find the offset voltage.

$$\Delta V = V \frac{R_3 R_2 - R_1 R_4}{(R_1 + R_3)(R_2 + R_4)}$$

$$\Delta V = -20.7\text{mV}$$

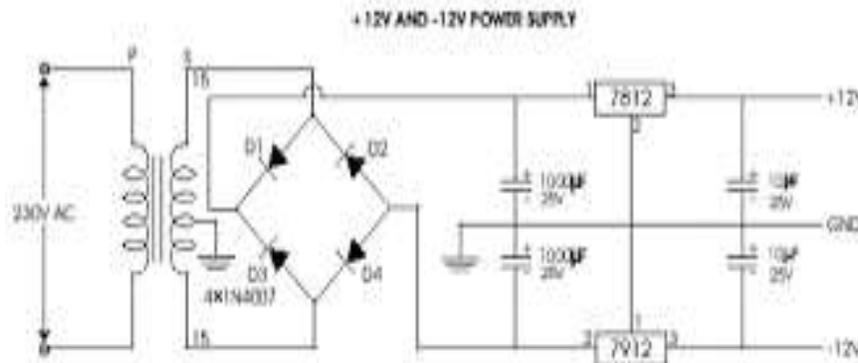
- (d) Draw and explain Sample and Hold circuit.  
 (e) Design a  $\pm 12\text{V}$  power supply using IC 78xx.



- Q2 (a) Define multivibrator? Explain astable multivibrator using IC 555 and also **20**  
 design astable multivibrator for 50% duty cycle.  
 (b) Draw and explain circuit for ideal integrator with waveforms. Discuss the

problems associated with ideal integrator and draw the circuit diagram for practical integrator.

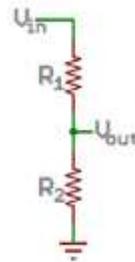- Q3 (a) A thermistor is to monitor room temperature. It has a resistance of  $3.5\text{ K}\Omega$  at  $20^\circ\text{C}$  with a slope of  $-10\%/^\circ\text{C}$ . The dissipation constant is  $P_D=5\text{mW}/^\circ\text{C}$ . It is proposed to use the thermistor in the divider as shown below to provide a voltage of  $5.0\text{V}$  at  $20^\circ\text{C}$ . Evaluate the effect of self-heating. ( $R_2$ = Thermistor;  $R_1=3.5\text{K}\Omega$ ) **20**



At  $20^\circ\text{C}$ , the thermistor resistor will be  $3.5\text{K}\Omega$ , and the divider voltage will be

$$V_D = \frac{3.5\text{K}\Omega}{3.5\text{K}\Omega + 3.5\text{K}\Omega} 10 = 5\text{V}$$

The power dissipation in the thermistor

$$P = \frac{V^2}{R_{TH}} = 7.1\text{mW}$$

Temperature rise of the thermistor


$$\Delta T = \frac{P}{P_D} = \frac{7.1\text{mW}}{5\text{mW}/^\circ\text{C}} = 1.42^\circ\text{C}$$

The Thermistor Resistance is given by

$$R_{TH} = 3.5\text{K}\Omega - 1.42^\circ\text{C}(0.1/^\circ\text{C})(3.5\text{K}\Omega) = 3.0\text{K}\Omega$$

$$V_D = 4.6\text{V}$$

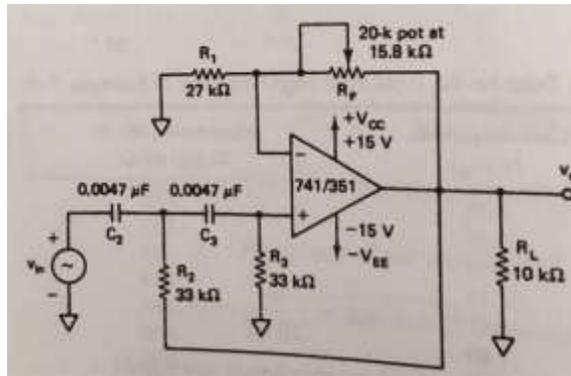- (b) Draw and explain the principle and construction of metal strain gauges. What is the signal conditioning associated with it.
- Q4 (a) Explain successive approximation analog to digital converter. Find ADC output **20** for a 4-bit converter to a  $2.187\text{V}$  input, if the reference is  $5\text{V}$ .
- Set  $b_1=1 \implies V_F=5(2^{-1})=2.5\text{V}$   
 $b_2=1 \implies V_F=5(2^{-2})=1.25\text{V}$   
 $b_3=1 \implies V_F=5(2^{-3})=.625\text{V}$   
 $b_4=1 \implies V_F=5(2^{-4})=.3125\text{V}$
- $b_2b_3b_4=1.25+.625+.3125=2.187$
- (b) Design a second order high pass filter for cutoff frequency equal to  $1.5\text{ KHz}$ .



$$f_L = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

Assume  $C_2 = C_3 = C = 0.0047 \mu\text{F}$ , and  $R_2 = R_3 = R$ ;

$$f_l = \frac{1}{2\pi RC}$$

$$R = 22.5 \text{K}\Omega$$

$$\text{Gain} = 1 + \frac{R_F}{R_1}$$

Assume  $R_1 = 27 \text{K}\Omega$ ;  $R_F = 15.8 \text{K}\Omega$


- Q5 (a) A potentiometric displacement sensor is to be used to measure work-piece motion from 0 to 10 cm. The resistance changes linearly over this range from 0 to  $1 \text{K}\Omega$ . 20

Develop signal conditioning to provide a linear, 0- to 10-V output.

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

Negative sign can be removed by using a constant negative voltage (Zener diode)
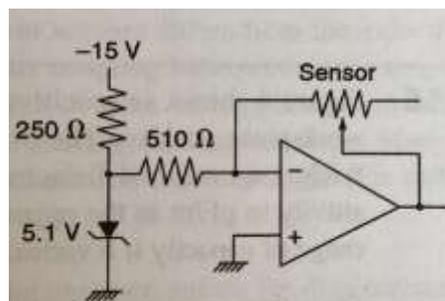
$$10 = -\frac{1000}{R_1} (-5.1) \\ = 510 \Omega$$



- (b) Explain the absolute value circuit with labelled circuit diagram and its

waveform.

- |           |   |           |
|-----------|---|-----------|
| <b>Q6</b> | (a) Draw and explain the principle and construction of RTD. What is the signal conditioning associated with it. | <b>10</b> |
|           | (b) Phase Locked loop   | <b>5</b>  |
|           | (c) SMPS  | <b>5</b>  |