

Questions should be —
WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.
SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,
so as to avoid mistakes in the printed question papers.

Duration 3:00 Hours.

Total Marks assigned to the paper ... 80 marks

Q. No.

Solution

Marks

N.B. ① Design approach other than mentioned
 can also be considered as long as
 component values are valid.


② Assumptions are accepted.

③ Appropriate weightage can be given if
 any extra/additional information written.

Q-1-A. Both the breakdown mechanisms should be
 explained in detail.

Any other additional point to be added

Q-1-B

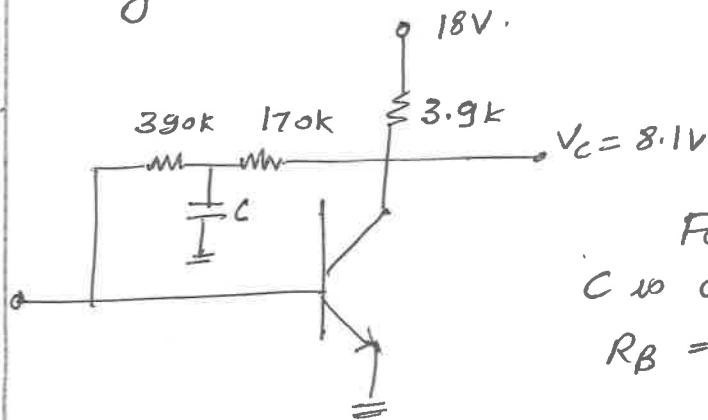

For dc analysis,
 C is open circuit.

$$R_B = 390k + 170k = 560k$$

$$I_{BQ} = \frac{V_C - V_B}{R_B}$$

$$= \frac{8.1 - 0.6}{560k} = 13.39 \mu A$$

$$I_{BQ} + I_{CQ} = \frac{V_{CC} - V_C}{R_C}$$

$$= 2.53 mA$$

$$\therefore I_{CQ} = 2.516 mA$$

$$\beta = \frac{I_{CQ}}{I_{BQ}} = 187.2$$

$$V_{CEQ} = V_{CC} - V_{CQ}$$

$$= 8.1 V$$

④

①

Q. No.
Q-1-C.

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right]$$


$$= \frac{-2I_{DSS}}{V_P} \left[1 - \frac{V_{GS}}{V_P} \right] = \frac{-2 \times 10 \text{ mA}}{-5} \left[1 - \frac{(-2.5)}{(-5)} \right]$$

$$= 2.5 \text{ mA}$$

Marks

Q-1-D.

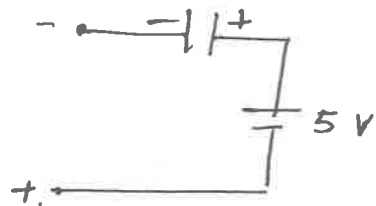In -ve h/f cycle, D is forward biased $V_{in} = 20V$




$$-V_{in} + V_C - 5 = 0$$

$$-20 + V_C - 5 = 0$$

$$V_C = 25V$$

$$\therefore V_o = 5V$$

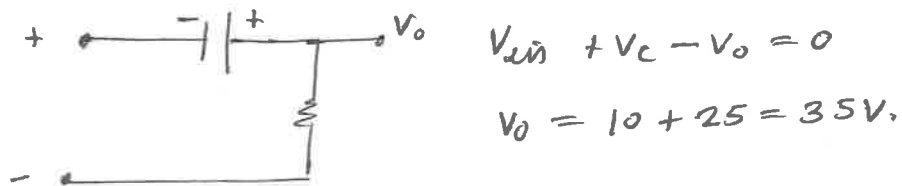
In +ve h/f cycle, D is reverse biased. $V_{in} = 10V$.



$$V_{in} + V_C - V_o = 0$$

$$V_o = 10 + 25 = 35V$$

Q-1

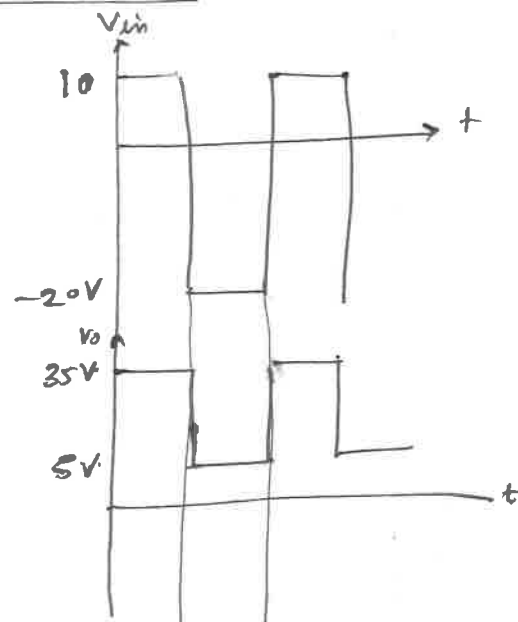

Q-2-A.

Page No.....

Q. No.

Single stage CS amp^t.

Marks

Step ① - For zero temperature drift

$$0.007 I_{DQ} = 0.0022 g_m$$

$$V_{GSQ} = - (|V_P| - 0.63) \\ = -1.87V.$$

$$\textcircled{2} \quad I_{DQ} = I_{DSS} \left[1 - \frac{V_{GSQ}}{V_P} \right]^2 \\ = 0.44 \text{ mA}$$

③ Select $R_G = 1 \text{ M}\Omega / 2 \text{ M}\Omega$

④ $V_{GSQ} = -I_{DQ} \cdot R_S$ for self bias confⁿ.

$$R_S = 4.21 \text{ k}\Omega$$

$$\textcircled{5} \quad A_v = -g_m (R_D || r_d)$$

R_S bypassed
 $r_d \approx 50 \text{ k}\Omega$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right] \\ = 1.26 \text{ mA/V.}$$

$$R_D = 3.389 \text{ k}\Omega$$

$$I_{DQ} = \frac{V_{GSQ}}{R_S} = \frac{1.87}{4.3} = 0.4348 \text{ mA.}$$

⑥ Check $I_{DQ} \cdot R_D$ is less than $V_{O(peak)}$.

\therefore increasing R_D select $R_D = 10 \text{ k}\Omega / 1/4 \text{ W.}$

Select
JFET BFW 11

$$V_{DS(max)} = 30$$

$$P_{d(max)} = 300 \text{ mW.}$$

$$I_{DSS} = 7 \text{ mA}$$

$$g_{m0} = 5000 \mu\text{S}$$

$$V_P = -2.5 \text{ V}$$

$$r_d = 50 \text{ k}\Omega$$

$$V_{O(peak)} = 3 \text{ V}$$

$$V_{O(rms)} = \frac{3}{\sqrt{2}}$$

$$= \frac{3}{\sqrt{2}} = 2.12 \text{ V.}$$

Q. No.

7

$$V_{DD} = V_{R_D} + V_{DS_Q} + V_{R_S}$$

$$\text{where } V_{R_D} = I_{D_Q} \cdot R_D = 7.848 \text{ V}$$

$$\therefore V_{DD} = 14.156 \text{ V} \approx 15 \text{ V}$$

8

$$C_S = \frac{1}{2\pi f_L \cdot X_{C_S}}$$

$$X_{C_S} = 0.1 R_S$$

$$= 430 \Omega$$


$$= 33 \mu\text{F} / 25 \text{ V}$$

$$C_{C_{in}} = C_{C_o} = \frac{1}{2\pi f_L \cdot R_i} \quad R_i = R_G = 1 \text{ M}\Omega$$

$$\therefore = 0.0106 \mu\text{F} = 0.02 \mu\text{F}$$

Ckt diagram -

09

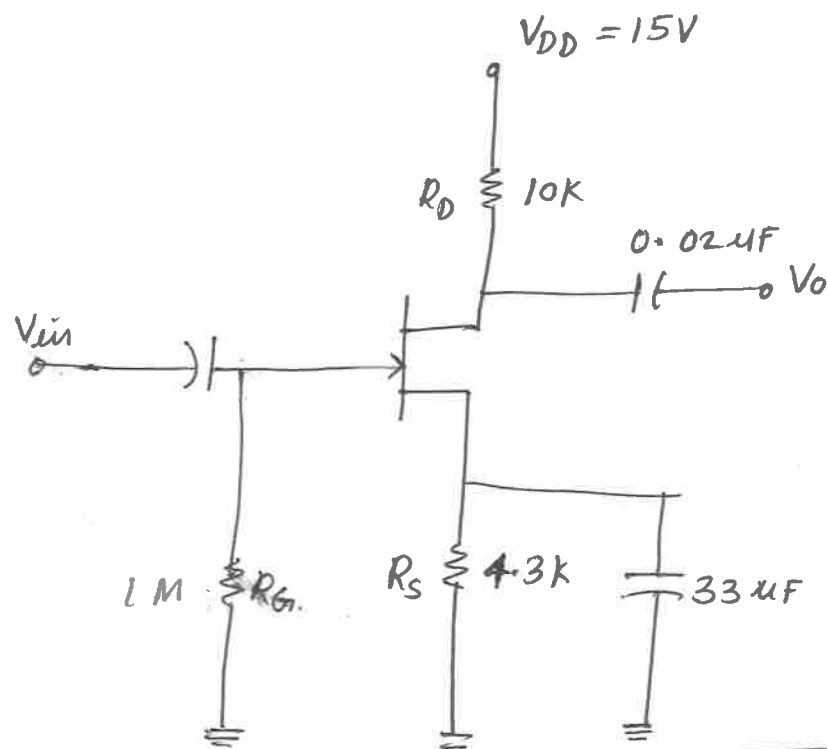

Evenly distribute marks throughout the problem.

Q. No. Q-2-B

$$V_{th} = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$= 20 \times \frac{56}{220 + 56} = 4.05V$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{220K \times 56K}{220 + 56K} = 44.63K$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta)R_E} = \frac{4.05 - 0.7}{44.63K + (101) \times 2.2K}$$

$$= 0.01255 \text{ mA}$$


$$I_{CQ} = \beta \cdot I_{BQ} = 1.255 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E) = 20 - 1.255 \text{ mA}(6.8K + 2.2K)$$

$$= 20 - 11.25 = 8.75 \text{ V}$$

ac equivalent :-
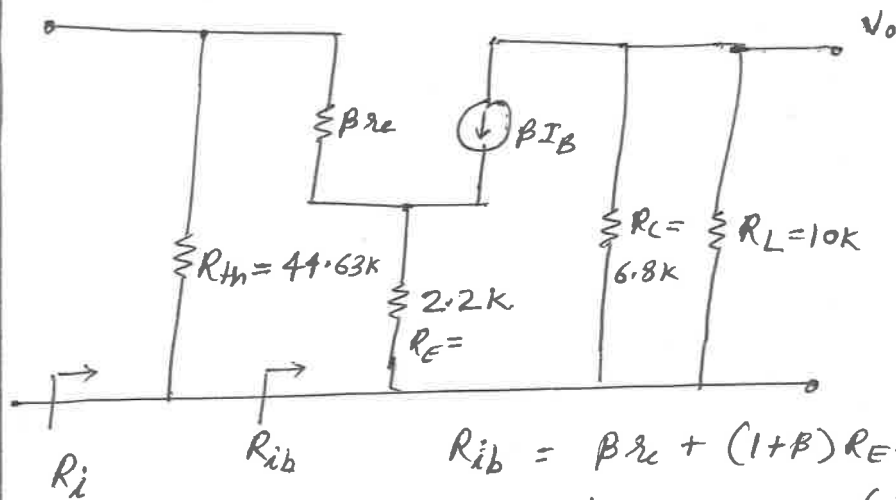
$$r_e = \frac{26 \text{ mV}}{I_{CQ}} = \frac{26 \text{ mV}}{1.255 \text{ mA}} = 20.71 \Omega$$



$$R_{ib} = \beta r_e + (1+\beta)R_E$$

$$= 100 \times 20.71 + (101 \times 2.2K) = 224.27K$$

$$R_i = R_{th} \parallel R_{ib}$$

$$= 44.63K \parallel 224.27K$$

$$= 37.17K$$

$V_{CC} = 20V$


$R_C = 6.8K$

Page No.

Open in dc.

Marks

$\beta = 100$

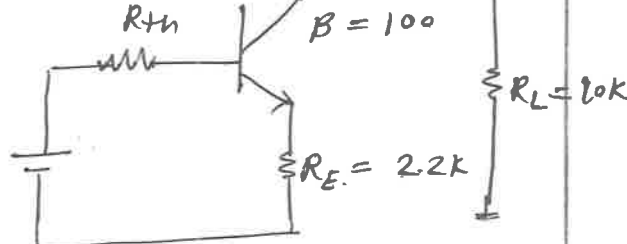

05

Q. No.

Marks

$$|A_v| = \frac{(R_c || R_L)}{R_E}$$

$$= \frac{6.8 \text{ K} || 10 \text{ K}}{2.2 \text{ K}} = 2.2427 \text{ K}$$

$$R_o = (R_c || R_L) = (6.8 \text{ K} || 10 \text{ K}) = \frac{6.8 \text{ K} \times 10 \text{ K}}{6.8 \text{ K} + 10 \text{ K}}$$

$$= \frac{68 \text{ K}}{16.8 \text{ K}} = \underline{\underline{4.04 \text{ K}}}$$

Q-3-A.

EMOSFET - DMOSFET symbol - ①

Constructional difference - ①

Drain characteristics - sketches, explanation - ④

Transfer characteristics - sketches, explanation - ④

Q-3-B.

① Self bias circuit -

$$V_{GSQ} = -I_{DQ} \cdot R_S$$

② V_{GSQ} can be found out analytically or graphically.

$$V_{GSQ} = -0.924 \text{ V} \quad I_{DQ} = +3.85 \text{ mA}$$


$$\textcircled{3} \quad V_{DSQ} = V_{DD} - I_D (R_D + R_S)$$

$$= \underline{\underline{1.45 \text{ V}}}$$

Q. No.

Q-4-A

Marks

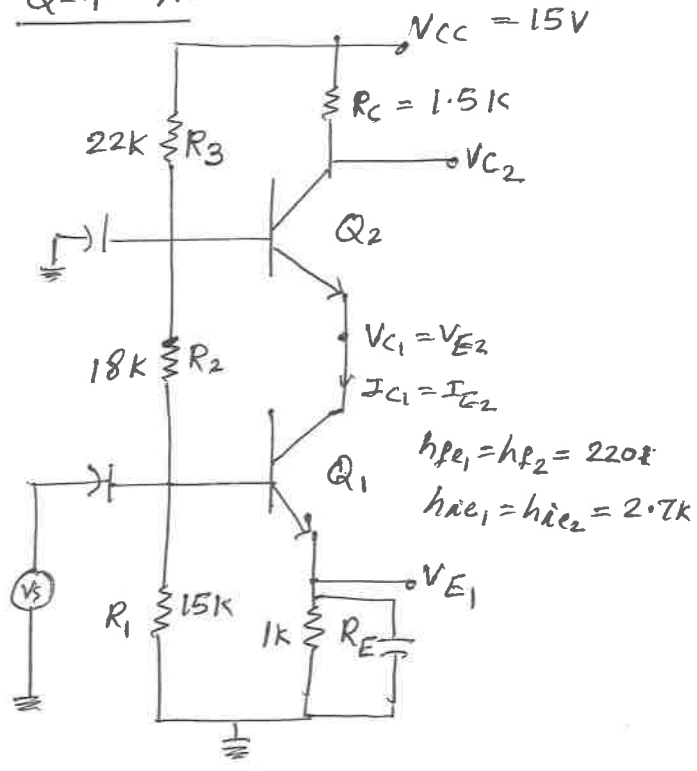

$$I_{C1} = I_{C2} = I_{E1} = I_{E2}$$

$$V_{B1} = R_1 \cdot \frac{V_{CC}}{R_1 + R_2 + R_3}$$

$$= \frac{15V \times 15k}{15k + 18k + 22k}$$

$$= 4.09V$$

$$I_{E1} = \frac{V_{E1}}{R_E} = \frac{3.39}{1k}$$

$$= 3.39mA$$

$$V_{E1} = V_{B1} - V_{BE1}$$

$$= 4.09 - 0.7V = 3.39V$$

$$r_e = \frac{26mV}{I_E}$$

$$= \frac{26mV}{3.39mA} = 7.66\Omega$$

$$V_{B2} = V_{CC} \cdot \frac{R_1 + R_2}{R_1 + R_2 + R_3}$$

$$= 9V$$

$$V_{E2} = V_{B2} - V_{BE2}$$

$$= 9 - 0.7 = 8.3V$$

$$V_{C2} = V_{CC} - I_{C2} \cdot R_C$$

$$= 15 - (3.39 \times 1.5k)$$

$$= 9.915V$$

$$V_{CE1} = V_{C1} - V_{E1}$$


$$= 8.3 - 3.39 = 4.91V$$

$$V_{CE2} = V_{C2} - V_{E2}$$

$$= 9.915 - 8.3 = 1.615V$$

Q. No.

Marks

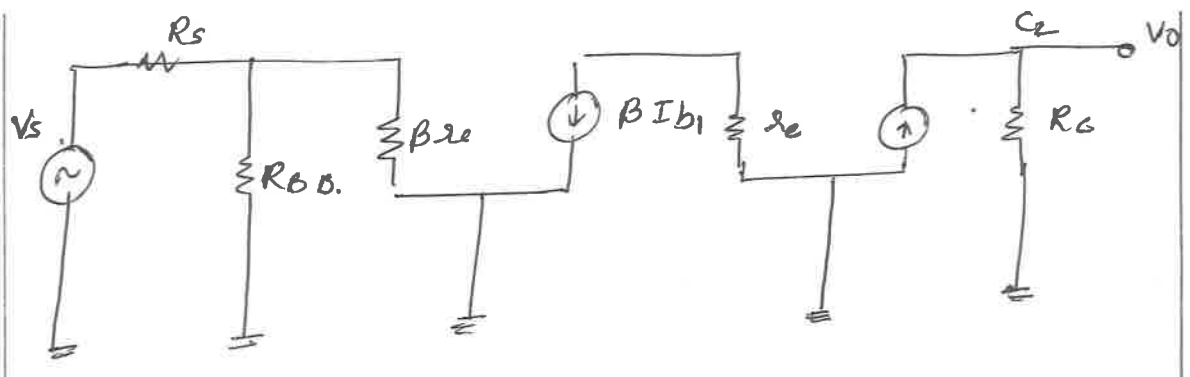

$$\begin{aligned}
 Z_i &= R_{BB} \parallel \beta \cdot r_e \\
 &= 8.18k \parallel (220 \times 7.66) \\
 &= 8.18k \parallel 1.68k \\
 &= 1k.
 \end{aligned}$$

$$\begin{aligned}
 R_{BB} &= R_1 \parallel R_2 \\
 &= \frac{R_1 R_2}{R_1 + R_2} = \frac{15k \times 18k}{15k + 18k} \\
 &= 8.18k.
 \end{aligned}$$

$$r_e = \frac{26mV}{I_{CQ}} = \frac{26mV}{I_{CQ}}$$

$$Z_o = R_c = 1.5k.$$

$$A_{v_2} = \frac{R_c}{r_e} = \frac{1.5k}{7.66\Omega} = 195.82$$

$$A_{v_1} = \underline{\underline{-1}}$$

$$A_{v(t)} = -\frac{R_c}{r_e} = \text{trans} - 195.82$$

Q-4-B

CG amplifier.

ckt diagram - ①

ac equivalent circuit - ①


$$Z_i - \textcircled{3} \quad A_v - \textcircled{3}$$

$$Z_o - \textcircled{2}$$

Q. No.

Q-5-A.

Marks

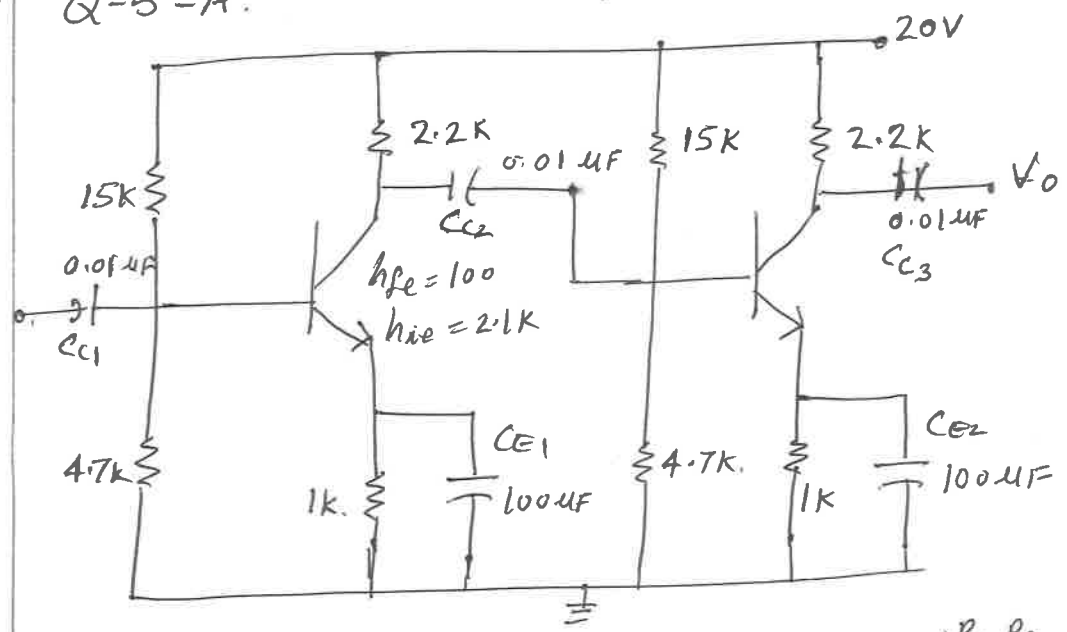


$$f_{LCc1} = \frac{1}{2\pi X_{Cc1} C_{C1}}$$

$$R_{th1} = R_{th2} = \frac{R_1 R_2}{R_1 + R_2} =$$


a.c. equivalent :-
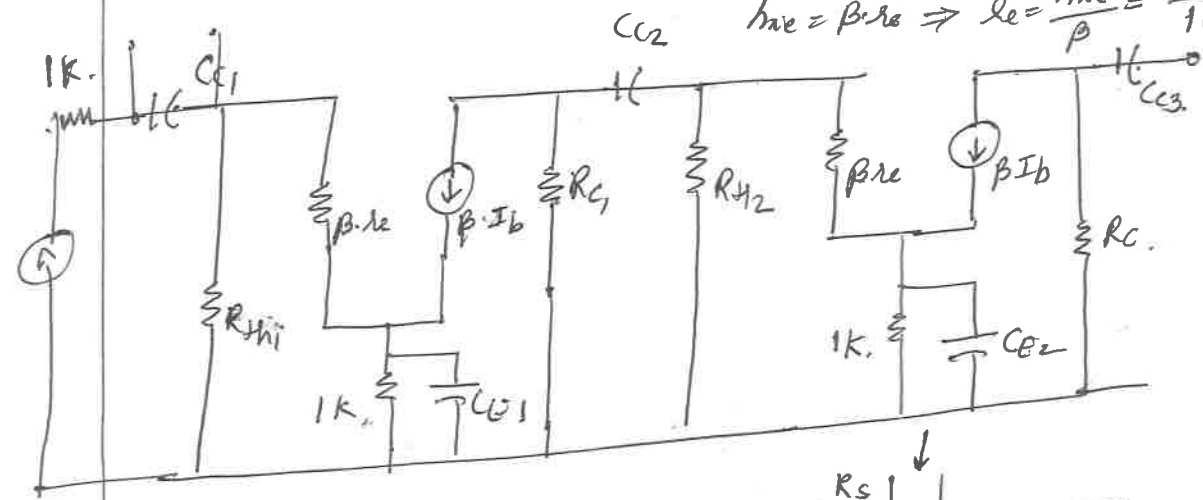
$$h_{ie} = \beta r_e \Rightarrow r_e = \frac{h_{ie}}{\beta} = \frac{2.1K}{100} = 21 \Omega$$



$$f_{LCc1} = \frac{1}{2\pi X_{Cc1} C_{C1}}$$

$$X_{Cc1} =$$

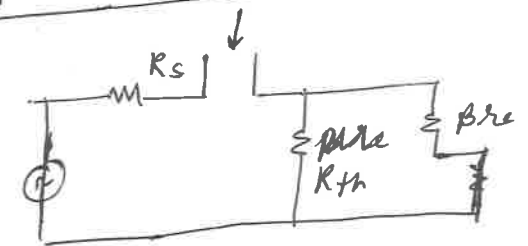


$$X_{Cc1} = (R_{th} \parallel \beta r_e) + R_s$$

=

Q. No.


Marks
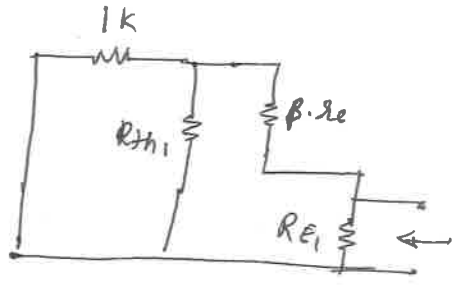
$$f_{LCE1} = \frac{1}{2\pi X_{CE1} \cdot C_{C1}}$$




$$X_{CE1} = \left(\frac{(1k \parallel R_{th1}) + \beta \cdot r_e}{1 + \beta} \right) \parallel R_{E1}$$
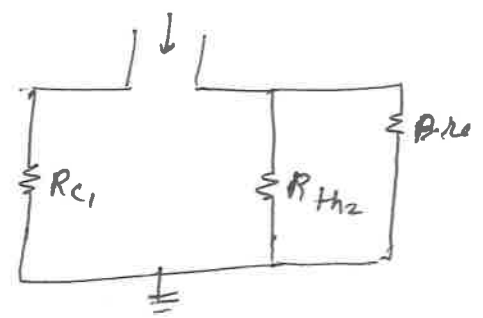
$$f_{LC2} = \frac{1}{2\pi R_{CE2} \cdot C_{C2}}$$



$$X_{CE2} = (R_{th2} \parallel \beta \cdot r_e) + R_{C1}$$
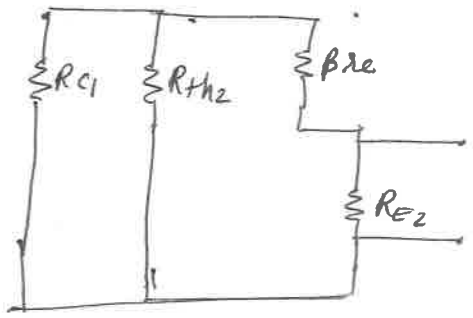
$$R_{CE2} = \frac{1}{2\pi X_{CE2} \cdot C_{C2}}$$



$$X_{CE2} = \left[\frac{(R_{C1} \parallel R_{th2}) + \beta r_e}{1 + \beta} \right] \parallel R_{E2}$$

$$R_{CE3} = \frac{1}{2\pi X_{CE3} \cdot C_{C3}}$$

$$X_{CE3} = R_C$$

Lower cut-off frequency is the highest frequency amongst five calculated.

Q. No.

Q-6 -

Marks

A BJT as a switch -

2 different modes of operation & equivalent circuits to be written.

B Reason for considering voltage divider biasing most useful - (1), ckt. diagrams - (1)

Derivation of S - (2)

formula for $S = (1)$

C. Zero temperature drift -

D. Clipper.

Series clipper one type to be explained
shunt clipper, one type to be explained.
Concept of biased clipper to be explained.
waveforms are essential.

E. Basic diagrams of CE amp^r, CS amp^r - (2)
High frequency model. - (3)