

Solution

Q.P. code: 40504

①

①

Page No.....

Q. No.

Marks

1. (a) Comparison between E-MOSFET and D-MOSFET: working, characteristics, symbol, biasing network, definition (Any five points) (5M)


(b) High frequency model of BJT (2M)  
Explanation on each component (3M)

(c) n-channel FET: Diagram (1M)  
working (3M) characteristics (1M)

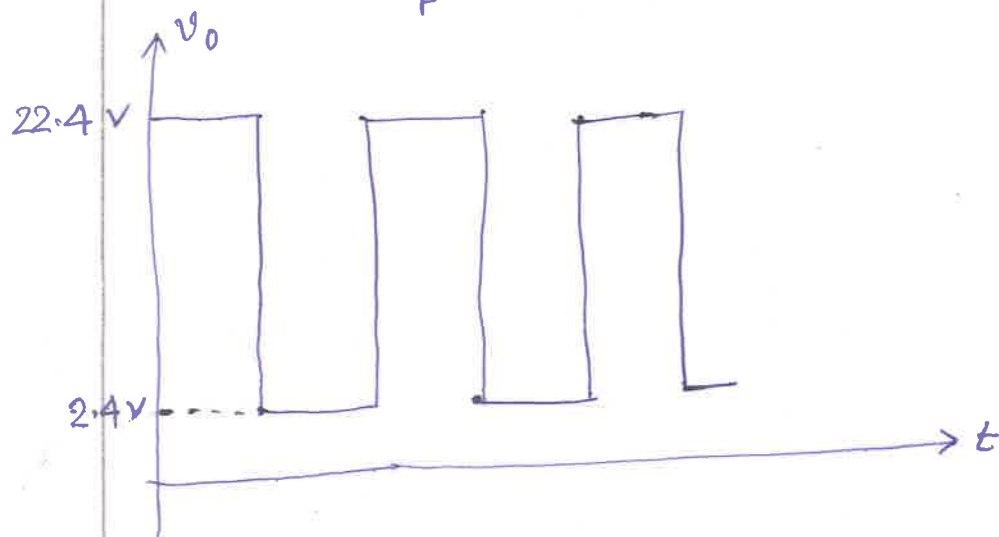(d) During negative half cycle, capacitor charges.  
 $V_C = V_m + 3 - 0.6 = 12.4 \text{ V}$  (2M)

During positive half cycle, diode acts as open circuit.

$$V_{O_p} = V_m + V_C = 22.4 \text{ V} \quad (1M)$$



(2M)

2. (a)

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_{B1} + R_{B2} + (1 + \beta)(R_C + R_E)}$$

$$= 35.9 \text{ } \mu\text{A}$$

(2M)

$$I_{CQ} = 3.59 \text{ mA}$$

(1M)

$$I_{EQ} = 3.63 \text{ mA}$$

(1M)

$$V_{CEQ} = V_{CC} - I_E (R_C + R_E) = 7.77 \text{ V (1M)} \quad (2)$$

Derivation for (s) (3M)

$$S = \frac{1 + \beta}{1 + \frac{\beta(R_C + R_E)}{R_{B1} + R_{B2} + R_C + R_E}} = 38 \quad (2M)$$

2. (b)  $I_{DSS} = 12 \text{ mA}$ ,  $V_P = -3 \text{ V}$ ,  $r_d = 100 \text{ k}\Omega$ ,  $V_{in} = 20 \text{ mV (P-P)}$

$$V_{G1} = \frac{V_{DD} R_2}{R_1 + R_2} = 1.98 \text{ V} \quad V_{GS} = V_{G1} - I_D R_S = 1.98 - 560 I_D$$

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$= 12 \times 10^{-3} \left[ 1 - \frac{1.98 - 560 I_D}{-3} \right]^2$$

$$\therefore I_{D1} = 5.3 \text{ mA}, \quad V_{GS1} = -1 \text{ V}$$

$$I_{D2} = 15 \text{ mA}, \quad V_{GS2} = -6.42 \text{ V}$$

$$\therefore V_{GSQ} = -1 \text{ V} \quad I_{DQ} = 5.3 \text{ mA} \quad g_m = \frac{2 I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GS}}{V_P} \right] \quad (1M)$$

$$Z_{in} = R_1 \parallel R_2 = 9 \text{ M}\Omega \quad g_m = 5.33 \text{ mS} \quad Z_o = r_d \parallel R_D = 2.15 \text{ k}\Omega \quad (2M)$$

$$A_v = -g_m (r_d \parallel R_D) = 11.5 \quad (1M)$$

$$V_o = A_v V_{in} = 230 \text{ mV (P-P)} \quad (1M)$$

3. (a) Circuit diagram of cascode amp - (2M)

$$V_{B1} = \frac{V_{CC} R_{B1}}{R_{B1} + R_{B2} + R_{B3}} = 8 \text{ V} \quad I_{E1} = I_{E2} = \frac{V_{B1} - V_{BE}}{R_E} \quad (3M)$$

$$r_e = \frac{26 \text{ mV}}{I_{EQ}} = 3.5 \Omega$$

Derivation for  $A_v$  and  $A_i$  (3M)

$$A_v = -\frac{R_C}{r_e} = -428.6 \quad (1M)$$

$$A_i = \frac{\beta (R_{B1} \parallel R_{B2})}{(R_{B1} \parallel R_{B2}) + \beta r_e} = 185 \quad (1M)$$

Q3

Page No. 3

Q. No.

Marks

3. (b) Derivation of voltage gain, input impedance, AC equivalent circuit (5M)

$$A_v = \frac{-h_{fe} R_c}{h_{ie} + (1+h_{fe}) R_{E1}} = -6.8 \quad (1/2M)$$

$$Z_{in} = [h_{ie} + (1+h_{fe}) R_{E1}] \parallel R_1 \parallel R_2 = 7k\Omega \quad (1/2M)$$

$$f_{L_{in}} = \frac{1}{2\pi (R_1 \parallel R_2 \parallel h_{ie}) C_{in}} = 3.8 \text{ Hz} \quad (1M)$$

$$f_{L_{C0}} = \frac{1}{2\pi R_c C_0} = 4.8 \text{ Hz} \quad (1M)$$

$$f_{L_{CE}} = \frac{1}{2\pi \left[ \left( \frac{R_1 \parallel R_2 \parallel h_{ie}}{h_{fe}} + R_{E1} \parallel R_{E2} \right) C_E \right]} = 14.27 \text{ Hz} \quad (2M)$$

~~4. (a)~~  $\therefore f_L = 14.27 \text{ Hz}$

4. (a)  $|A_v| \geq 150$ ,  $5 \leq 10$ ,  $V_0 = 5V$ ,  $V_{CC} = 20V$

$$f_L \leq 20 \text{ Hz}$$

Step 1: Select BC147B with potential divider bias.  $h_{ie} = 4.5k\Omega$ ,  $h_{fe_{min}} = 240$ ,  $V_{CE(sat)} = 0.25V$

$$|A_v| = \frac{h_{fe_{min}} R_c}{h_{ie}} \quad \therefore R_c = 2.8k\Omega$$

Select  $R_c = 3k\Omega / \frac{1}{4} \text{ } R_c =$

Step 2  $V_{CEQ} = 1.5 [V_{OP} + V_{CE(sat)}] = 6.74 V$

$$I_{OP} = \frac{V_{OC(P)}}{R_C} = 2.24 \text{ mA}$$

Select  $I_{CQ} = 3 \text{ mA}$

~~Let  $V_{RE} = 10\% V_{CC} = 2 V$~~

$$V_{RE} = V_{CC} - V_{CEQ} - I_C R_C = 2.26 V$$

$$R_E = 753 \Omega$$

Select  $R_E = 720 \Omega$   $P_{RE} = 6.48 \text{ mW}$

$$\therefore R_E = 720 \Omega / \frac{1}{4} W$$

Step 3  $S \leq 10 \therefore$  use  $\beta_{max} = 450$

$$R_{th} = \left[ \frac{\left[ \frac{1 + \beta_{max}}{S} - 1 \right]^{-1} - 1}{\beta_{max}} \right] R_E = 6.6 \text{ k}\Omega$$

$$V_{th} = V_{BE} + I_C \left( \frac{R_{th}}{\beta_{typ}} + R_E \right) = 2.82 V$$

$$R_1 = \frac{V_{CC} R_{th}}{V_{th}} = 35 \text{ k}\Omega$$

$$R_2 = 8.13 \text{ k}\Omega$$

Select  $R_1 = 33 \text{ k}\Omega / \frac{1}{4} W$

$$R_2 = 8.2 \text{ k}\Omega / \frac{1}{4} W$$

Step 4  $C_{C1} = \frac{1}{2\pi (h_{ie} || R_{th}) f_L} = 3 \text{ }\mu\text{F} / 30 \text{ V}$

$$C_E = \frac{1}{2\pi \left[ \frac{h_{ie}}{1 + h_{fe,typ}} || R_E \right] f_L} = 600 \text{ }\mu\text{F} / 30 \text{ V}$$

$$C_O = \frac{1}{2\pi R_C f_L} = 2.65 \text{ }\mu\text{F} / 30 \text{ V}$$

Circuit with designed values

04

05

5

Page No.....

Q. No.

Marks

4. (b) Darlington amplifier circuit (2M)  
D.C. analysis (2M)  
A.C analysis (4M)

$$5. (a) V_{th} = \frac{V_{cc} R_2}{R_1 + R_2} = 7.5 V \quad R_{th} = R_1 \parallel R_2 = 6.87 k\Omega$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = 52.5 \mu A \quad (2M)$$

$$I_{CQ} = \beta I_{BQ} = 10.5 mA \quad I_{EQ} = (1 + \beta) I_{BQ} = 10.55 mA$$

$$r_e = \frac{26 mV}{I_{EQ}} = 2.46 \Omega \quad (1M) \quad \alpha = \frac{\beta}{1 + \beta} = 0.995 \quad (1M)$$

$$Z_{in} = r_e \parallel R_E = 2.45 \Omega$$

$$A_v = \frac{\alpha R_C}{r_e} = 485$$

$$A_I = \frac{-\alpha R_E}{R_E + r_e} = 0.99$$

Derivation (4M)

(2M)

$$5.(b) \quad A_v = -g_m R_D = -6 \quad (1/2 M) \quad (6)$$

$$f_{L_{cin}} = \frac{1}{2\pi (R_s + R_G) C_{in}} = 1.6 \text{ Hz} \quad (1 M)$$

$$f_{L_{co}} = \frac{1}{2\pi (R_D + R_L) C_O} = 3.4 \text{ Hz} \quad (1 M)$$

$$f_{L_{cs}} = \frac{1}{2\pi (R_s \parallel \frac{1}{g_m}) C_s} = 45 \text{ Hz} \quad (1 M)$$

$$\therefore f_L = 45 \text{ Hz}$$

$$f_{H_{in}} = \frac{1}{2\pi (R_s \parallel R_G) (C_{wi} + C_{gs} + (1 - A_v) C_{gd})} \quad (1/2 M) \quad (2 M)$$

$$= 4.3 \text{ MHz}$$

$$f_{H_o} = \frac{1}{2\pi (R_D \parallel R_L) (C_{wo} + C_{ds} + \frac{A_v - 1}{A_v} C_{gd})} \quad (2 M)$$

$$= 8.79 \text{ MHz}$$

$$\therefore f_H = 4.3 \text{ MHz} \quad (1/2 M)$$

High frequency model  $(1 1/2 M)$

07

7

Page No.....

Q. No.

Marks

6. (a) Graphs (4M)  
Explanation with equation (6M)
- (b) Circuit diagram (2M)  
DC analysis (3M)  
AC analysis (5M)
- (c) Graph (1M) Working (4M)

88