

Q. P. Code - 2757G · ECAD

04A0F14 (01)


SE - Sem-III - BME - CBCGS

$\tau_{os} = 20 \text{ ms}$, Page No.....


Q. No.

Q-2-a

Marks

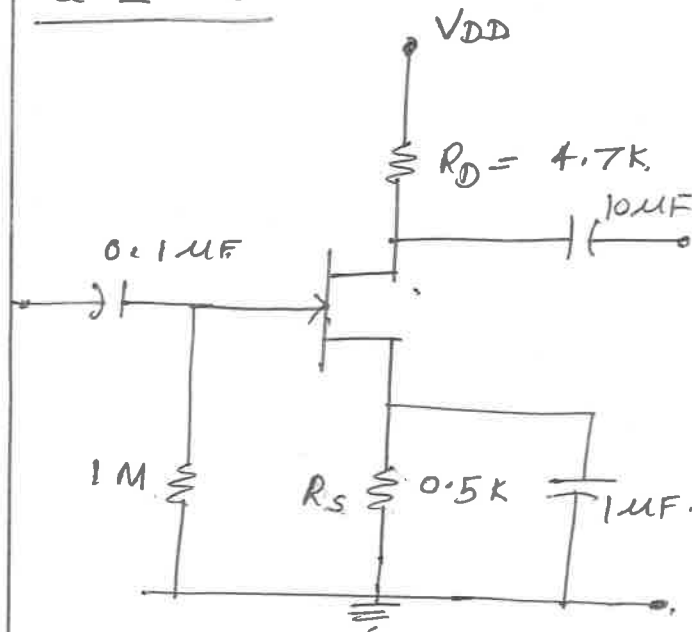
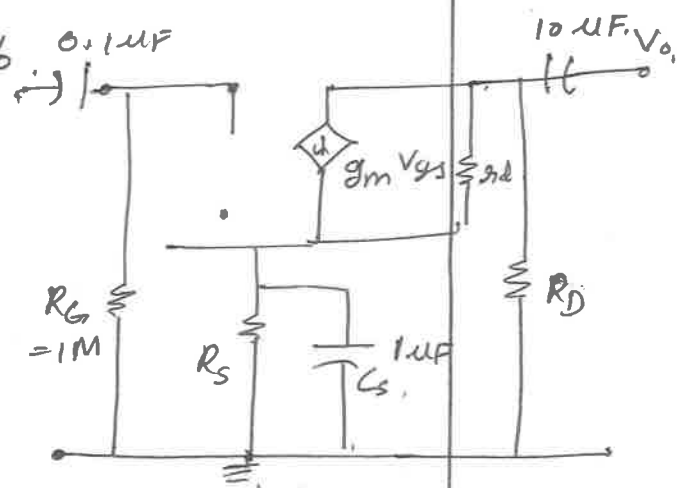
$$\therefore \tau_d = \frac{1}{\tau_{os}} = 50 \text{ K}\Omega$$



①

$$f_{LC_{in}} = \frac{1}{2\pi R C_{in}} = \frac{1}{2\pi \cdot R_{C_{in}} \cdot C_{in}}$$

$$R_{C_{in}} = R_G =$$

$$\therefore f_{LC_{in}} = \frac{1}{2\pi \times 1 \text{ M} \times 0.1 \times 10^{-6}} =$$

②

$$f_{LC_s} = \frac{1}{2\pi R_{C_s} \cdot C_s}$$

$$\text{where } R_{C_s} = \frac{1}{2\pi \left[0.5 \parallel \frac{1}{g_m} \right] C_s}$$

$$g_m = g_{m0} \left[1 - \frac{V_{gs}}{V_P} \right]$$

$$= \frac{1}{2\pi [0]}$$

③

$$f_{LC_{o2}} = \frac{1}{2\pi R_{C_{o2}} \cdot C_{o2}}$$


$$R_{C_{o2}} = R_D \parallel \tau_d$$

$$= \frac{1}{2 \times \pi \times 10 \times 10^{-6} \times X}$$

Q. No.

Q-2-b

Marks

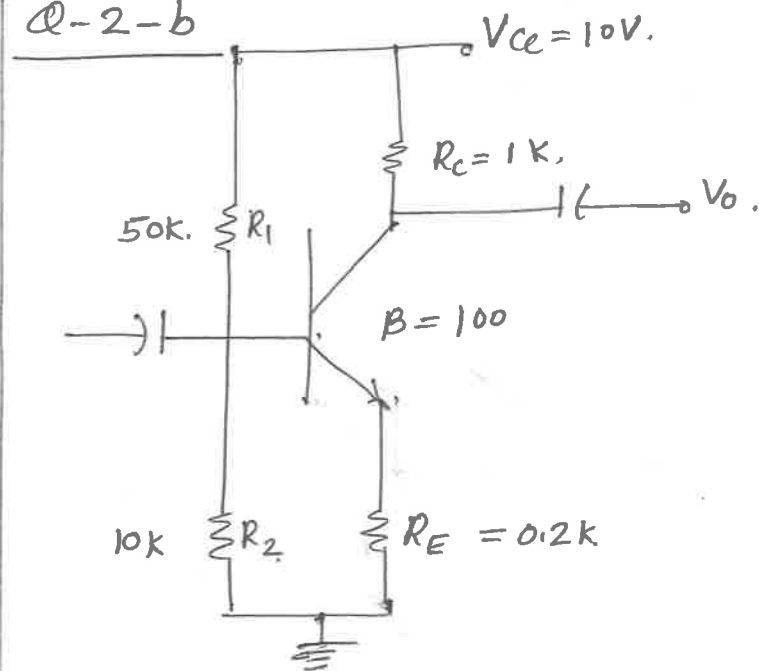

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{50k \times 10k}{60k} = 8.33k$$

$$V_{th} = \frac{V_{cc} \times R_2}{R_1 + R_2} = 10 \times \frac{10k}{60k} = 1.66V$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = \frac{1.66 - 0.7}{8.33k + (101 \times 0.2k)}$$

$$= \frac{0.96}{28.53k}$$

$$= 0.033 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 100 \times 0.033 \text{ mA}$$

$$= 3.36 \text{ mA}$$

$$V_{CEQ} = V_{cc} - I_C (R_C + R_E)$$


$$= 10 - 3.36 \text{ mA} (1k + 0.2k)$$

$$= 10 - 4.03 = 5.97 \text{ V}$$

ac equivalent

Q. No.

Marks

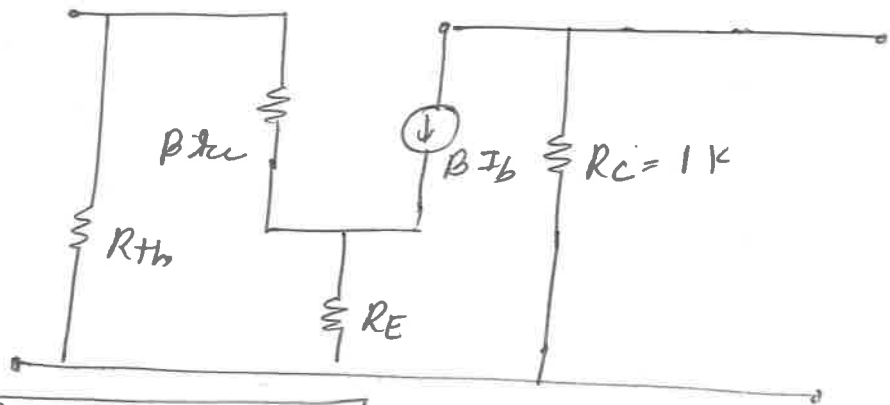

R_E is bypassed.

$$A_v = \frac{R_c}{R_E} \cdot \frac{R_c}{r_e}$$

$$r_e = \frac{26 \text{ mV}}{I_{ce}}$$

$$= \frac{1 \text{ K}}{0.2 \text{ K}}$$

$$= \frac{26 \text{ mV}}{3.36 \text{ mA}}$$

$$= 0.129 \cdot 10^3$$

$$= 7.73 \Omega$$

$A_v = 129$

$$R_i = R_{Th} \parallel [\beta R_c + (1 + \beta) R_E]$$

$$= 8.33 \parallel [100 \times 7.73 + 101 \times 0.2 \text{ K}]$$

$$= 8.33 \parallel [773 + 20.2 \text{ K}]$$

$$= 8.33 \text{ K} \parallel 20.97 \text{ K}$$

$$= \frac{8.33 \times 20.97}{8.33 + 20.97} = \frac{174.68}{29.3} = 5.96 \text{ K}$$

$$R_o = R_c = 1 \text{ K}$$

R_E unbypassed

$$A_v = \frac{R_c}{R_E}$$

$$= \frac{1 \text{ K}}{0.2 \text{ K}} = 5$$

$|A_v| = 5$

Q. No.

②

If R_L is connected - $|A_v| = \frac{R_C \parallel R_L}{R_E}$
 R_E unbypassed. -

Marks

If R_L is connected' = $|A_v| = \frac{R_C \parallel R_L}{R_E}$
 R_E bypassed.

$$= \frac{\cancel{R_C} \parallel \cancel{R_L}}{\cancel{R_E}}$$

R_L is not mentioned. Student can assume
 & proceed.

Q. No. Q-3 - Different design approaches can be considered.

Marks

Given $|A_v| \geq 70$, $V_o = 1.5 \text{ V}$,
 $f_L = 15 \text{ Hz}$. (peak is given).


R_i not specified select suitable transistor.
 BC147A or BC147B.

From data sheet min or typical values can be taken.

- Step I - Selection of transistor. — ①
- II - selection of R_c from gain eqⁿ - ②
- III - Determination of operating point — ②
 $Q. (V_{CEQ}, I_{CQ})$. - check operating condition - ②
 $I_{CQ} \cdot R_c > V_o(\text{peak})$.
- IV - selection of R_E . — ①
- V - selection of V_{CC} . — ②
- VI - Design of R_1 & R_2 . — ②
- VII - Design of C_{in} , C_{co} , C_{μ} . — ③
- VIII - Designed ckt to be drawn. — ②
- Calculate A_v — ①
 Z_i — ①
 Z_o . — ①

Q. No. Q-5-C

Marks

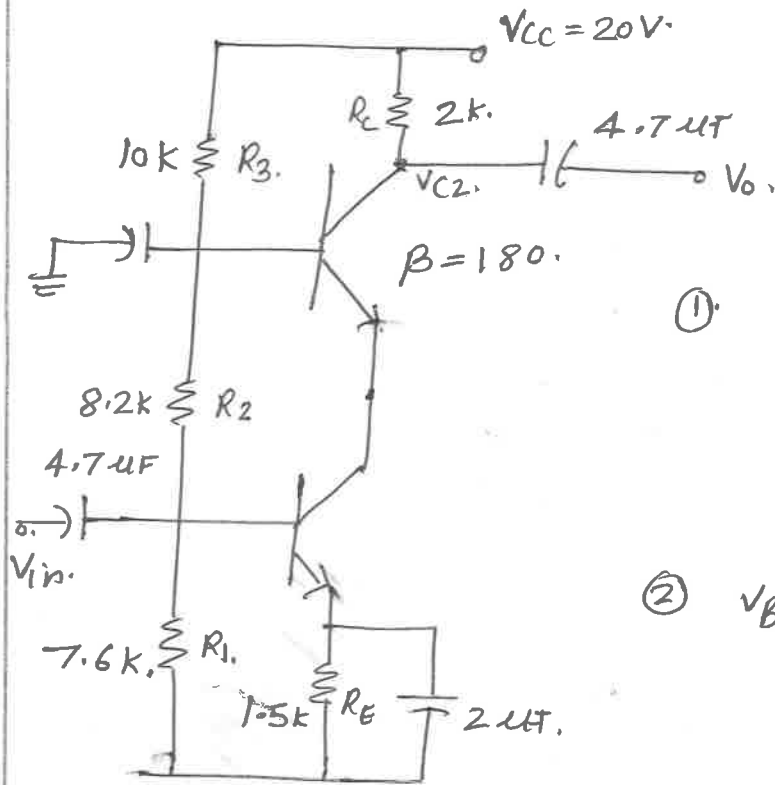

① $I_{C1} \cong I_{C2} \cong I_{E1} \cong I_{E2}$

②
$$V_{B1} = R_1 \times \frac{V_{CC}}{R_1 + R_2 + R_3}$$

$$= 20 \times \frac{7.6k}{25.8k} = 5.89V$$

③
$$V_{B2} = V_{CC} \cdot \frac{R_1 + R_2}{R_1 + R_2 + R_3}$$

$$= 20V \times \frac{7.6 + 8.2}{25.8k}$$

$$= 12.24V$$

$V_{CE2} = V_{C1}$

④
$$V_{E2} = V_{B2} - V_{BE2}$$

$$= 12.24 - 0.7 = 11.54V$$

$$V_{C2} = V_{CC} - I_{C2} \cdot R_{C2}$$

$$= \text{down}$$

⑤
$$V_{E1} = V_{B1} - V_{BE1}$$

$$= 5.89 - 0.7V = 5.19V$$

$V_{CE2} = V_{C2} - V_{E2}$

~~$$I_{C2} = \frac{V_{CC} - V_{C2}}{R_{C2}}$$~~

$$I_{E1} = \frac{V_{E1}}{R_E}$$

$$= \frac{5.19V}{1.5k}$$


$$I_{E1} = 3.46mA \cong I_{C2}$$

$$r_e = \frac{26 \text{ mV}}{I_{CQ}} = \frac{26 \text{ mV}}{3.46 \text{ mA}} = 7.51 \Omega.$$

Q. No.

d.c analysis -

Marks

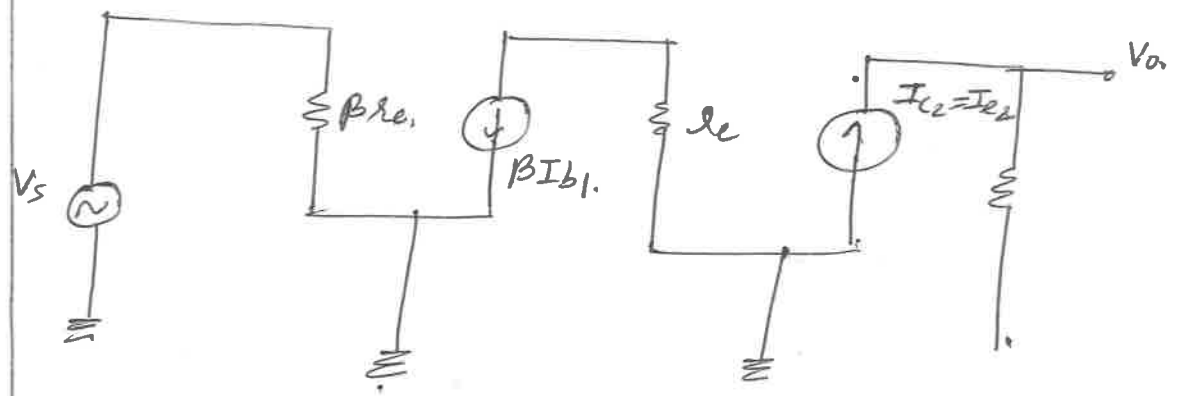

$$Z_{in} = R_{BB} \parallel \beta \cdot r_e.$$

$$= (R_1 \parallel R_2) \parallel \beta \cdot r_e = (7.6 \parallel 8.2) \parallel \cancel{180} (180 \times 7.51)$$

$$= \left[\frac{7.6 \times 8.2}{7.6 + 8.2} \right] \parallel [180 \times 7.51]$$

$$Z_o = R_C = 2 \text{ k}.$$

$$= 62.32 \parallel 1351.8 = 3.94 \text{ k} \parallel 1.35 \text{ k} = \frac{3.94 \times 1.35}{3.94 + 1.35}$$

$$Z_{in} = 1.005 \text{ k}$$

$$A_{vT} = \frac{-R_C}{r_e}$$


$$|A_{vT}| = \frac{2 \text{ k}}{7.51}$$

$$|A_v| = 0.26$$

Q. No.

Q-6

Marks

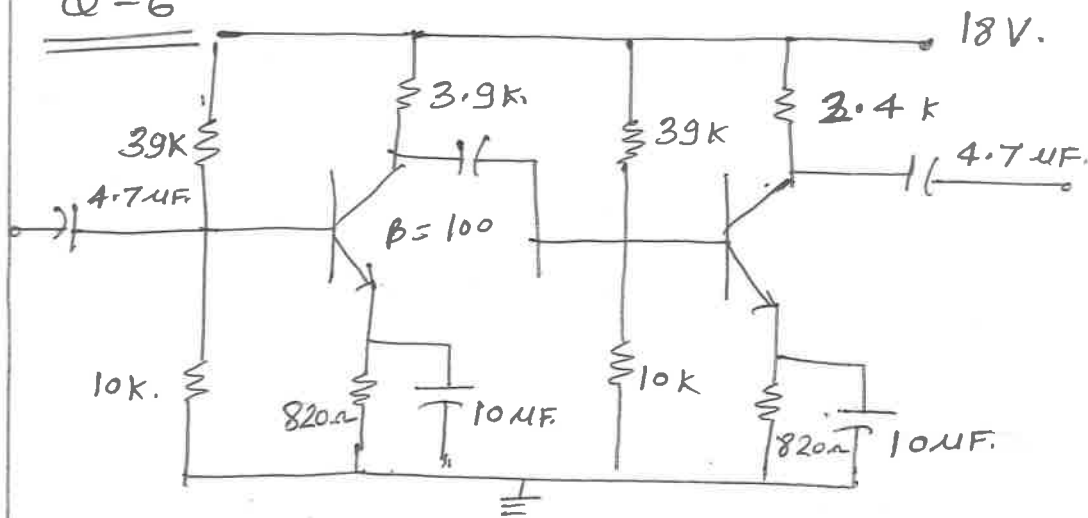

D.C analysis:- ~~Q~~ I_{CQ} remains same for both the stages.

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{39k \times 10k}{39 + 10} = 7.95k.$$

$$V_{th} = V_{CC} \frac{R_2}{R_1 + R_2} = \frac{18V \times 10k}{39k + 10k} = 3.67V.$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E}$$

$$= \frac{3.67 - 0.7}{7.95 + (101 \times 0.82k)}$$

$$= \frac{2.97}{90.77k}$$

$$= 0.032 \text{ mA.}$$

$$I_{CQ} = \beta I_{BQ} = 100 \times 0.032 = 3.2 \text{ mA.}$$

Q. No.


$$\begin{aligned}
 V_{CEQ_1} &= V_{CC} - I_C (R_{C_1} + R_{E_1}) \\
 &= 18 - 3.2 \text{ mA} (3.9 + 0.82 \text{ k}) \\
 &= 18 - 15.40 = 18 - 15.104 \\
 &= 2.896 \text{ V.}
 \end{aligned}$$

$$\begin{aligned}
 V_{CEQ_2} &= V_{CC} - I_C (R_{C_2} + R_{E_2}) \\
 &= 18 - 3.2 \text{ mA} (2.4 \text{ k} + 0.82 \text{ k}) \\
 &= 18 - 10.304 \\
 &= 7.698 \text{ V.}
 \end{aligned}$$

If same R_C is considered while solving give full marks. (for both stages)

ac equivalent ckt.

~~$|A_v| = R_c$~~

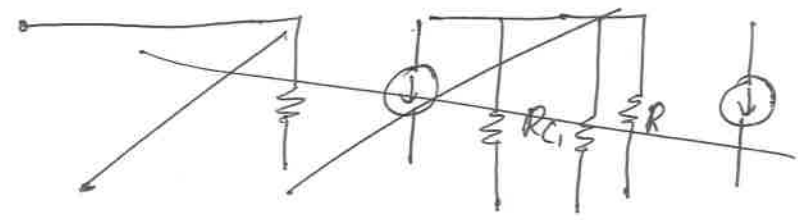


~~$r_e = \frac{R_c}{\beta}$~~

$$r_e = \frac{26 \text{ mV}}{I_{CQ}}$$

$$= \frac{26 \text{ mV}}{3.2 \text{ mA}} = 8.125 \Omega \Rightarrow 0.812 \text{ k.} \quad \beta \cdot r_e = 812.5 \Omega$$

Q. No.

Marks

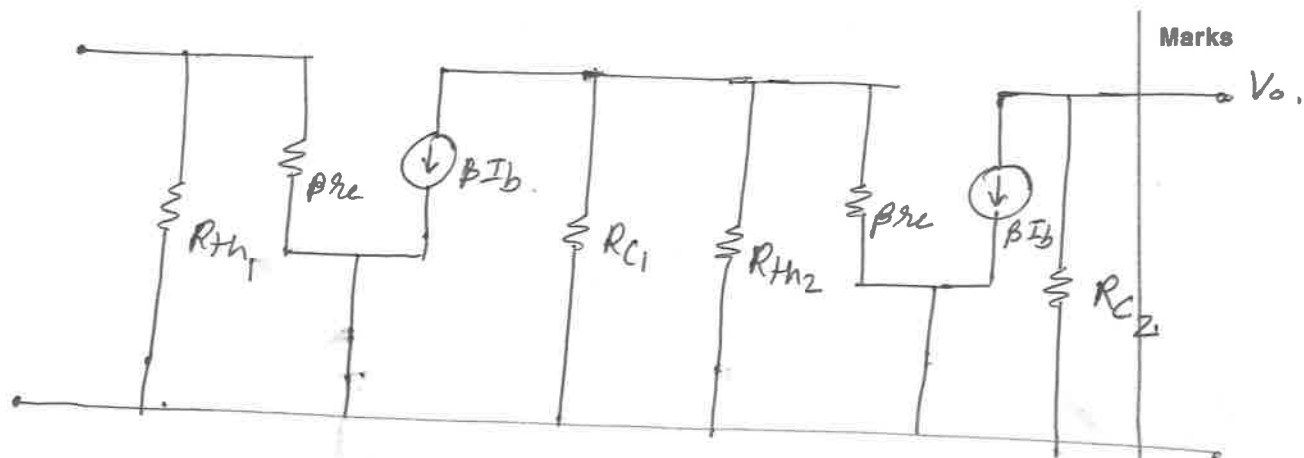

$$|A_{v1}| = \frac{R_{C1} \parallel R_{th2} \parallel \beta r_e}{r_e} \quad 2.4k \parallel 7.95k \parallel 0.81k$$

$$= \frac{0.56k}{8.12}$$

$$= 68.96$$

$$\frac{1}{R_p} = \frac{1}{2.4} + \frac{1}{7.95} + \frac{1}{0.81}$$

$$= 0.41 + 0.12 + 1.23$$

$$R_p = \frac{1}{1.76}$$

$$= 0.56k$$

$$|A_{v2}| = \frac{R_C}{r_e}$$

$$= \frac{2.4k}{8.12} = \text{or } 295.5$$

$$A_{v(\text{total})} = A_{v1} \times A_{v2}$$

$$= 68.96 \times 295.5$$

$$\boxed{Z_i = R_{th1} \parallel \beta \cdot r_e}$$

$$\boxed{Z_o = R_{C2}}$$

~~17 of 17~~
 R_s can be assumed or
 without R_s can be considered

Low frequency equivalent.

Page No.....

(11)

Q. No.

Marks

$$f_{LCE1} = \frac{1}{2\pi X_{CE1} \cdot C_{E1}}$$

$$f_{LCC3} = \frac{1}{2\pi X_{CC3} \cdot C_{C3}}$$

$$X_{CE1} = R_s + (R_{th1} \parallel \beta R_e)$$

$$X_{CC3} = R_c$$

$$f_{LCC2} = \frac{1}{2\pi X_{CC2} \cdot C_{C2}}$$

$$f_{LCE2} = \frac{1}{2\pi X_{CE2} \cdot C_{E2}}$$

$$X_{CC2} = R_c + (R_{th2} \parallel \beta R_e)$$

$$X_{CE2} = \left\{ \frac{(R_c \parallel R_{th2}) + \beta R_e}{1 + \beta} \right\} \parallel R_{E2}$$

$$f_{LCE1} = \frac{1}{2\pi X_{CE1} \cdot C_{E1}}$$

$$X_{CE1} = \left\{ \frac{(R_s \parallel R_{th1}) + \beta R_e}{1 + \beta} \right\} \parallel R_{E1}$$

Approximation. ~~formulas~~ should be considered
 for

Highest freqⁿ cut off is lowest one,