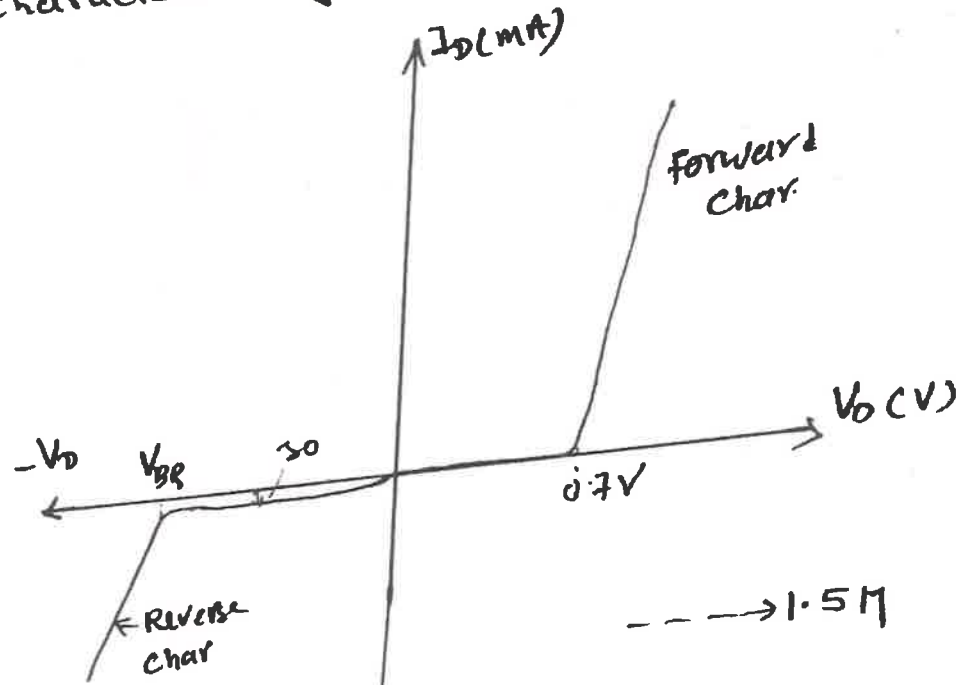



(Paper solution)

Q.P. Cod. 40502

Q.1 (a) Characteristics of P-N junction diode




Characteristics of Zener diode

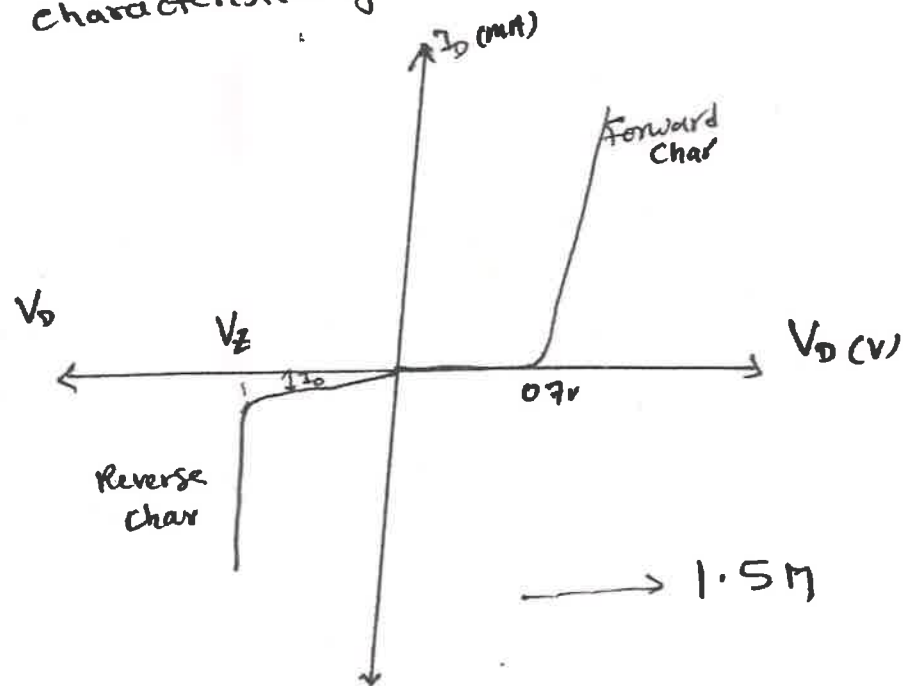

Description -----> 2M

Q.1 (b)

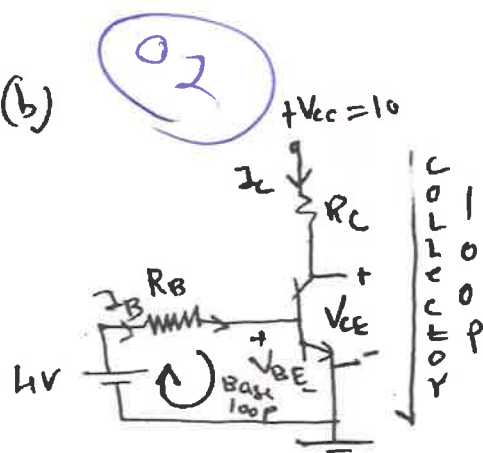

KVL to collector loop

$$V_{cc} - I_c R_c - V_{CE} = 0$$

$$V_{cc} - I_c R_c = V_{CE}$$

$$V_{CE} = 10 - 3.3 \text{ mA} \times 2 \text{ k}\Omega$$

$$V_{CE} = 3.4 \text{ V}$$

KVL to base loop

$$4 - I_B R_B - V_{BE} = 0$$

$$4 - 0.7 = I_B R_B$$

$$I_B = \frac{3.3}{220 \text{ k}} = 15 \mu\text{A}$$


$$I_B = 15 \mu\text{A}$$

$$I_c = \beta \cdot I_B = 220 \cdot 15 \mu\text{A}$$

$$I_c = 3.3 \text{ mA}$$

- Point to be covered
- Q.1 (c) → feedback capacitance
- effect of miller theorem
 - Parasitic and inter electrode capacitance at high freq.

Q.1 (d) effect of temperature on JFET

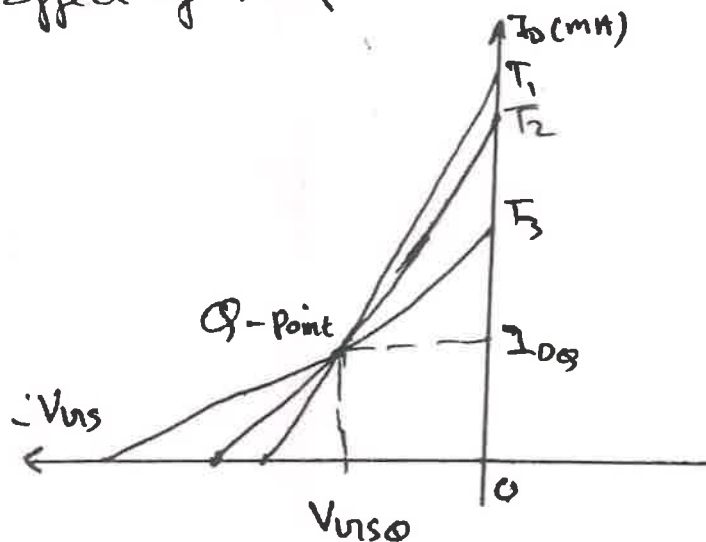

Increase in I_D with temp = Decrease in I_D with Temp

$$\Delta I_D = (0.7\% / ^\circ\text{C}) |I_D|$$

②

$$|V_p| - |V_{gs}| = 0.63 \text{ V}$$

3M

1(d)

Q3


Need of cascaded amplifier

- To increase overall voltage gain
- To control input impedance and output impedance → 2M

Types of cascaded configurations

- (i) CE-CE amplifier
 - (ii) CS-CE amplifier
 - (iii) CS-CS amplifier
- } 3M

Q.2 (a) For Fixed bias

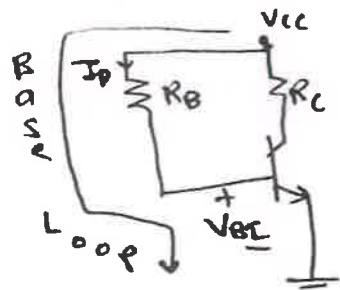

For current stability factor

$$S = \frac{1 + \beta}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

From base loop

$$V_{CC} - I_B R_B - V_{BE} = 0$$


diff. w.r.t. I_C

$$\frac{d}{dI_C} (V_{CC} - I_B R_B - V_{BE}) = 0$$


$$\therefore \frac{dI_B}{dI_C} = 0$$

$$S = 1 + \beta$$

For Voltage divider Bias

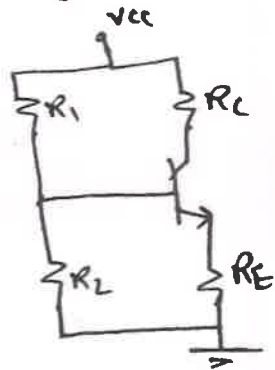


using Voltage divider rule

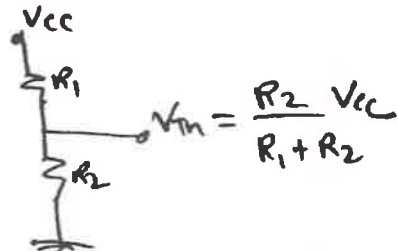

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$\therefore R_{th} = R_1 \parallel R_2$$

Thevenin's equivalent ckt

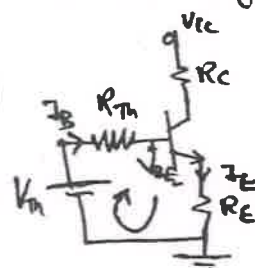

From base loop

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (I_C + I_B) R_E = 0$$

$$V_{th} - V_{BE} - I_B R_{th} - I_C R_E - I_B R_E = 0$$

$$V_{th} - V_{BE} - I_B (R_{th} + R_E) - I_C R_E = 0$$

diff w.r.t. I_C

$$0 - (R_{th} + R_E) \frac{dI_B}{dI_C} - R_E \frac{dI_C}{dI_C} \Rightarrow$$

$$-(R_{th} + R_E) \frac{dI_B}{dI_C} = R_E$$


$$\frac{dI_B}{dI_C} = \frac{-R_E}{R_{th} + R_E}$$

$$S = \frac{1 + \beta}{1 - \beta \left(\frac{-R_E}{R_{th} + R_E} \right)}$$

$$S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_{th} + R_E} \right)}$$

③

Q. 2 (b) DC equivalent ckt

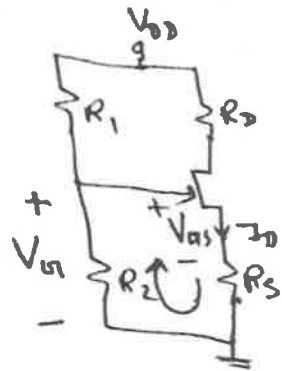

Using voltage divider rule

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$= \frac{180K}{420K + 180K} \times 20$$

$$= 6V$$

From gate loop

$$V_{GS} - V_{GS} - I_D R_S = 0$$

$$6 - V_{GS} - I_D \times 2.7K = 0$$

$$6 - I_D \times 2.7K = V_{GS} \quad \text{--- (1)}$$

For JFET

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\therefore I_D = 12m \left(1 - \frac{(6 - I_D \times 2.7K)}{-4}\right)^2$$

$$I_D = 12m \left[1 + \frac{6 - I_D \times 2.7K}{4}\right]^2$$

on solving

$$I_D = 2.967mA$$


~~From equation~~

from eq (1)

$$V_{GS} = 6 - 2.967m \times 2.7K$$

$$V_{GS} = -2.01V$$

ac equivalent ckt

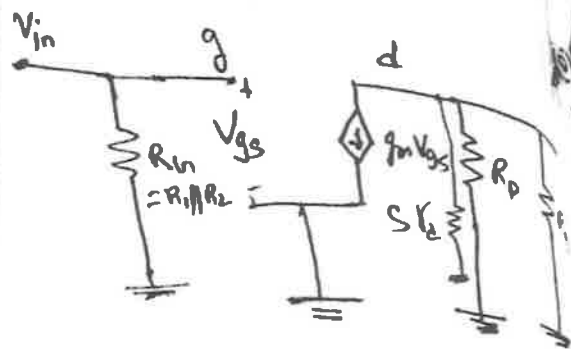

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$= \frac{2 \times 12m}{4} \left(1 - \frac{-2.01}{-4}\right)$$

$$g_m = 2.985mS$$

$$Z_i = R_{in} = R_1 || R_2$$

$$Z_i = 420K || 180K = 126K\Omega$$

$$Z_i = 126K\Omega$$

$$Z_o = R_L || R_D || \frac{1}{g_m} = 4K || 2.7K || 50\Omega$$


$$Z_o = 1.561K\Omega$$

$$A_v = -g_m (R_L || R_D || \frac{1}{g_m})$$


$$= -2.98m (1.561K)$$

$$A_v = -4.653$$

3(a)

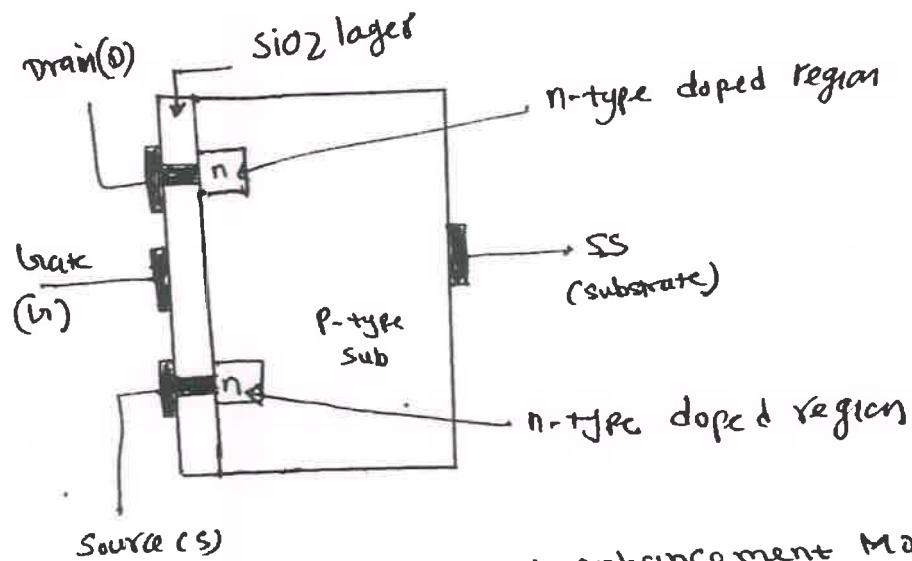

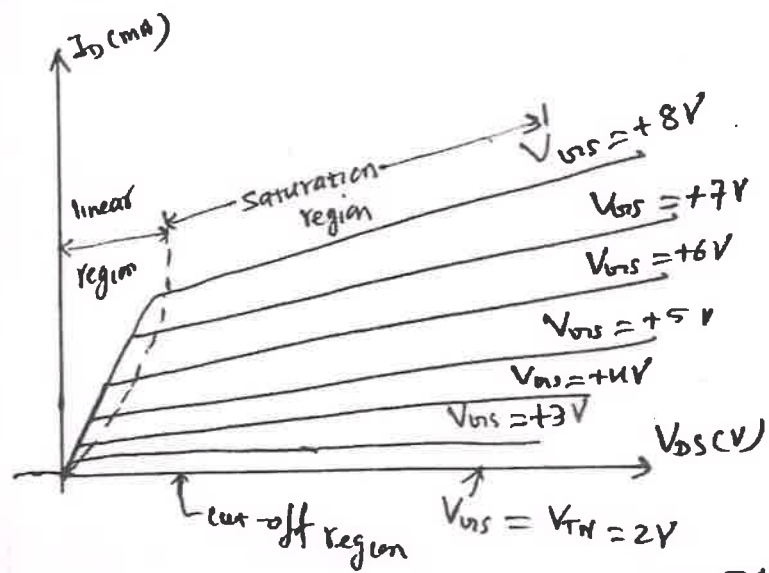Construction of n-channel enhancement MOSFET




$$I_D = K_n [V_{GS} - V_{th}]^2 \quad \text{--- In Saturation region}$$

$$I_D = K_n [2(V_{GS} - V_{th})V_{DS} - V_{DS}^2] \quad \text{--- linear region}$$

Description --- 3M

(5)

Q.3 (b)

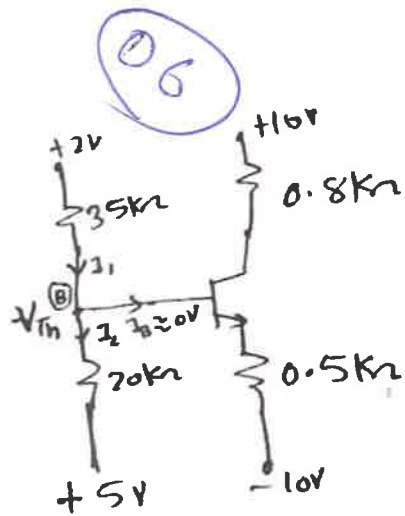

KCL at node (B)

$$\frac{2 - V_{th}}{35k} = \frac{V_{th} - 5V}{20k}$$

on solving


$$V_{th} = 3.90V$$

$$R_{th} = R_1 || R_2$$

$$= 35k || 20k$$

$$R_{th} = 12.72k\Omega$$

Thevenin's equivalent ckt

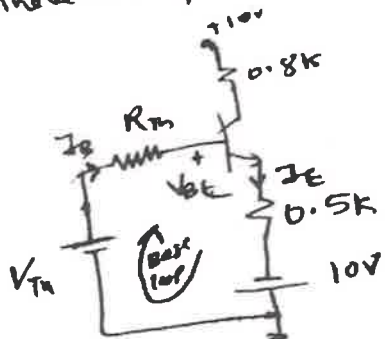

KVL to base loop

$$V_{th} - I_B R_{th} - V_{BE} - I_E (0.5k) + 10 = 0$$

$$3.90 - 0.7 + 10 = I_B R_{th} + (1 + \beta) I_B (0.5k)$$

$$I_B = \frac{13.20}{R_{th} + (1 + \beta)(0.5k)} = 108.79 \mu A$$

$$I_C = \beta \cdot I_B = 100 \times 108.79 \mu A$$

$$I_C = 20.87 mA$$

KVL from collector loop

$$10 - I_C (0.8k) - V_{CE} - I_E (0.5k) + 10 = 0$$

$$V_{CE} = 20 - 20.87 mA \times 0.8k - 20.87 mA \times 0.5k$$


$$V_{CE} = -7.13V$$

Q.4 (a) (i) Selection of Transistor

→ BC147B having $h_{ie} = 4.5k\Omega$

(ii) selection of biasing ckt

→ 1M.


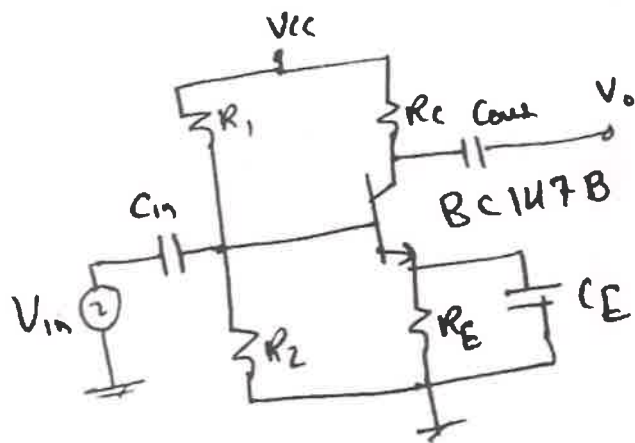


Selection of each component 1M/each

Selection of V_{CC} → 1M

1.5(a)

Cascode amplifier

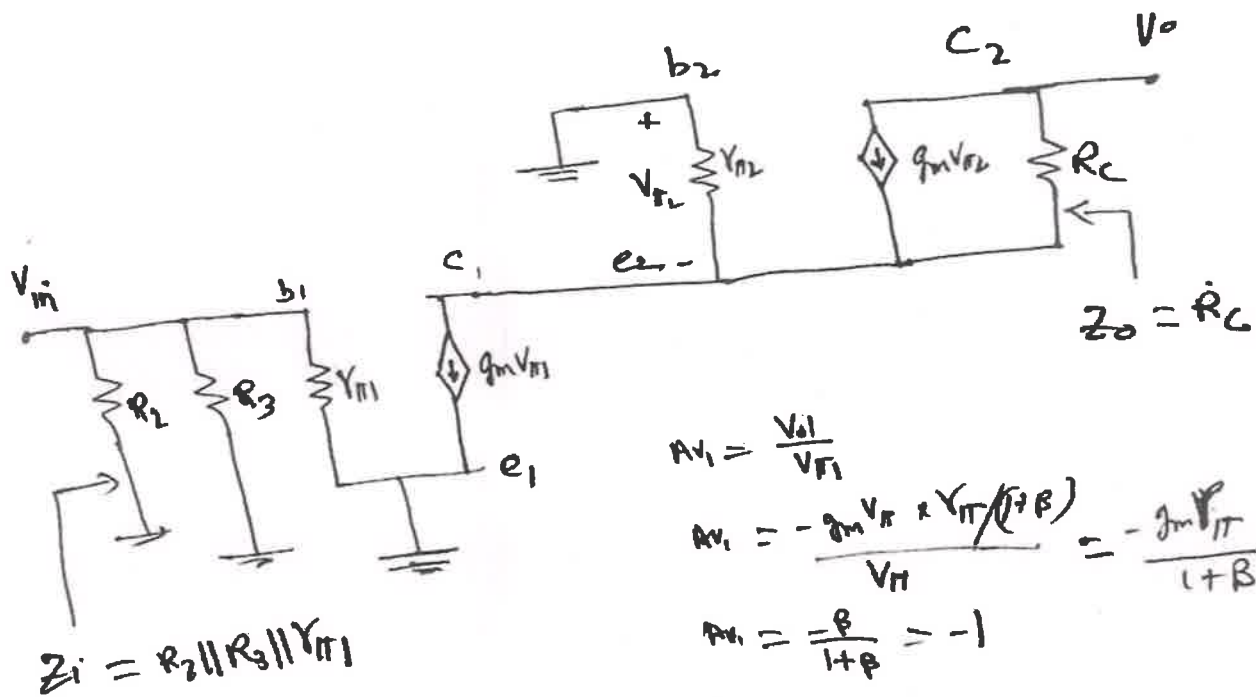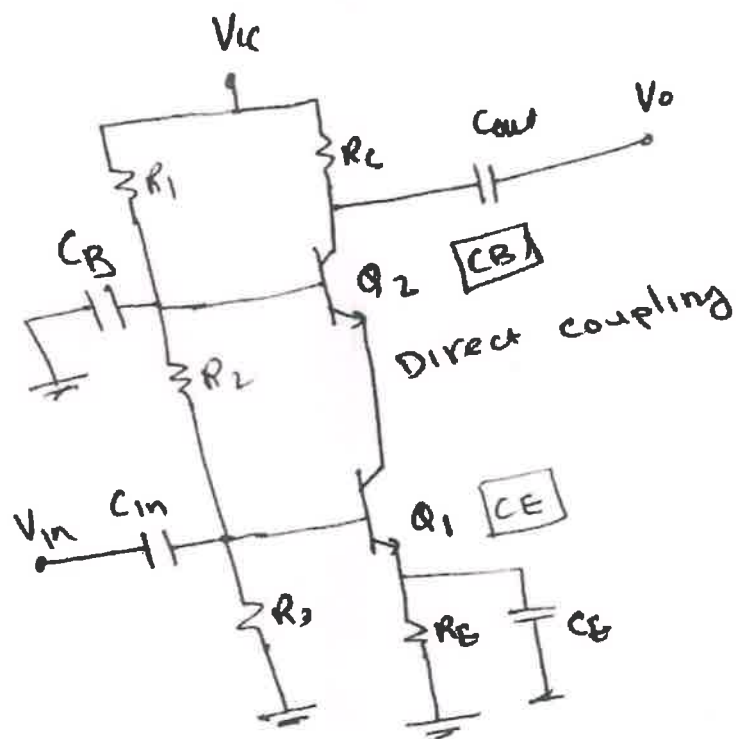

$$Z_i = R_2 \parallel R_3 \parallel Y_{\pi 1}$$

$$A_{V1} = \frac{V_{o1}}{V_{i1}}$$

$$A_{V1} = \frac{-g_m V_{BE} \times Y_{\pi 2} / (1+\beta)}{V_{i1}} = -\frac{g_m Y_{\pi 2}}{1+\beta}$$

$$A_{V1} = \frac{\beta}{1+\beta} = -1$$


$$A_{V2} = g_m R_C$$

$$A_{VT} = A_{V1} \times A_{V2}$$

$$A_{VT} = g_m R_C$$

Q5(b) DC equivalent ckt

(1) JFET

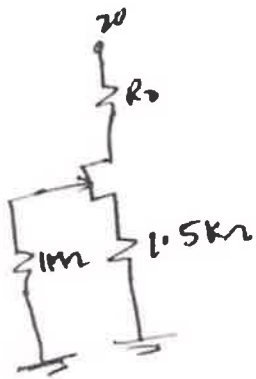

For JFET, $I_{B1} = 0$

$\therefore R_{in}$ can be replaced by short

$$\therefore V_{GS} = -I_D R_s = -I_D \times 1.5K$$

$$\therefore I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 10mA \left[1 - \frac{-I_D \times 1.5K}{-4}\right]^2$$

$$I_D = 10mA \left[1 - \frac{I_D \times 1.5K}{4}\right]^2$$

on solving

$$I_D = 1.6mA$$


$$V_{GS} = -1.6mA \times 1.5K$$

$$V_{GS} = -2.4V$$


$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{20mA}{4} \left(1 - \frac{-2.4}{-4}\right)$$

$$g_m = 2mS$$


ac equivalent ckt

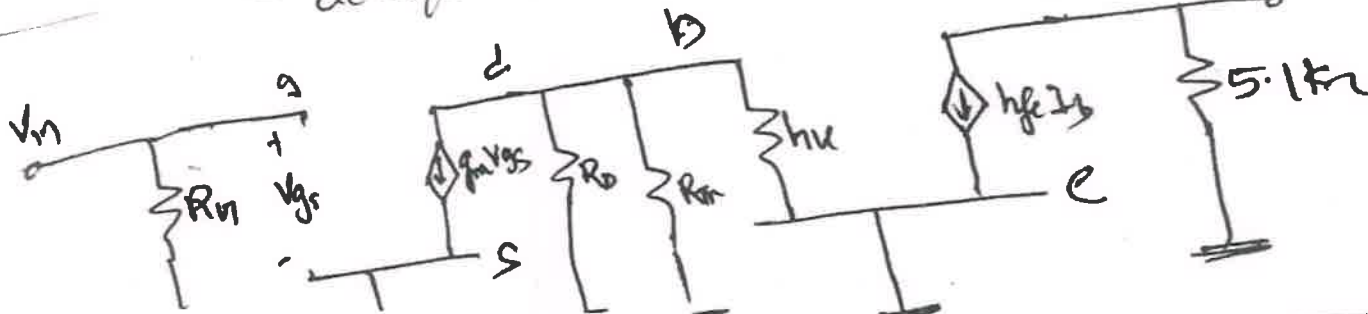

BJT
20V

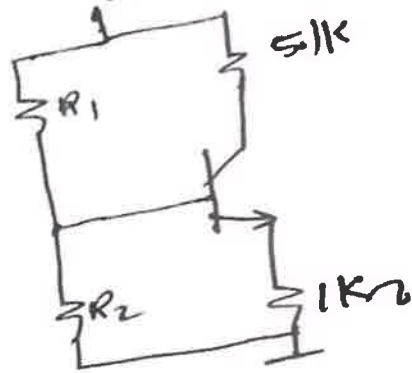

Voltage divider rule

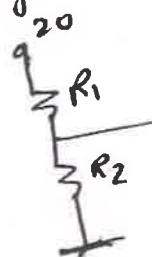


$$V_B = \frac{R_2}{R_1 + R_2} \times 20$$

$$= \frac{33K}{120K + 33K} \times 20 = 4.31$$

$$R_{Th} = R_1 \parallel R_2 = 120K \parallel 33K = 25.88K$$

Thevenin's equivalent ckt

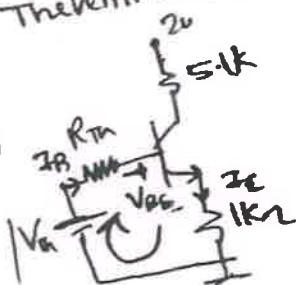

From Base loop

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (1+\beta)R_E}$$

$$I_B = \frac{4.31 - 0.7}{25.88K + 181 \times 1K} = 17.44\mu A$$

$$I_E = 3.14mA$$

Qc

$$\begin{aligned} A_{v1} &= \frac{-g_m (R_D \parallel R_m \parallel h_{ie})}{1 + g_m R_S} \\ &= \frac{-2m (3k \parallel 25.88k \parallel 4.5k)}{1 + 2m \times 1.5k} \\ &= \frac{-3.36}{1 + 3} = -0.84 \end{aligned}$$

$$A_{v2} = \frac{-h_{fe} R_L}{h_{ie}} = \frac{-180 \times 5.1k}{4.5k} = -204$$

Total (overall voltage gain), $A_{vT} = A_{v1} \times A_{v2}$


$$A_{vT} = (-0.84) (-204)$$

$$A_{vT} = +171.36$$

Q.6 (a) Self biasing for JFET

- Zero temp-drift condition.
- Circuit diagram
- Transfer char. with Q-point

(b) Miller Theorem

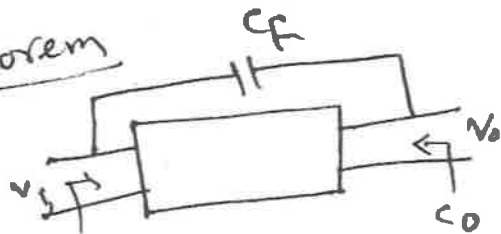


$$C_i = (1 - A_v) C_f \quad \& \quad C_o = (1 - \frac{1}{A_v}) C_f \quad (\text{Derivations})$$

(9)


Q.6(c) MOSFET applications

- CS amplifier
 - Inverter/Not gate
- Using CMOS

Q.6(d) Zener diode

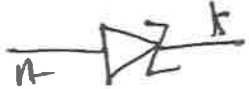- symbol 
- Characteristics
- Zener breakdown
- Zener voltage regulator

Q.6(e) Darlington Amplifier

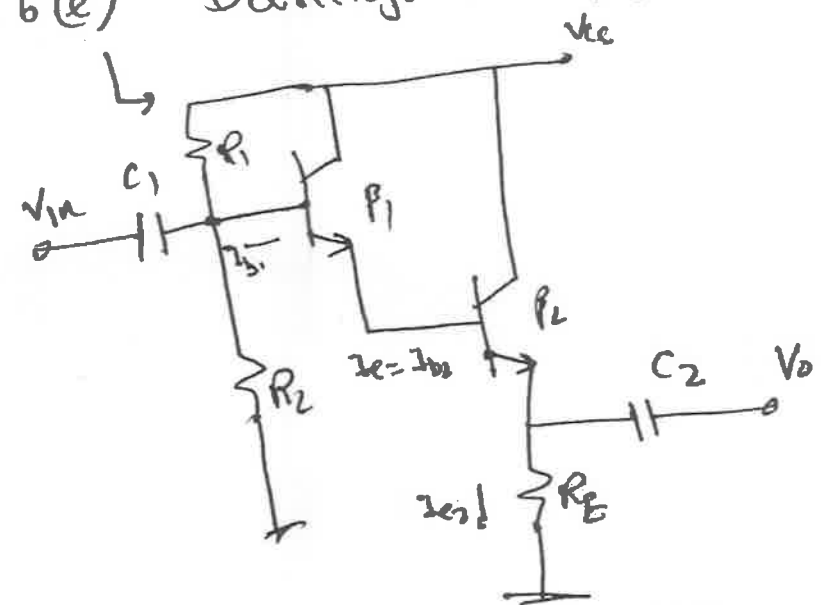

- ckt diagram.
- $\beta_T = \beta_1 \times \beta_2$
- Need
- Applications