

Questions should be —
WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.
SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,
so as to avoid mistakes in the printed question papers.

Duration Hours.

Total Marks assigned to the paper

Q. No.

Marks

SOLUTION

SEM III, S.E Biomed.


N.B.: Electrical Network Analysis & Synthesis
(CBCGS)

Q. 1a)
$$Z(s) = \frac{15(s+1)(s+0.5+j1.32)(s+0.5-j1.32)}{8(s+4)(s+2)}$$
 (03)


zeros at $s = -1, -0.5-j1.32, -0.5+j1.32$ (02)

poles at $s = 0, -4, -2$

b)

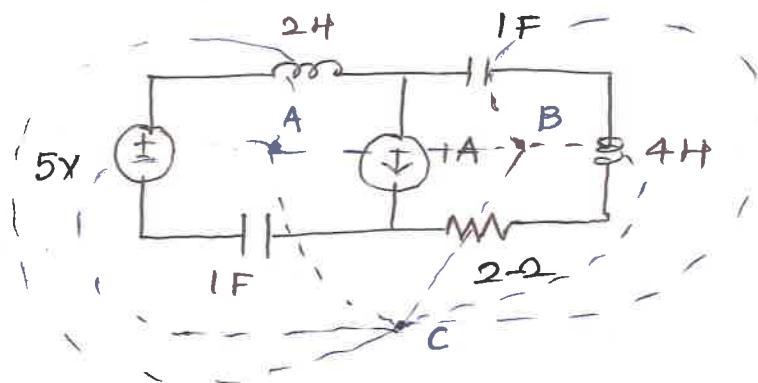

(02)

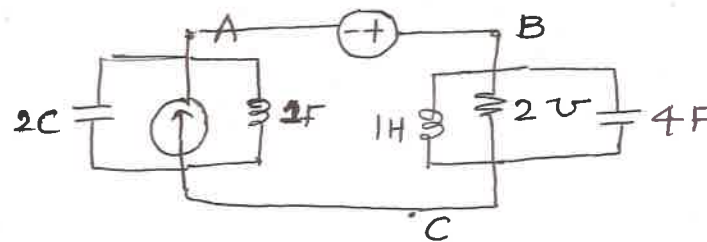

(03)

c)

$$5 + 2Ix = Ix$$

$$Ix = -5$$

$$Ix = \frac{V_A}{6}$$

$$V_A = -30$$

———— (02)

———— (01)

———— (02)

Q2

1 d) $P(s)$ is a odd polynomial

$$P'(s) = 5s^4 + 9s^2 + 2$$

$$\frac{P(s)}{P'(s)} = \frac{5s^4 + 9s^2 + 2}{5s^4 + 9s^2 + 2} \cdot \frac{s^5 + 3s^3 + 2s}{s^5 + 3s^3 + 2s} \left(\frac{3}{5} \right)$$

$$\frac{6/s^3 + 8/s}{5s^4 + 9s^2 + 2} \cdot \frac{5s^4 + 9s^2 + 2}{5s^4 + 9s^2 + 2} \left(\frac{29}{6} s \right)$$

$$\frac{7/s^2 + 2}{6/s^3 + 8/s} \cdot \frac{6/s^3 + 8/s}{6/s^3 + 8/s} \left(\frac{18}{35} s^3 \right)$$

$$\frac{244/s}{7/s^2 + 2} \cdot \frac{7/s^2 + 2}{7/s^2 + 2} \left(\frac{245}{732} s \right)$$

$$\frac{244/s}{7/s^2 + 2} \left(\frac{244}{70} s \right)$$


$$\frac{244}{35} s$$

0

∴ Given polynomial is Hurwitz

Q.2 a) complete incidence matrix is

	1	2	3	4	5
A	0	-1	1	0	0
B	0	0	-1	-1	-1
C	-1	0	0	0	1
D	1	1	0	1	0

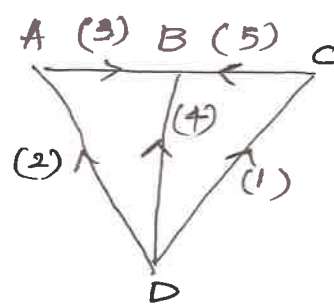

	1	2	3	4	5
tree 2	0	1	1	-1	0
tree 1	1	0	0	-1	1
cutset 3	0	-1	1	0	0
4	0	0	-1	-1	-1
5	-1	0	0	0	1



Q. No.

Marks

Q.2 b)

$$V_N = 5V.$$

To find I_{sc} .

Apply KCL.

$$I = \frac{V}{5} + 4I_{sc} + I_{sc}$$

$$I_{sc} = 0.1923A.$$

$$R_N = \frac{5}{0.1923} = 25.87\Omega$$

$$I_{10\Omega} = 0.1386A.$$

$$\therefore P_{10\Omega} = 0.192W.$$

Q.3 a)

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} \quad R_{TH} = R_L$$

b) - Initial values of voltage and current

- response of voltage & current
- initial conditions for R, L & C.c) condition of reciprocity for Y -parameters

$$Y_{12} = Y_{21}$$

condition of symmetry for Y -parameters

$$Y_{11} = Y_{22}$$

Q.4 a)

initially s/w is open $i(0) = 0 \therefore i(0^+) = 0$ at 0^+ s/w is closed, m acts as open

$$\therefore V_L(0^+) = 100V.$$

$$V_L = 0.1 \frac{d}{dt} (2 - 2e^{-500t})$$

for $t > 0$ apply KVL

$$100 = 50i + 0.1 \frac{di}{dt}$$

$$\frac{di}{dt} + 500i = 1000$$

$$\therefore i(t) = \frac{1000}{500} + Ke^{-500t}$$

$$\therefore i(0) = 0 \quad K = 2$$

$$\therefore i(t) = 2(1 - e^{-500t})$$

$$= 0.1(0 - 2e^{-500t}(-500))$$

$$V_L = 100e^{-500t}$$

04

Q.4 b) $i(0^-) = 0 \quad \therefore i(0^+) = 0$

for $t > 0$ apply KVL

$$5 = 2i + \frac{di}{dt}$$

$$5 = 2i(0^+) + \frac{di}{dt}(0^+)$$


$$\therefore \frac{di}{dt}(0^+) = 5 \text{ A/s.}$$

$$0 = 2 \frac{di}{dt} + \frac{d^2i}{dt^2}$$

$$= 2(5) + \frac{d^2i}{dt^2}$$

$$\therefore \frac{d^2i}{dt^2} = -10 \text{ A/s}^2$$

Q.5 a)

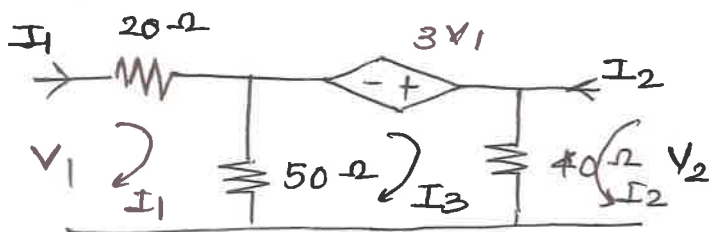

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$V_1 = 70I_1 - 50I_3 \quad \text{--- (1)}$$

$$V_2 = 40I_2 + 40I_3 \quad \text{--- (2)}$$

$$+50I_1 - 90I_3 - 40I_2 + 3V_1 = 0 \quad \text{--- (3)}$$

$$\frac{50I_1 - 40I_2 + 3V_1}{90} = I_3$$

$$V_1 = 70I_1 - 50 \left(\frac{50I_1 - 40I_2 + 3V_1}{90} \right)$$

$$= 70I_1 - \frac{2500I_1}{90} + \frac{2000I_2}{90} + \frac{150}{90}V_1$$

Q. No.

$$V_1 + \frac{150}{90} V_1 = \frac{3800}{90} I_1 + \frac{2000}{90} I_2$$

$$\frac{240}{90} V_1 = \frac{3800}{90} I_1 + \frac{2000}{90} I_2$$

$$V_1 = 15.83 I_1 + 8.33 I_2$$

$$V_2 = 40 I_2 + 40 \left(\frac{50 I_1 - 40 I_2 + 3 V_1}{90} \right)$$


$$= 40 I_2 + \frac{2000 I_1}{90} - \frac{1600}{90} I_2 + \frac{120}{90} V_1$$

$$= 40 I_2 + 22.22 I_1 - 17.77 I_2 + 1.33 (15.83 I_1 + 8.33 I_2)$$

$$V_2 = 33.33 I_2 + 43.27 I_1$$

$$Z = \begin{bmatrix} 15.83 & 8.33 \\ 43.27 & 33.33 \end{bmatrix}$$

b)

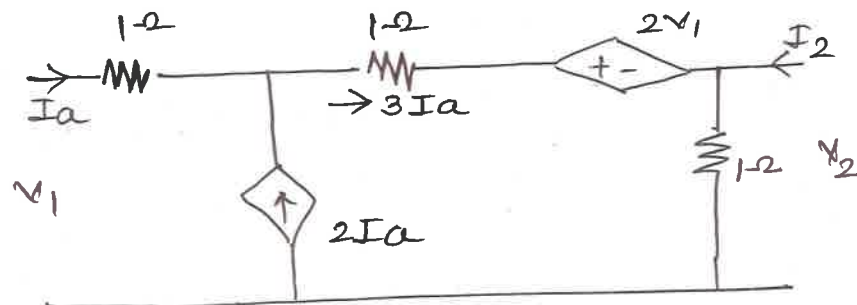

Applying KVL to outer loop

$$V_1 - I_a - 3I_a - 2V_1 - 3I_a = 0$$

$$V_1 = -7I_a$$

$$V_2 = 3I_a$$

$$\frac{V_2}{V_1} = -\frac{3}{7} \quad \therefore G_{21} = -\frac{3}{7}$$

Q. 6 a) circuit I

$$Z(s) = \frac{S(S^2 + 6S + 8)}{S^2 + 3S}$$

$$\begin{array}{r} S^2 + 3S \) \ S^3 + 6S^2 + 8S \ (S \\ \underline{S^3 + 3S^2} \\ 3S^2 + 8S \) \ S^3 + 3S^2 \ (S/3 \\ \underline{S^3 + 8S} \end{array}$$

$$Z(s) = \frac{3(S^2 + 6S + 8)}{S^2 + 3S}$$


$$\begin{array}{r} S^2 + 3S \) \ 3S^2 + 18S + 24 \ (3 \leftarrow Z(s) \\ \underline{3S^2 + 9S} \end{array}$$

$$\begin{array}{r} 9S + 24 \) \ S^2 + 3S \ (S/9 \leftarrow Y(s) \\ \underline{S^2 + 24S/9} \end{array}$$

$$\begin{array}{r} \frac{1}{3}S \) \ 9S + 24 \ (27 \leftarrow Z(s) \\ \underline{9S} \end{array}$$

$$\begin{array}{r} 24 \) \ \frac{1}{3}S \ (\frac{1S}{72} \leftarrow Y(s) \\ \underline{\frac{1}{3}S} \end{array}$$

$$\frac{0}{0}$$

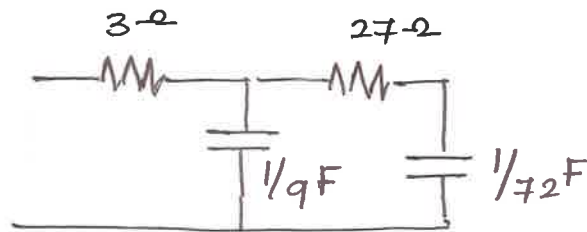

Q. No.

Q.6 b)

$$Z(s) = \frac{2s + s^3}{3 + 4s^2 + s^4}$$

$$\begin{array}{r} 3 + 4s^2 + s^4 \quad 2s + s^3 \left(\frac{2s}{3} \right) \\ \underline{2s + \frac{8}{3}s^3 + \frac{2}{3}s^5} \\ -\frac{5}{3}s^3 - \frac{2}{3}s^5 \end{array}$$


$$\therefore Y(s) = \frac{3 + 4s^2 + s^4}{2s + s^3}$$

$$\begin{array}{r} 2s + s^3 \quad 3 + 4s^2 + s^4 \left(\frac{3}{2s} \right) \leftarrow Y(s) \\ \underline{3 + \frac{3}{2}s^2} \end{array}$$

$$\begin{array}{r} \frac{5}{2}s^2 + s^4 \quad 2s + s^3 \left(\frac{4}{5s} \right) \leftarrow Z(s) \\ \underline{2s + \frac{4}{5}s^3} \end{array}$$

$$\begin{array}{r} \frac{1}{5}s^3 \quad \frac{5}{2}s^2 + s^4 \left(\frac{25}{2s} \right) \leftarrow Y(s) \\ \underline{\frac{5}{2}s^2} \end{array}$$
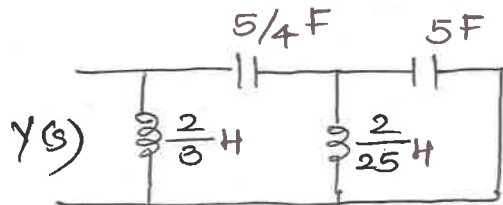
$$\begin{array}{r} s^4 \quad \frac{1}{5}s^3 \left(\frac{18}{5s} \right) \leftarrow Z(s) \\ \underline{\frac{1}{5}s^3} \\ 0 \end{array}$$



Q. 6 c) $\frac{s^2+1}{s^3+4s} \leftarrow$ even fun. $2s \frac{s^2+1}{2s} -$ Hurwitz. 08

$$P_1(s) = 3s^2 + 4$$

$$3s^2+4 \mid s^3+4s \quad (s/3)$$

$$\underline{s^3 + \frac{4}{3}s}$$

$$\frac{8}{3}s \mid 3s^2+4 \quad (9/8)$$

$$\underline{3s^2}$$

$$4 \mid \frac{8}{3}s \quad (\frac{2}{3}s)$$

$$\underline{\frac{8}{3}s}$$

$$0$$

\therefore Hurwitz.

$$F(s) = \frac{(s+j)(s-j)}{s(s^2+4)} = \frac{(s+j)(s-j)}{s(s+j2)(s-j2)}$$

poles at $s=0, s=-j2, s=+j2$

\therefore on jw axis.

\therefore residue test.

$$A = 1/4, B = 3/8, C = 3/8$$

residues are real & +ve

Even part $(s^2+1) \circledast$ odd part $(s^3+4s) \circ$

$\therefore A(\omega^2) \geq 0$ for all $\omega \geq 0$

$\therefore F(s)$ is P.R.F.