

**Questions should be —**  
**COMPUTER LASER PRINTED OR TYPED OR WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.**  
**SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,**  
**so as to avoid mistakes in the printed question papers.**

Questions should be written one below the other and in every front page only.

Duration ..... Hours. Total Marks assigned to the paper .....

Marks assigned to each question should be stated against each question.

**Instructions to the candidates, if any :—**



N.B. : Valid

- 1) ~~valid~~ Design steps other than given in the solutions can be considered right.
- 2) Suitable assumptions, ~~suitable~~ valid circuit diagrams, should be considered right.

Q. No.	Marks
--------	-------


Q-1-a. Class C Power amplifier.

Circuit diagram -

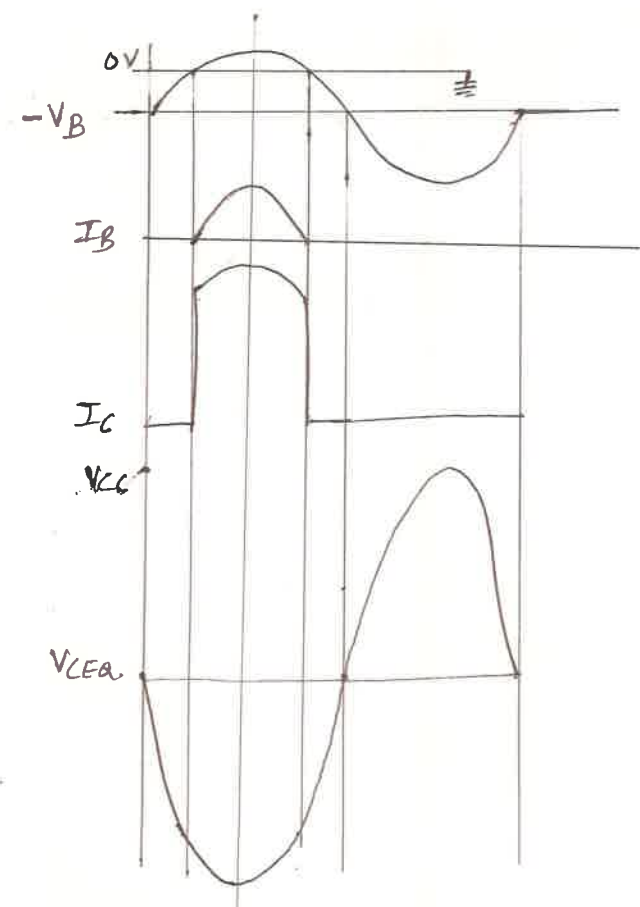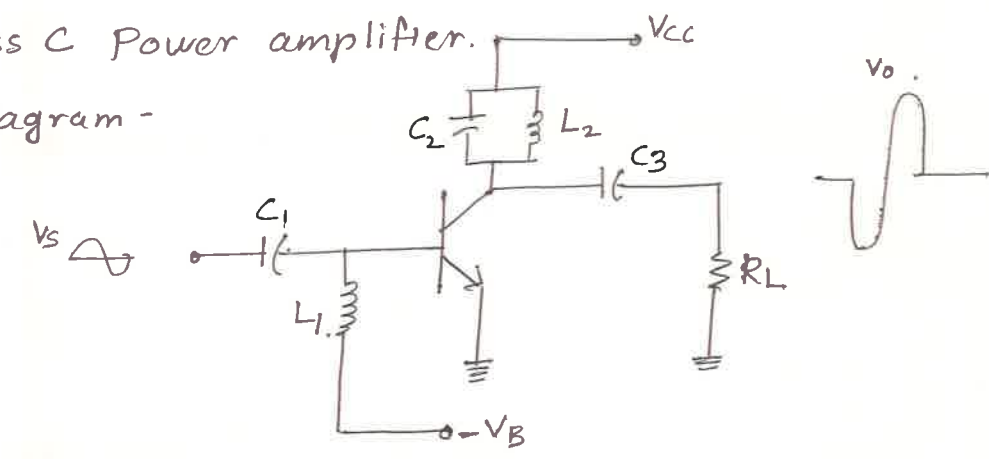

ckt - ① mark  
 w/f - ① mark  
 expl. - ③ marks.

Q-1-b. Current mirror circuit -

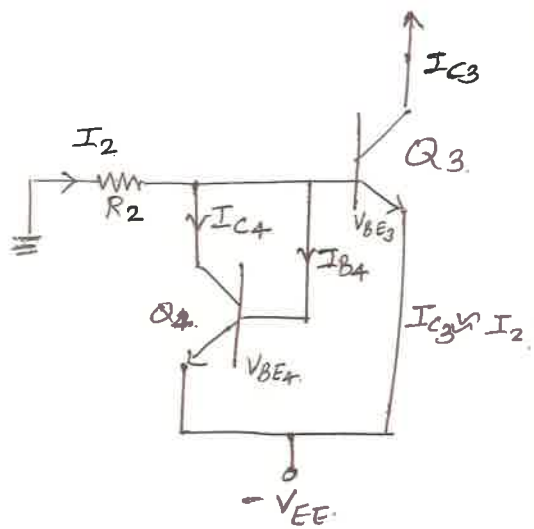

CKT dia - 02

$$V_{BE3} = V_{BE4}, \quad I_{C3} = I_{C4} \text{ \& } I_{B3} = I_{B4}$$

At node A ;

$$\begin{aligned} I_2 &= I_{C4} + I = I_{C4} + I_{B3} + I_{B4} \\ &= I_{C4} + 2I_{B4} \end{aligned}$$

$$\begin{aligned} \text{Also } I_2 &= I_{C3} + 2I_{B3} \\ &= I_{C3} + 2 \left( \frac{I_{C3}}{\beta} \right) \\ &= I_{C3} \left( 1 + \frac{2}{\beta_{dc}} \right) \end{aligned}$$

As  $\beta$  is large, 2<sup>nd</sup> term is neglected

$$\therefore I_2 \approx I_{C3} \approx \frac{V_{EE} - V_{BE3}}{R_2}$$

Q-1-c. Voltage series Conf<sup>n</sup>

- 1) other name
- 2) Block diagram
- 3) I/O signal.
- 4) Mixing signal
- 5) equivalent circuit.
- 6) Gain formulas.
- 7) comment on impedances.

Block diagram - (2) marks.

& Any ~~two~~ three are exp expected.

Voltage shunt Conf<sup>n</sup>

03

Q. No.

Q-1-d. S.R. =  $\omega V_{pk}$ .

For IC 741

$$f_{max} = \frac{S.R.}{2\pi V_{pk}}$$

$$= 7.95 \text{ KHz}$$

∴ 741 is not suitable.

For IC TL081

$$f_{max} = 206.9 \text{ KHz}$$

$f_{max}$  of 741 - ②

of TL081 - ②

Comment - ①

Q-2-a Step ① - selection of power transistor.  $\eta$   
Assume  $\eta = 80\%$  to  $90\%$   
&  $P_L = 5W$ .

$$n_T = \frac{P_L}{P_L'}$$

step ②  $P_D(\text{max}) = 2 P_L'$

Select Power transistor having  $P_D(\text{max}) > \text{required}$ .

step ③ -  $V_{RE}$  Calculation of  $R_E$  -

$$R_E = \frac{V_{RE}}{I_{CQ}} = \frac{15\% V_{CC}}{I_{CQ}}$$

$$R_L' = \frac{[V_{CC} - V_{CE(\text{sat})}]^2 \times \eta}{2 \times P_L}$$

step ④ -  $S = 1 + \frac{R_{Th}}{R_E}$

$$\therefore \frac{R_{Th}}{R_E} = S - 1$$

Assume  $R_2 \ll R_1 \Rightarrow R_2 \approx R_{Th}$ .

$$V_{BQ} = V_{R_2} = V_{BE} + V_{RE}$$

$$V_{R_2} = V_{CC} \frac{R_2}{R_1 + R_2}$$

Calculate  $R_1$  &  $R_2$ .

step ⑤ -  $\frac{N_1}{N_2} = \sqrt{\frac{R_L'}{R_L}}$

Calculate  $N_1 : N_2$


Q. No.

Step ④ - 
$$\eta = \frac{P_o(ac)}{P_i(dc)}$$

Note  $\eta$  should be less than 50%.  
 All resistor's power ratings should be calculated.  
 Diagram with values should be shown in the ans.


Q-2-b. eq<sup>n</sup> is  $V_o = -2V_1 - 4V_2 - 6V_3$ .

∴ INV. adder will be used.

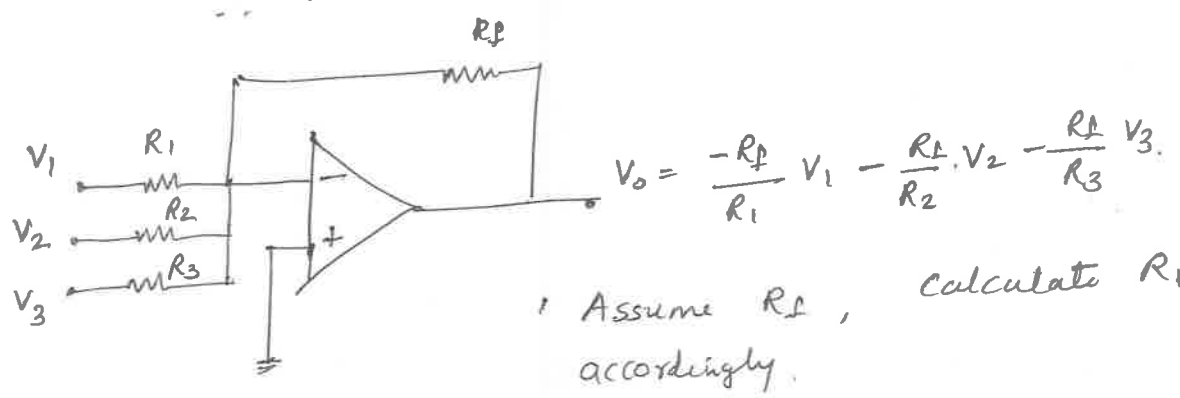

Assume  $R_f$ , calculate  $R_1, R_2, R_3$  accordingly.

Q-2-c. Sample & hold circuit -

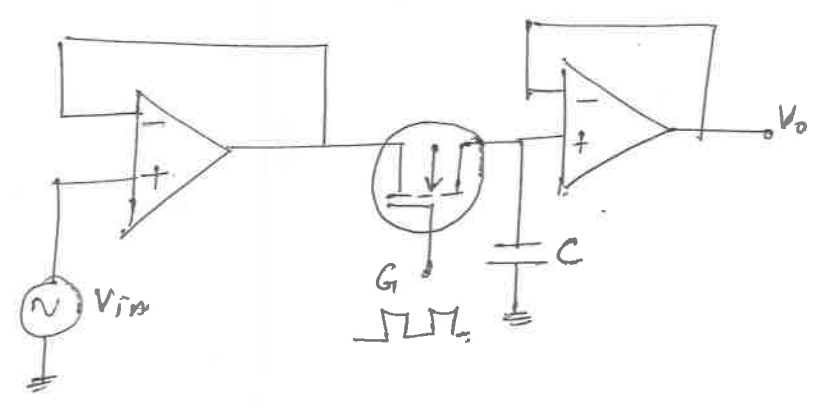

06

Q. No.

$$A_I = \frac{I_o}{I_s} = \frac{-I_{c2}}{I_s}$$

$$= \frac{-I_{c2}}{I_{b2}} \times \frac{I_{b2}}{I_{c1}} \times \frac{I_{c1}}{I_{b1}} \times \frac{I_{b1}}{I_s}$$

$$= h_{fe} \times \frac{I_{b2}}{I_{c1}} \times h_{fe} \times \frac{I_{b1}}{I_s}$$

$$\text{Now } \frac{I_{b2}}{I_{c1}} = \frac{h_{fe} \cdot I_{b1} \times \frac{R_{c1}}{R_{c1} + R_{i2}}}{I_{c1}} = \frac{R_{c1}}{R_{c1} + R_{i2}}$$

$$\& \frac{I_{b1}}{I_s} = \frac{I_s \cdot R_s \parallel (R_F + R_e)}{[R_s \parallel (R_F + R_e)] + h_{ie}} = \frac{R_s \parallel (R_F + R_e)}{R_s \parallel (R_F + R_e) + h_{ie}}$$

Now

$$\therefore R_{i2} = h_{ie} + (1 + h_{fe})(R_e \parallel R_F)$$

$$= 1k + [(1 + 50)(500 \parallel 1000)] = 3.42k$$

$$\therefore A_I = h_{fe} \times \left( \frac{3k}{3k + 3.42k} \right) \times h_{fe} \times \frac{1k \parallel (1k + 500\Omega)}{[1k \parallel \{(1k + 500\Omega)\} + 1k]}$$

$$= 50 \times 50 \times 0.467 \times \frac{512.10}{1512.2}$$


$$= 395$$

$$D = 1 + B \cdot A_I = 1 + (0.047) \times 395 = 19.565$$

$$\frac{1000 \times 1050}{1000 + 1050}$$

$$\frac{1000 \times 1050}{1000 + 1050} + 1k$$


Q. No.  
Q-3-A.

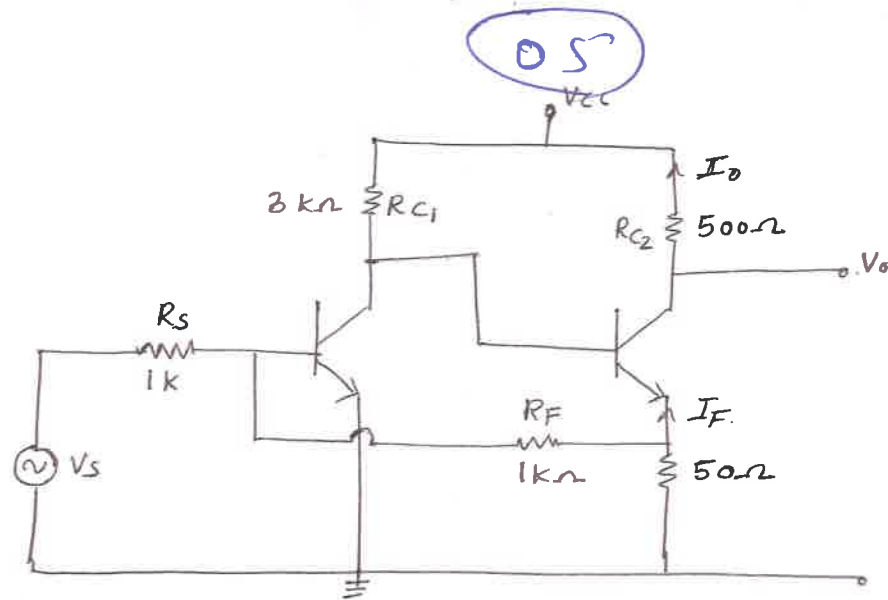


Page No..... 5

Marks

Amplifier without feedback -

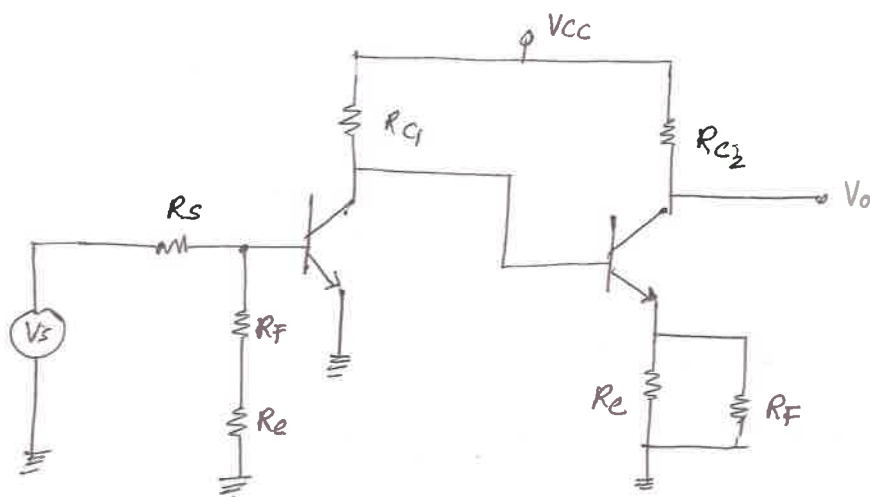

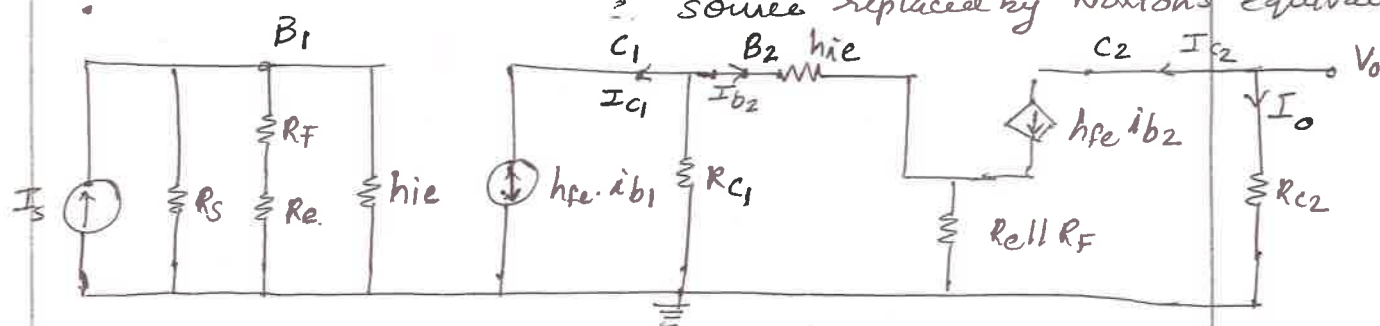Equivalent circuit: - Type - Current shunt (or shunt Series)  
= source replaced by Norton's equivalent



$$\beta = \frac{I_f}{I_o} = \frac{I_o \cdot \frac{R_e}{R_e + R_F}}{I_o} = \frac{R_e}{R_e + R_F}$$

$$= \frac{50\Omega}{50 + 1k} = 0.047$$

07

Page No. .... 7

Marks

Q. No.

$$A_{IF} = \frac{A_I}{D} = \frac{395}{19.8} = 19.94$$

$$A_{VF} = \frac{V_o}{V_s} = \frac{-I_{C2} \cdot R_{C2}}{I_s \cdot R_s} = \frac{A_{IF} \cdot R_{C2}}{R_s}$$

$$= \frac{19.94 \times 500}{1000}$$

$$= 9.97$$

$$R_i = [R_s \parallel (R_F + R_e)] \parallel h_{ie}$$

$$= [1000 \parallel (1000 + 50)] \parallel 1000$$

$$= 338.7 \Omega$$

$$R_{IF} = \frac{R_i}{D}$$

$$= \frac{338.7}{19.8}$$

$$= 17.1 \Omega$$

Q. No.

Integrator ckt.


Q-3-b.

$$R_1 = 500 \Omega, R_f = 5k, C = 0.1 \mu F.$$

Period of i/p sig = 0.5 ms.

Find  $f_a$  &  $f_b$ 

Marks

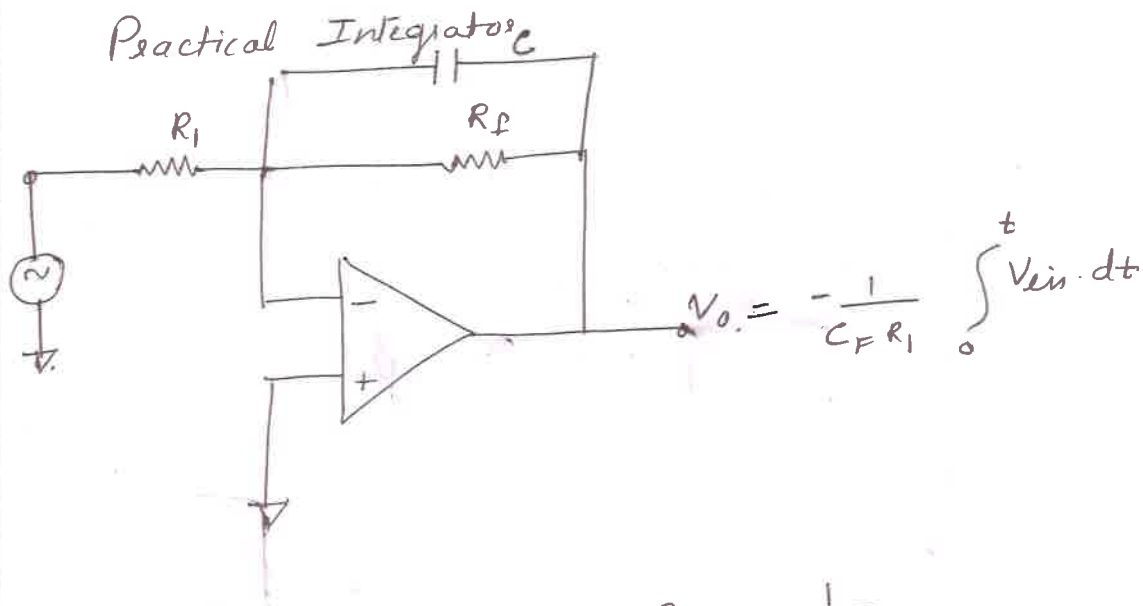

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$= \frac{1}{2 \times \pi \times 5k \times 0.1 \times 10^{-6}}$$

$$= \frac{1}{3.14 \times 10^{-3}}$$


$$= 0.32 \text{ kHz}$$

$$f_b = \frac{1}{2\pi R_1 C_f}$$

$$= \frac{1}{2\pi \times 500 \times 0.1 \times 10^{-6}}$$

$$= \frac{1}{314.15 \times 10^{-6}}$$


$$= 3.18 \text{ MHz}$$

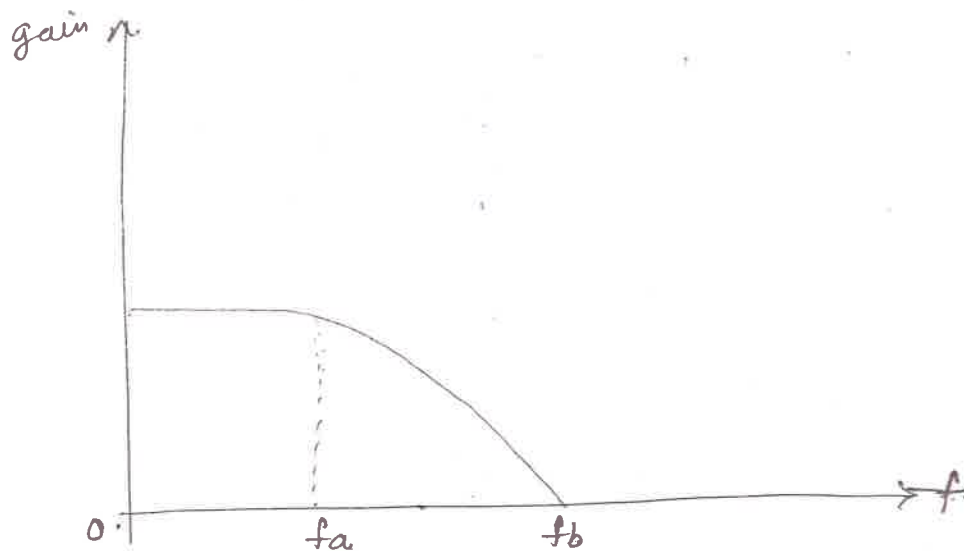



Q. No. Q-3-C. Logarithmic amplifier -

Marks

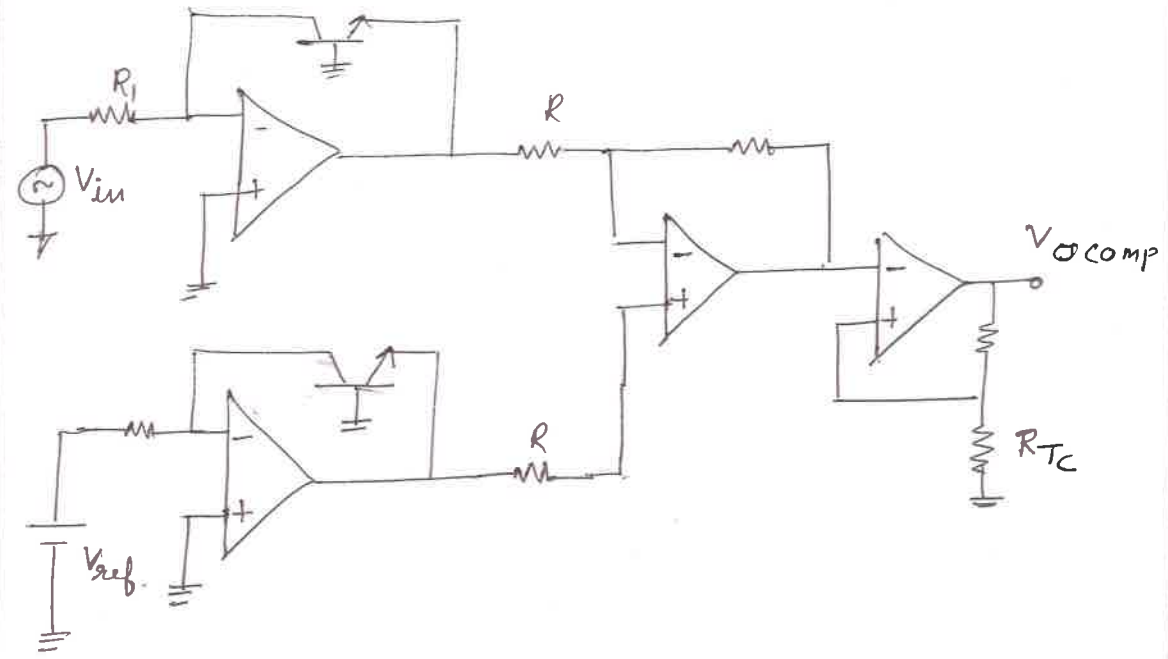

$$V_1 = -n V_T \ln \left[ \frac{V_{in}}{R_1 I_0} \right]$$

$$V_2 = -n V_T \ln \left[ \frac{V_{ref}}{R_1 I_0} \right]$$


$$\therefore V_0 = V_2 - V_1 = n V_T \ln \left[ \frac{V_{in}}{V_{ref}} \right]$$

The temp variations are compensated by last stage op-amp whose gain =  $1 + \frac{R_2}{R_{TC}}$ .

Q. No.

Q-4 (a)

Wein Bridge Osc<sup>r</sup>

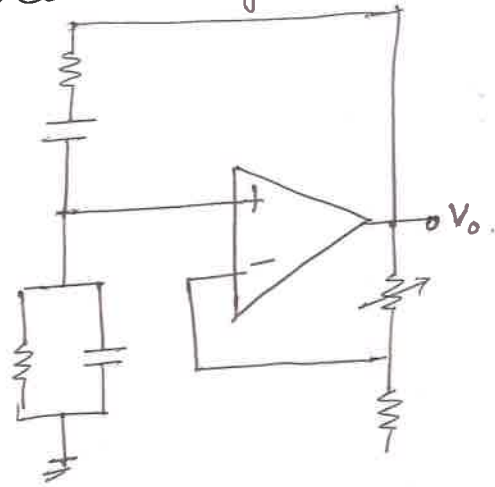

Marks

Diagram - (2)  
 Explanation - (2)

Derivation for frequency - 3  
 of osc<sup>r</sup> =  $f_0 = \frac{1}{2\pi RC}$   
 & condition for oscillations - 3  
 $A_v = \frac{1}{\beta}$

Q-4 (b)  $\theta_{dev-case} = 1.75^\circ C/W$      $\theta_{case-sink} = 1^\circ C/W$   
 $\theta_{sink-amb} = 5^\circ C/W$      $\theta_{case-amb} = 50^\circ C/W$

$T_A =$  ambient Temp =  $30^\circ C$  ,  $T_{j(max)} = 120^\circ C$

~~$P_{D(max)} = \frac{T_{j(max)} - T_A}{\theta_{JA(max)}}$~~

Considering design for 50W power dissipation

~~$50 = \frac{120 - 30}{\theta_{JA(max)}}$~~

~~$\therefore \theta_{JA(max)} = \frac{90}{50} = 1.8^\circ C/W$~~

~~$\therefore P_{D(max)} = \frac{T_j - T_A}{\theta_{JA(max)}}$~~


But  $\theta_{JA(max)} = \theta_{CA} + \theta_{jc} = 50 + 1.75 = 51.75$

$P_{D(max)} = \frac{120 - 30}{51.75} = 1.73 W$  (Without heat sink)

Now with heat sink,

$P_{D(max)} = \frac{T_j(max) - T_A}{\theta_{jc} + \theta_{cs} + \theta_{SA}}$   
 $= \frac{90}{1.75 + 1 + 5} = 11.61 W$

Marks

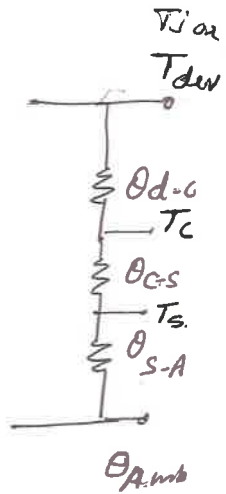

Q. No.


Q-4-C

Advantages of -ve fb. (Any 5 or if 3 with explanation is accepted)

- 1) Stabilization of gain
- 2) Reduction in frequency distortion
- 3) Reduction in nonlinear distortion
- 4) Reduction in noise
- 5) Increases bandwidth
- 6) Increases input impedance
- 7) Reduces output impedance

Q-5-a

3 op-amp Instrumentation amp<sup>s</sup>

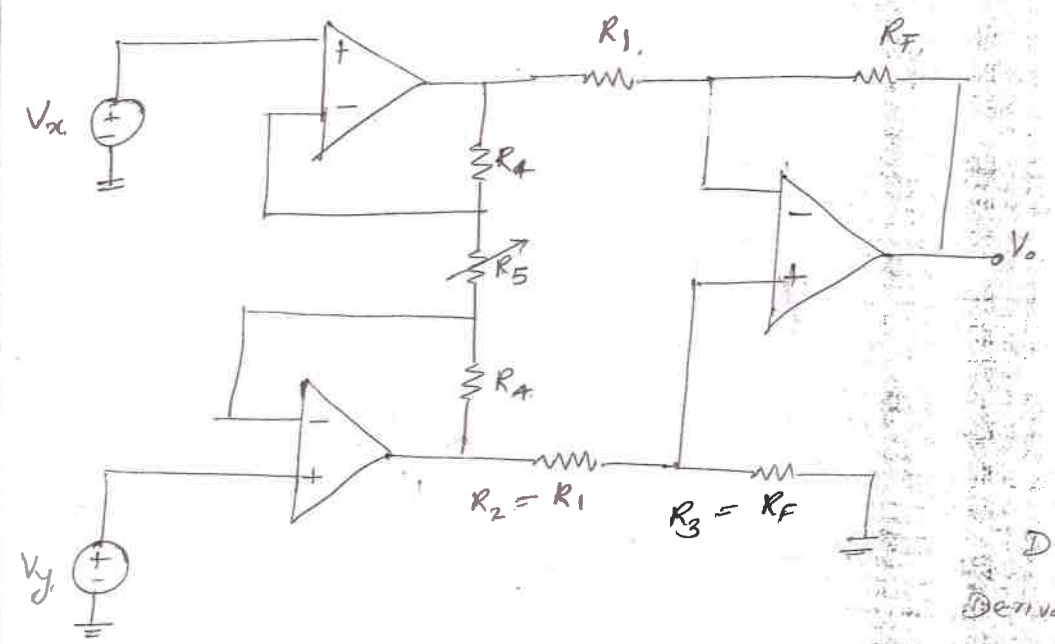

$$A_D = - \left( 1 + \frac{2R_4}{R_5} \right) \left( \frac{R_F}{R_1} \right)$$

Dia - (2)  
 Derivation - (4)  
 Char / Specification - (2)  
 Appl<sup>n</sup> - (2)

Questions should be —  
 WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.  
 SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,  
 so as to avoid mistakes in the printed question papers.

Duration ..... Hours.

Total Marks assigned to the paper .....

Q. No.

N.B. :

Marks

Q-5-b - CMRR - Common Mode Rejection Ratio -  
 It is the ability of the op-amp to reject common mode signals.

Ideal value =  $\infty$  , prac = 90 dB.


Slew rate - It is the rate of change of o/p voltage w.r.t. time at const i/p volt.

Ideal =  $\infty$  prac 0.5 V/ $\mu$ s.

i/p offset volt = It is the <sup>i/p</sup> voltage that should be applied between 2 i/p terminals to null the o/p.

Ideal = 0 prac - 6 mV.

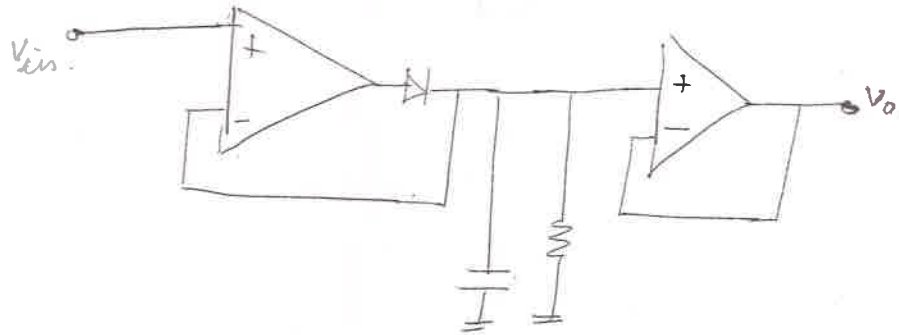Q-5-c. Peak detector circuit - (INV or NINV any conf<sup>n</sup>).



Questions should be —

WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.  
SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,  
so as to avoid mistakes in the printed question papers.


Duration ..... Hours.

Total Marks assigned to the paper .....

Q. No.

Q-6-a.

N.B.:

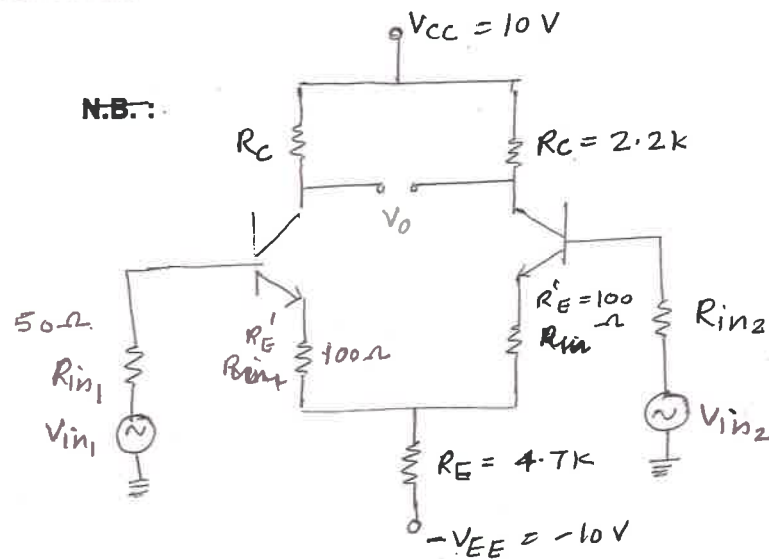

Marks

$$I_{CQ} = I_E = \frac{V_{EE} - V_{BE}}{2R_E + R_E' + R_{in}/\beta} = \frac{10 - 0.715}{2 \times 4.7k + 100 + \frac{50}{100}} = 0.977 \text{ mA}$$

$$V_{CEQ} = V_{CC} + V_{BE} - I_{CQ} \cdot R_C = 10 + 0.715 - 0.977 \times 10^{-3} \times 2.2 \times 10^3 = 8.56 \text{ V}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26}{0.977 \text{ mA}} = 25.6 \Omega$$

$$A_d = \frac{R_C}{r_e + R_E'} = \frac{2.2 \times 10^3}{25.6 + 100} = 17.52$$

$$R_i = 2\beta(r_e + R_E') = 2 \times 100 \times (25.6 + 100) = 25.12 \text{ k}\Omega$$

(14)

**Questions should be —**  
**WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.**  
**SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,**  
**so as to avoid mistakes in the printed question papers.**

Duration ..... Hours.

Total Marks assigned to the paper .....

Q. No.

Marks

Q-6-b

N.B. :

$$\text{Design } V_o = - \int V_{in} \cdot dt$$

$$\text{For an integrator } V_o = - \frac{1}{R_F C_F} \int_0^t V_{in} \cdot dt + C$$

$$1. \frac{1}{R_F C_F} = 1$$

$$\text{Let } R_F = 10 \text{ K}$$

$$\therefore C_F = \frac{1}{10 \times 10^3} = 0.1 \text{ mF}$$

$$f_c = \frac{1}{2\pi R_F C_F} = \frac{1}{2\pi \times 10 \text{ K} \times 0.1 \text{ mF}} = 0.159 \text{ MHz}$$

$$f_b = \frac{1}{2\pi R_1 C_F}$$

$$\text{Let } R_1 = f_b = 10 \text{ fa.}$$

$$\therefore f_b = 1.59$$

$$1.59 = \frac{1}{2\pi R_1 \times 0.1 \text{ mF}}$$

$$\therefore R_1 = \frac{1}{1.59 \times 2 \times \pi \times 0.1 \text{ mF}}$$

$$= 1 \text{ K}\Omega$$


Q. No.  
Q-6-C

Schmitt trigger. - (NINV or INV. anyone).

CKT dia. - 1. marks.

threshold points - with explanation - 2 marks.

waveforms - 2

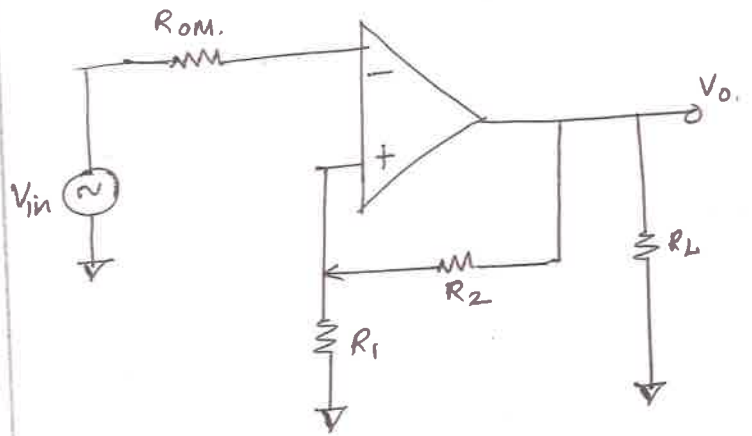

$$V_{ut} = \frac{R_1}{R_1 + R_2} (+V_{sat})$$

$$V_{lt} = \frac{R_1}{R_1 + R_2} (-V_{sat})$$

$$V_{hysteresis} = \frac{R_1}{R_1 + R_2} [V_{sat} - (-V_{sat})]$$

