

Q. 4b)

EPS

①

37871

Ⓐ

$$K = \frac{\text{shunt } C}{\text{self } C} = 0.11$$

$$V_{tg} \text{ across string, } V = 33/\sqrt{3} = 19.05 \text{ kV}$$

at junction A,

$$\begin{aligned} V_2 &= V_1(1+K) \\ &= V_1(1+0.11) \\ V_2 &= 1.11 V_1 \end{aligned}$$

at junction B, $I_3 = I_2 + i_2$

$$\begin{aligned} V_3 &= V_2 + (V_1 + V_2)K \\ V_3 &= 1.342 V_1 \end{aligned}$$

i) V_{tg} across whole string is,

$$\begin{aligned} V &= V_1 + V_2 + V_3 \\ &= V_1 + 1.11 V_1 + 1.342 V_1 = 3.452 V_1 \\ 19.05 &= 3.452 V_1 \end{aligned}$$

$$\therefore V_1 = 19.05 / 3.452 = \underline{5.52 \text{ kV}}$$

$$V_2 = 1.11 V_1 = 1.11 \times 5.52 = 6.13 \text{ kV}$$

$$V_3 = 1.342 V_1 = 1.342 \times 5.52 = 7.4 \text{ kV}$$

$$\text{i) String } \eta = \frac{19.05}{3 \times 7.4} \times 100 = 85.8 \%$$

$$= \underline{\underline{85.8 \%}}$$

02

$$110 = \frac{2 \times 1000}{2 \times 110}$$

110 = 2000 / 110

A solution is

$$110 = 2000 / 110$$

$$110 = 2000 / 110$$

$$110 = 2000 / 110$$

110 = 2000 / 110

$$110 = 2000 / 110$$

$$110 = 2000 / 110$$

110 = 2000 / 110

$$110 = 2000 / 110$$

$$110 = 2000 / 110$$

$$110 = 2000 / 110$$

110 = 2000 / 110

$$110 = 2000 / 110$$

$$110 = 2000 / 110$$

110 = 2000 / 110

$$110 = 2000 / 110$$

$$110 = 2000 / 110$$

Q.3 (b)

03

A

$$\text{Total R/ph, } R = 0.1 \times 100 = 10 \Omega$$

$$\text{Total X/ph, } X_L = 0.2 \times 100 = 20 \Omega$$

$$\text{cap. } Y = 0.04 \times 10^{-4} \times 100 = 4 \times 10^{-4} \text{ S}$$

$$V_R = \frac{10,000 \times 10^3}{\sqrt{3} \times 66 \times 10^3 \times 0.8} = 109 \text{ A}$$

$$\cos \phi_R = 0.8; \sin \phi_R = 0.6$$

$$\vec{Z} = R + jX_L = 10 + j20$$

i) Taking receiving end vtg as ref phasor

$$\text{R end vtg, } \vec{V}_R = V_R + j0 = 38,105 \text{ V}$$

$$\vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R)$$

$$= 109 (0.8 - j0.6) = 87.2 - j65.4$$

$$\vec{V}_1 = \vec{V}_R + \vec{I}_R \vec{Z} / 2$$

$$= 38105 + (87.2 - j65.4) (5 + j10)$$

$$= 39195 + j545$$

$$\vec{I}_C = jY \vec{V}_1 = j4 \times 10^{-4} (39195 + j545) = -0.218 + j15.6$$

$$\text{Send. end } \vec{I}, \vec{I}_S = \vec{I}_R + \vec{I}_C = (87.2 - j65.4) + (-0.218 + j15.6)$$

$$= 100 \angle -29^\circ 47' \text{ A}$$

$$\therefore \text{Send. end } I = \underline{100 \text{ A}}$$

$$\text{ii) } \vec{V}_S = \vec{V}_1 + \vec{I}_S \vec{Z} / 2$$

$$= (39195 + j545) + (100 \angle -29^\circ 47') (5 + j10)$$

$$= 40145 \angle 1^\circ 40' \text{ V}$$

$$\text{Line value of send. end vtg, } = 40145 \times \sqrt{3} = 69533 \text{ V}$$

$$\text{iii) Ref. to ph. dig } \phi_1 = 1^\circ 40', \phi_2 = 29^\circ 47'$$

$$\phi_S = \phi_1 + \phi_2 = 31^\circ 27'$$

$$\therefore \text{Send. end pf} = \cos \phi_S = \cos 31^\circ 27' = 0.853 \text{ lag}$$

$$\begin{aligned}
 \text{iv) send-end power} &= 3 V_s I_s \cos \phi_s \\
 &= 3 \times 40145 \times 100 \times 0.853 \\
 &= 10273105 \text{ W} = 10273.105 \text{ kW}
 \end{aligned}$$

$$\text{Power delivered} = 10,000 \text{ kW}$$

$$\therefore \text{X'm } \eta = \frac{10,000}{10273.105} \times 100 = \underline{\underline{97.34\%}}$$