

Questions should be —  
WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.  
SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,  
so as to avoid mistakes in the printed question papers.

Duration ..... 03 Hours.



Total Marks assigned to the paper ..... 80

Q. No.

Marks

Q-1 @

N.B. :

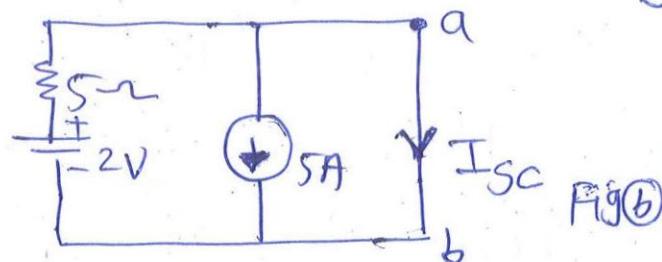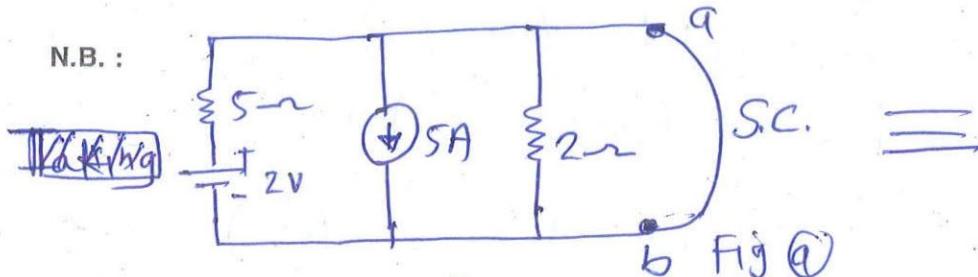

Taking first 2 volt source in fig (b)

$$2 = 5 \times I_{Sc}' \therefore I_{Sc}' = \frac{2}{5} = 0.4 \text{ Amp}$$

(2m)

Taking 5 A current source only in fig (b)

$$I_{Sc}'' = -5 \text{ Amp}$$

$$\therefore I_{Sc} = I_{Sc}' + I_{Sc}'' = -4.6 \text{ Amp}$$

(1m)

To find  $R_{ab}$ , the constant source are deactivated in fig (a)

$$\therefore R_{ab} = \frac{5 \times 2}{5+2} = 1.43 \Omega$$


(1m)

Norton's eq. Ckt is shown in fig. (c)



(1m)

Total = 5m

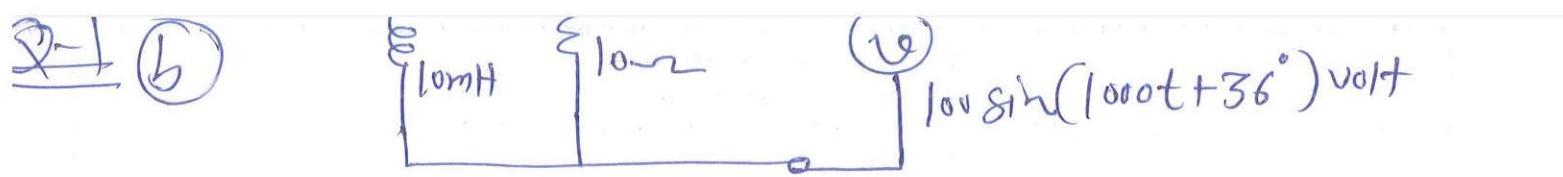

$$\begin{aligned}
 I_R &= \frac{V_m}{R} \sin(1000t + 36^\circ) \\
 &= 10 \sin(1000t + 36^\circ) \\
 &= 10 \cos(1000t - 54^\circ) \text{ Amp} \quad \text{--- (1)} \tag{1M}
 \end{aligned}$$

$$\begin{aligned}
 I_L &= \frac{V_m}{WL} \sin(1000t + 36^\circ - 90^\circ) \\
 &= 10 \sin(1000t - 54^\circ) \\
 &= 10 \cos(1000t - 144^\circ) \quad \text{--- (2)} \tag{1M}
 \end{aligned}$$

From eqn (1) and (2), RMS value of Current are

$$\begin{aligned}
 I_R &= 10 \angle -54^\circ \\
 I_L &= 10 \angle -144^\circ \\
 \therefore \text{Net RMS Current, } I &= I_R + I_L \tag{1M}
 \end{aligned}$$

$$\begin{aligned}
 \therefore I &= 10 \angle -54^\circ + 10 \angle -144^\circ \\
 &= 10(\cos 54^\circ - j \sin 54^\circ) + 10(\cos(-144^\circ) + j \sin(-144^\circ)) \\
 &= 5.88 - j 8.1 - 8.1 - j 5.88
 \end{aligned}$$


$$I =$$

2M  
Total = 5M

Q. No.

Page No. ....

Marks

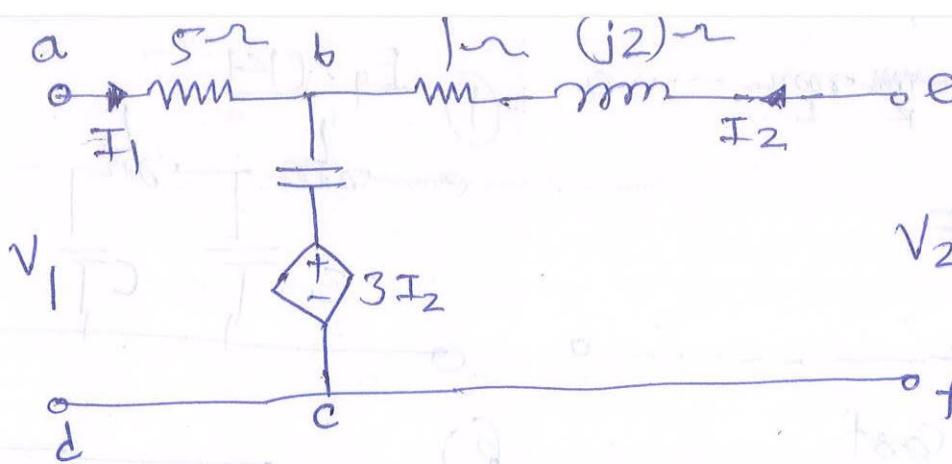Q10

Applying KVL to loop abcd in above fig.

$$V_1 = 5I_1 - j5I_1 + 3I_2 + (-j5I_2)$$

$$V_1 = (5-j5)I_1 + (3-j5)I_2 \rightarrow \textcircled{1} \quad 2M$$

Apply KVL to loop bcfc,

$$I_2(1+j2-j5) + I_1(-j5) + 3I_2 - V_2 = 0$$



$$\therefore V_2 = (-j5)I_1 + (4-j3)I_2 \rightarrow \textcircled{2} \quad 2M$$

Writing eqn \textcircled{1} and \textcircled{2} in matrix

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5-j5 & 3-j5 \\ -j5 & 4-j3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\therefore [Z]_{\text{matrix}} = \begin{bmatrix} 5-j5 & 3-j5 \\ -j5 & 4-j3 \end{bmatrix} \quad 1M$$

Total 5M

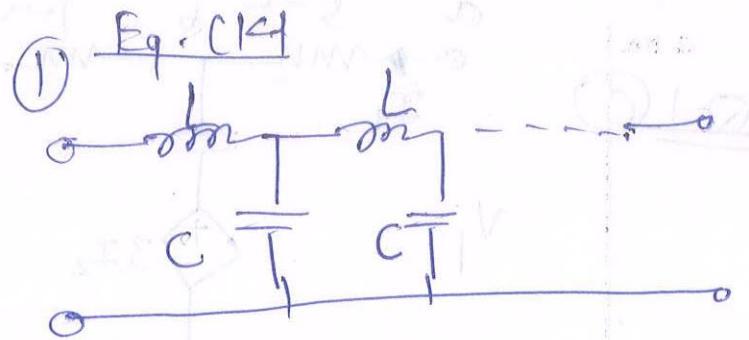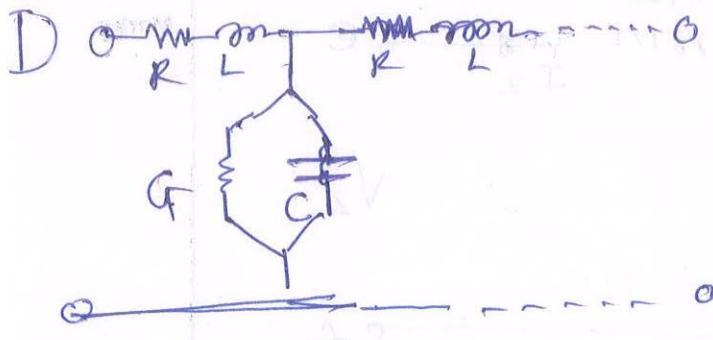

### 2) Propagation Cost

$$\gamma = \sqrt{ZY} = \sqrt{(R+jwL)(G+jwC)}$$

Attenuation Constant

$$3) \gamma = \alpha + j\beta$$

$$\therefore \alpha \neq 0$$

### 4) Characteristic Impd

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R+jwL}{G+jwC}}$$

$Z_0$  = Complex

### 5) Input Impedance

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_0 \tan \beta l}$$

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_0 \tan \beta l}$$

where,

$Z_0$  = Complex form

$$\gamma = \alpha + j\beta, \alpha \neq 0$$

②

$$\gamma = \sqrt{jwL \times jwC}$$

$$\gamma = jw \sqrt{LC} = \omega \sqrt{LC}$$

$$\therefore \beta = \lambda \sqrt{LC}$$

③  $\gamma = \alpha + j\beta$

$$\therefore \alpha = 0, \beta = \omega \sqrt{LC}$$

④

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{jwL}{jwC}} = \sqrt{\frac{L}{C}}$$

$$Z_0 = \text{real}$$

⑤


$$Z_L + jZ_0 \tan \beta l$$

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_0 \tan \beta l}$$

where  $Z_0$  = real form

$$\therefore \alpha = 0 \\ \therefore \gamma = j\beta$$

1 Mark for each point : Total = 5M

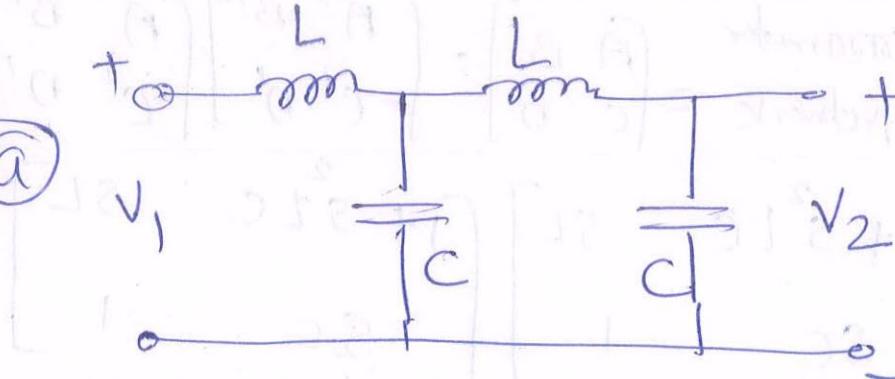Q2@

Writing in S domain and splitting —

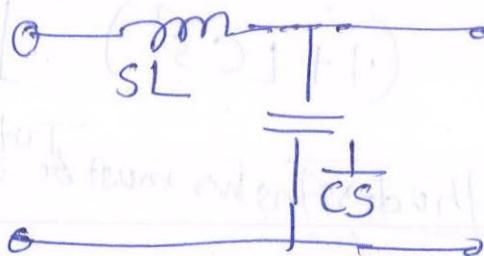


Fig @


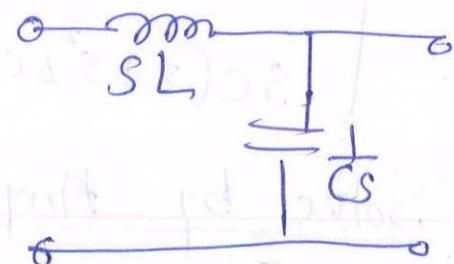


Fig b

Again splitting fig @ into —

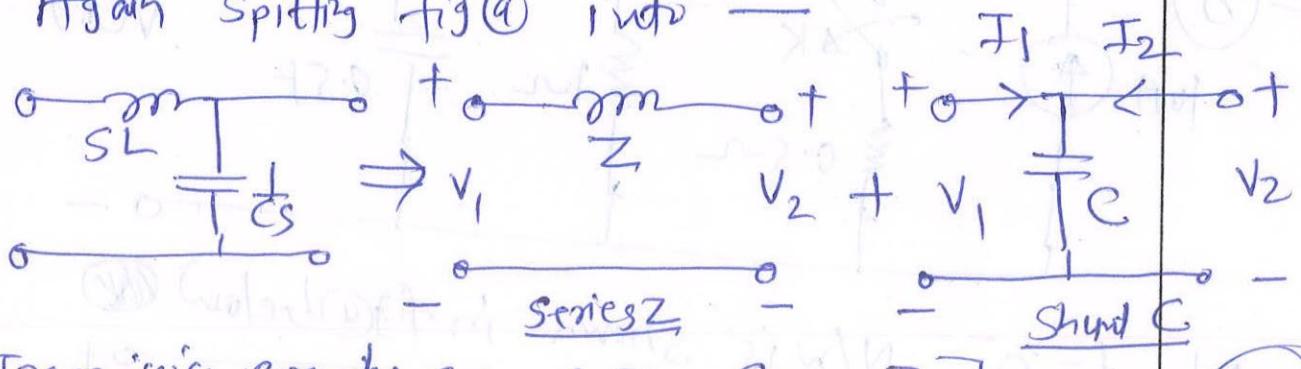

Transmission parameters

of Series Z

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

2M

Transmission para.

of shunt C

$$\begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

$$\begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$


$$= \begin{bmatrix} 1 & LS \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ CS & 1 \end{bmatrix} = \begin{bmatrix} 1 + SLC & SL \\ SC & 1 \end{bmatrix}$$

6M


$$\begin{aligned}
 & A' B' C' D' \text{ parameter} \\
 \text{of entire network} &= \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} A & B' \\ C' & D' \end{bmatrix} \\
 &= \begin{bmatrix} 1+s^2 LC & SL \\ SC & 1 \end{bmatrix} \begin{bmatrix} 1+s^2 LC & SL \\ SC & 1 \end{bmatrix} \\
 &= \begin{bmatrix} 1+3LCs^2 + L^2C^2s^4 & SL(2+s^2LC) \\ SC(2+s^2LC) & (1+LCs^2) \end{bmatrix}
 \end{aligned}$$

(2M)

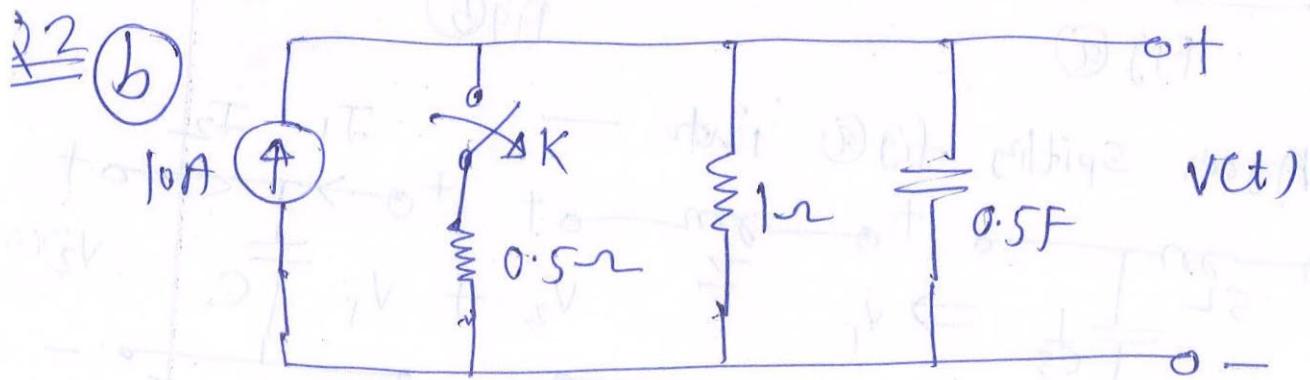OR Solve by Any method  $\rightarrow$  Answer must be same Total = 10m



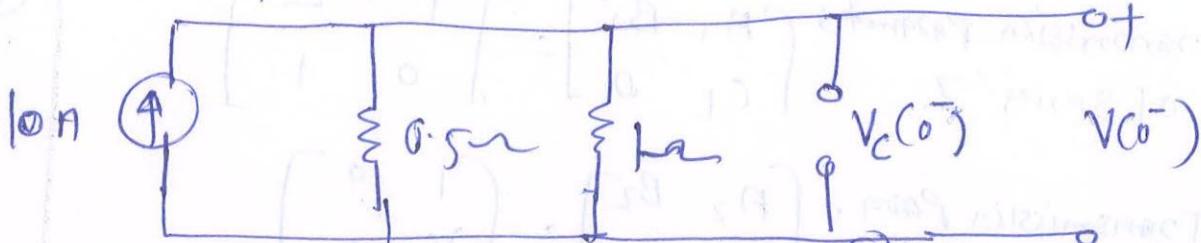At  $t=0^-$ , N/w is shown in fig @ below



At  $t=0^-$ , the network attains Steady state condition  
and hence capacitor  $C$  acts as  $0/\text{C}$

$$V_c(0^-) = 0$$

(2M)

Writing the KCL at  $t=0^-$  for above fig @

$$\frac{V(0^-)}{1} + \frac{V(0^-)}{0.5} = 10$$

$$\therefore V(0^-) = 3.33 \text{ volt}$$

Q. No.

Marks

Since the voltage across Capacitor Cannot Change Instantaneously

$$V_C(0^+) = V(0^+) = 3.33 \text{ volt}$$

For  $t > 0$ , the network is shown in fig (b) below

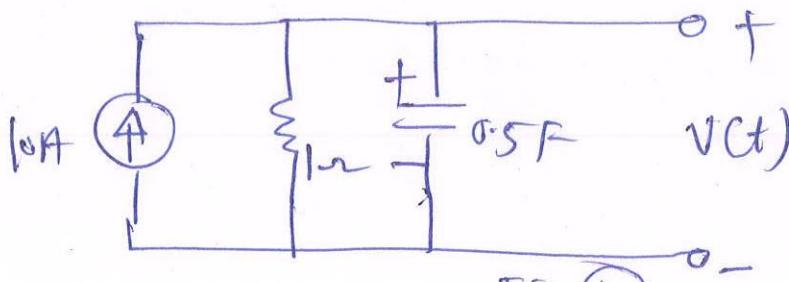


Fig (b)

Writing KCL for  $t > 0$

$$0.5 \cancel{\frac{dV}{dt}} + V = 10$$

$$\therefore \frac{dV}{dt} + 2V = 20 \quad \text{--- (1)}$$

Comparing with differential eqn  $\frac{dV}{dt} + PV = Q$

$$P=2 \quad Q=20$$

The solution of eqn (1) is given by -

$$\begin{aligned} V(t) &= e^{-Pt} \int Q e^{Pt} dt + K e^{-Pt} \\ &= e^{-2t} \int 20 e^{-2t} dt + K e^{-2t} \end{aligned}$$

$$V(t) = \frac{20}{2} + K e^{-2t} = 10 + K e^{-2t}$$

$$\text{At } t=0, V(0) = 3.33 \text{ volt}$$

$$\therefore 3.33 = 10 + K \therefore K = 6.67$$

$$\boxed{V(t) = 10 + 6.67 e^{-2t}}$$

(2m)


(3m)

(3m)

Total 10M



~~Q-3~~  
①

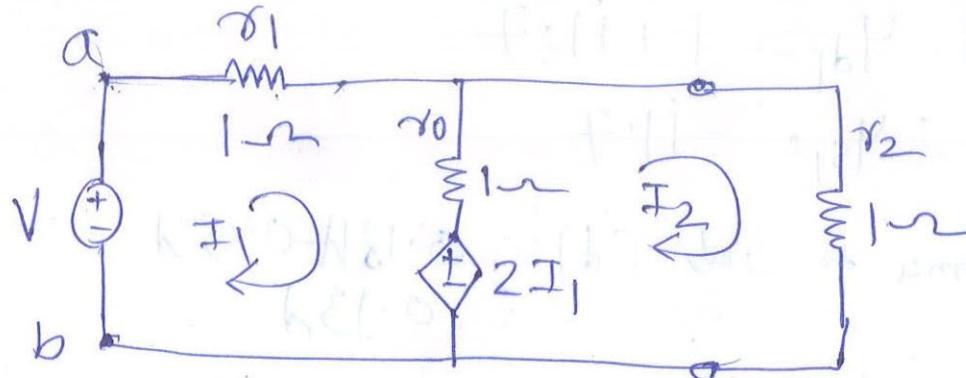

\* Left terminal a-b be O/C of above fig.  
This leads to  $I_1 = 0$ , also, dependent voltage source  $2I_1 = 0 \therefore I_2 = 0 \therefore V_{ab} = V_{oc} = 0$

\* Now apply DC voltage source  $V_{dc}$  across ab such that  $I_{lp}$  cannot be  $I_1$  at terminal a.  
Applying KVL at the left loop ( $I_1$ ) under this condition-

$$V_{dc} = I_1 r_1 + I_1 r_0 - I_2 r_0 + 2 I_1$$

$$V_{dc} = r_1 I_1 + r_0 (I_1 - I_2) + 2 I_1 \quad \left. \right\}$$

Applying KVL to the outer loop } - ①

$$V_{dc} = r_1 I_1 + r_2 I_2$$

$$\text{Put } r_0 = r_1 = r_2 = 1 \text{ in eqn } ①$$

$$V_{dc} = 4 I_1 - I_2 \quad \text{--- } ②$$

$$V_{dc} = I_1 + I_2 \Rightarrow I_2 = V_{dc} - I_1 \quad \text{--- } ③$$

Put eqn ③ in eqn ②

$$V_{dc} = 4 I_1 - V_{dc} + I_1$$

$$\therefore 2 V_{dc} = 5 I_1$$

$$\therefore \frac{V_{dc}}{I_1} = \frac{5}{2} = 2.5$$

Thus internal resistance across a-b is  $2.5 \Omega$

The given circuit is thus Thevenised to give  
 $R_{in} = 2.5 \Omega \quad V_{oc} = 0 \text{ volt} \quad \text{Total 10m}$

b

$$Y_{D1} = 1 + j1 \cdot 7$$

$$\therefore Y_{S1} = -j1 \cdot 7$$

$$\therefore \text{Distance to Stub } (d) = 0.181 + 0.051 \\ = 0.131$$

$$Y_{S1} = -j1 \cdot 7$$

$\therefore$  Stub length =  $(l) = 0.085d$  (From S/C end of Smith chart ie. right most end)

$$d = \frac{C}{\lambda} = \frac{3 \times 10^7}{100 \times 10^6} = \frac{3 \times 10 \times 10^7}{10^8} = 3 \text{ m}$$

$$(d = 0.13 \times 3 \text{ m} =$$

$$l = 0.085 \times 3 \text{ m} =$$

Total = 10 m

Q. No.

24@

$$Z_{LC}(s) = \frac{s(s^2+4)(s^2+6)}{(s^2+1)(s^2+5)}$$

$$Z_{LC}(s) = \frac{s^5 + 10s^3 + 24s}{s^4 + 6s^2 + 5}$$

Continued fraction expansion is shown below

$$\begin{aligned} & s^4 + 6s^2 + 5 \Big) s^5 + 10s^3 + 24s \\ & - \frac{s^5 + 6s^3 + 5s}{4s^3 + 19s} s^4 + 6s^2 + 5 \Big( s/4 \\ & \quad \frac{s^4 + \frac{19}{4}s^2}{\frac{5}{4}s^2 + 5} \\ & \quad \frac{4s^3 + 16s}{3s} \\ & \quad 3s \Big) \frac{\frac{5}{4}s^2 + 5}{\frac{5}{4}s^2} \Big( \frac{5}{12}s \\ & \quad \frac{3s}{\frac{3s}{5}} \end{aligned}$$

$Z_{LC}(s) \rightarrow \infty$  with  $s \rightarrow \infty$ ; also  $Z_{LC}(s) \rightarrow 0$  with  $s \rightarrow 0$ .

Thus for the function  $Z_{LC}(s)$ , having  $n > m$ , the first element is  $L_1$  and the last element is also an inductor

$$Z_{LC}(s) = s + \frac{1}{\frac{s}{4} + \frac{1}{\frac{16s}{5} + \frac{1}{\frac{5s}{12} + \frac{1}{\frac{3s}{15}}}}}$$

Thus  $L_1 = 1H$ ,  $Z_1(s) = 1 \cdot s (= L_1 s)$

$$C_2 = \frac{1}{4} F \quad Y_2(s) = \frac{s}{4}$$


$$\text{Giving } Z_2(s) = \frac{4}{s} = \frac{1}{s/4} F \cdot \frac{1}{Cs}$$

$$C_4 = \frac{5}{12} F, Y_4(s) = \frac{5}{12} s$$


$$\therefore Z_4(s) = \frac{1}{\frac{5}{12}s}$$

$$L_5 = \frac{3}{5} H, Z_5(s) = \frac{3}{5} s$$

∴ First Cauer form is —

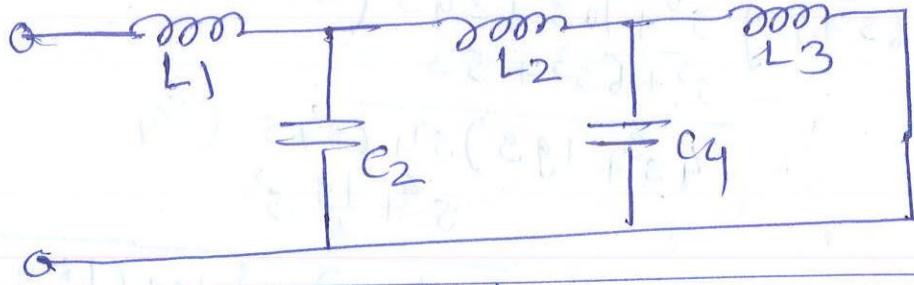

Total = 10m

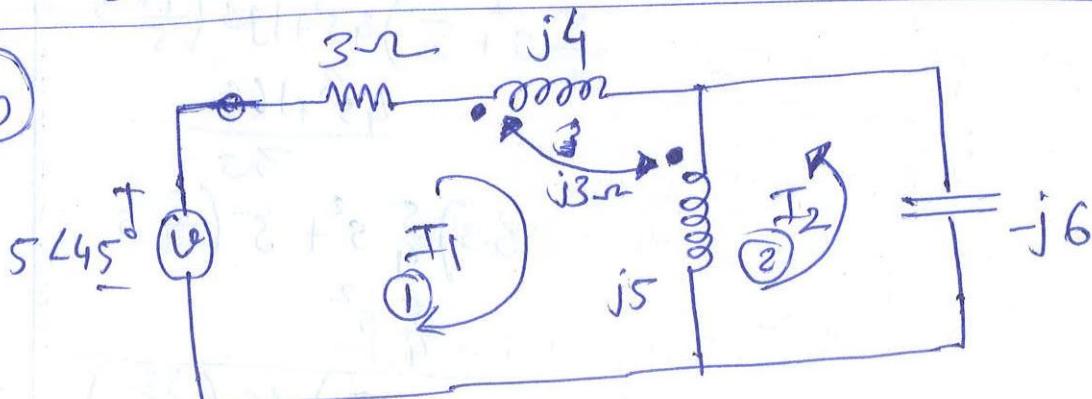

Applying KVL to Loop ①,

$$3I_1 + j4I_1 + j5(I_1 + I_2) + j3(I_2 + I_1) + j3I_1 = 5\angle 45^\circ$$

or \$(3 + j15)I\_1 + (j8)I\_2 = 5\angle 45^\circ\$

Applying KVL to loop ②

$$j5(I_1 + I_2) - j6I_2 + j3I_1 = 0$$

$$\therefore (j8)I_1 - jI_2 = 0$$

(3m)

In matrix form,

$$\begin{bmatrix} 3 + j15 & j8 \\ j8 & -j1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5\angle 45^\circ \\ 0 \end{bmatrix}$$

Q. No.

Marks

$$\therefore I_1 = 0.063 \angle -47.175^\circ \text{ Amp}$$

$$I_2 = -0.506 \angle 132.83^\circ \text{ Amp}$$

∴ Drop across 3Ω resistor is -

$$= 3 \times I_1 = 0.189 \angle -47.175^\circ$$


Drop across  $-j6\Omega$  capacitor is

$$= (-j6) I_2 = -3.036 \angle 42.83^\circ \text{ volt}$$

(2m)

(2m)

Total = 10 M

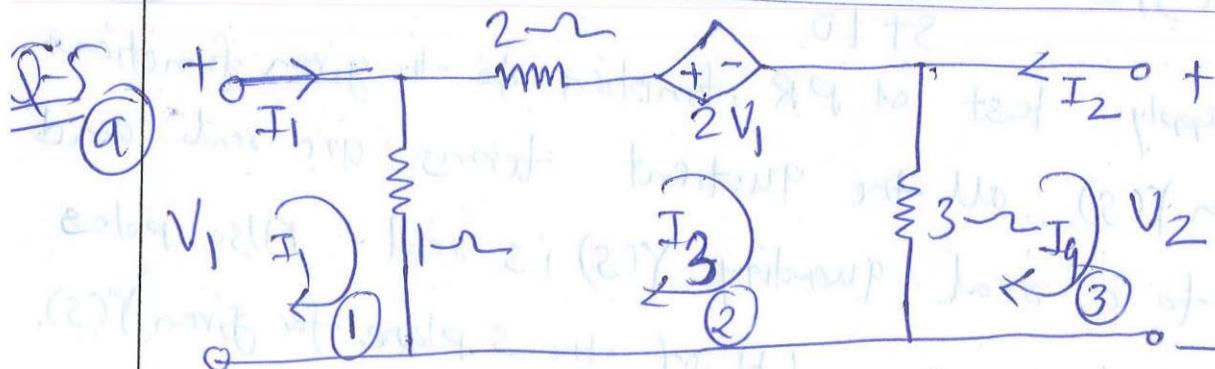

$$\text{For loop } ① \quad I_1 - I_3 = V_1 \quad ①$$

$$\text{For loop } ② \quad 2I_3 + 2V_1 + 3(I_3 - I_4) + 1(I_3 - I_1) = 0$$

$$-I_1 + 3I_2 + 6I_3 = -2V_1 \quad ②$$

$$\text{For loop } ③ \quad 3(I_4 - I_3) + V_2 = 0 \quad (I_4 = -I_2)$$

$$V_2 = 3I_3 + 3I_2 \quad ③$$

$$V_1 = \frac{5}{4} I_1 + \frac{3}{4} I_2$$

$$V_2 = -\frac{3}{4} I_1 + \frac{3}{4} I_2$$

Total = 10 V

$$Z_{11} = \frac{5}{4} \Omega, Z_{12} = \frac{3}{4} \Omega, Z_{21} = -\frac{3}{4} \Omega, Z_{22} = \frac{3}{4} \Omega$$

i-s  
①

Properties of positive real function

s-m

②

$$Y(s) = \frac{s^2 + 2s + 20}{s + 10}$$

s-m

Let us apply test of PR function to the given function.

- \* In given  $Y(s)$ , all the quotient terms are real and for  $s$  to a real quantity  $Y(s)$  is real. Also poles and zeros are on LH of the  $s$ -plane for given  $Y(s)$ .
- \* Next let us see the positive realness of given function in the  $j\omega$  domain

$$\operatorname{Re}[Y(j\omega)] = \operatorname{Re} \left[ \frac{(j\omega)^2 + 2(j\omega) + 20}{j\omega + 10} \right]$$


$$= \operatorname{Re} \left[ \frac{-\omega^2 + 2j\omega + 20}{j\omega + 10} \right] \left[ \frac{-j\omega + 10}{-j\omega + 10} \right]$$

$$= \operatorname{Re} \left[ \frac{-8\omega^2 + 200 + j\omega^3}{\omega^2 + 100} \right]$$

$$\operatorname{Re}[Y(j\omega)] = \frac{-8\omega^2 + 200}{\omega^2 + 100}$$

Total = 10 V

since for all values of  $\omega$ ,  $\operatorname{Re}[Y(j\omega)] \neq 0$ , this test certifies that given function  $Y(s)$  is not PRF.

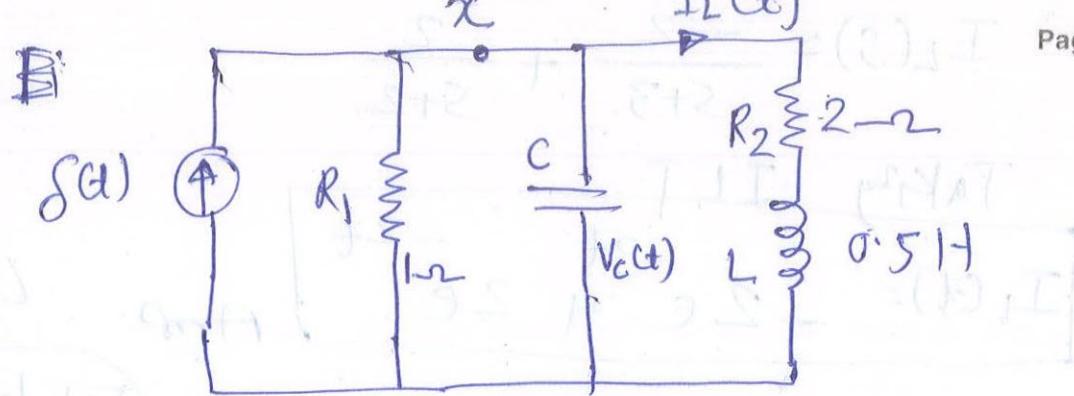~~Q. 6  
@~~

Using Nodal analysis to node x.

$$S(t) = \frac{V_c(t)}{R_1} + \frac{V_c(t)}{X_C} + \frac{V_c(t)}{Z_L} \quad \textcircled{1}$$

$$R_1 = 1\Omega, X_C = \frac{1}{j\omega C} = \frac{1}{j\omega \times 1} = \frac{1}{j\omega}$$

$$Z_L = R_2 + j\omega L = 2 + j0 - 5\omega = 2 + 0.5s$$

Taking Laplace transform of  $\textcircled{1}$

$$1 = \frac{V_c(s)}{1} + \frac{V_c(s)}{1/s} + \frac{V_c(s)}{2 + 0.5s}$$

$$\text{OR } V_c(s) = \frac{s+4}{s^2 + 5s + 6} = \frac{s+4}{(s+3)(s+2)} = \frac{A}{s+3} + \frac{B}{s+2}$$

Taking ILT and using Partial fraction

$$A = -1, B = 2$$

$$V_c(t) = -e^{-3t} + 2e^{-2t} \text{ volt}$$

6m

$$I_L(s) = \frac{V_c(s)}{Z_L(s)} = \frac{\frac{s+4}{(s+3)(s+2)}}{2 + 0.5s}$$

$$\text{OR } I_L(s) = \frac{2}{(s+3)(s+2)} = \frac{k_1}{s+3} + \frac{k_2}{s+2}$$

$$k_1 = -2, k_2 = 2$$


$$I_L(s) = \frac{-2}{s+3} + \frac{2}{s+2}$$

Taking ILT

$$I_L(t) = -2e^{-3t} + 2e^{-2t}$$

Amp 4m

Total 10m

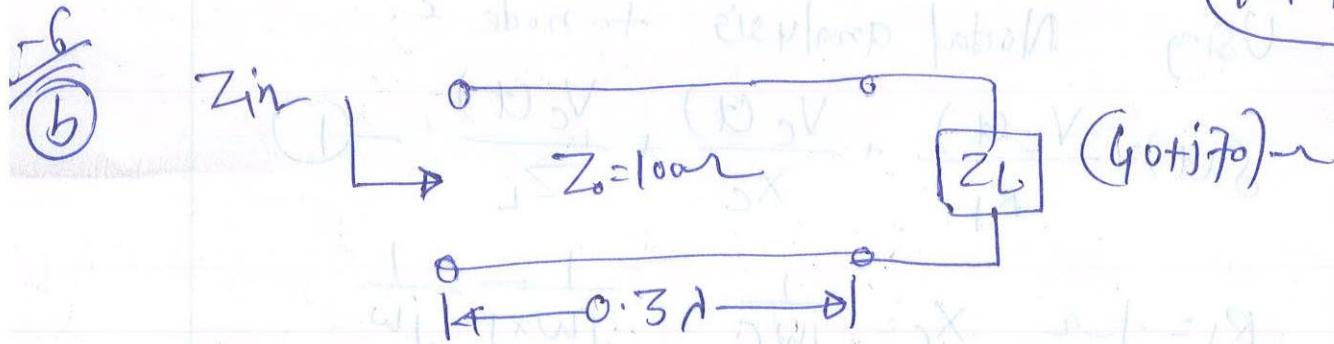

$$\textcircled{I} \quad Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

4m

$$Z_{in} = (36.5 - j61.1)\Omega$$

$$\textcircled{II} \quad \text{Load admittance at load } (Y_L) = \frac{1}{Z_L} = \frac{1}{40+j70} \times \frac{40-j70}{40-j70}$$

$$Y_L = \frac{40-j70}{(40)^2 + (70)^2} =$$

2m

$$\textcircled{III} \quad \text{Reflection coefficient at load } \Gamma_{load} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_{load} = \frac{40+j70 - 100}{40+j70 + 100} = 0.59 \angle 104^\circ$$

2m

$$\textcircled{IV} \quad \text{VSWR along the line } (\rho) =$$

$$\rho = \frac{1 - |\Gamma_{load}|}{1 + |\Gamma_{load}|} = \frac{1 + 0.59}{1 - 0.59}$$

2m

$$\rho = \frac{1.59}{0.41} = 3.878$$

Total 10m