

1

1

Solution

Q.P. code 24590

Q.1. A.


Soln

$$X_M = k \sqrt{X_{L1} X_{L2}}$$

$$= 0.8 \sqrt{(5)(10)}$$

$$X_M = 5.66 \Omega \quad (1 \text{ Mark})$$

Equivalent circuit.

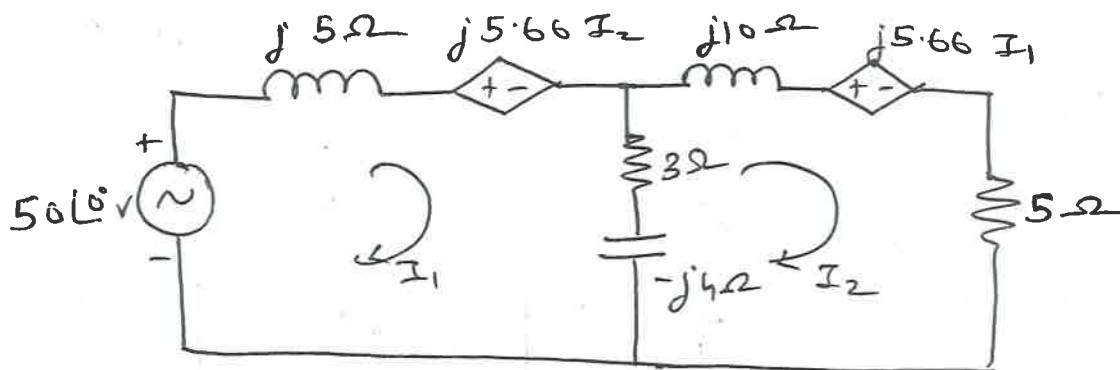


(4 marks)

B)

Soln

at $t = 0^-$, the equivalent circuit

is

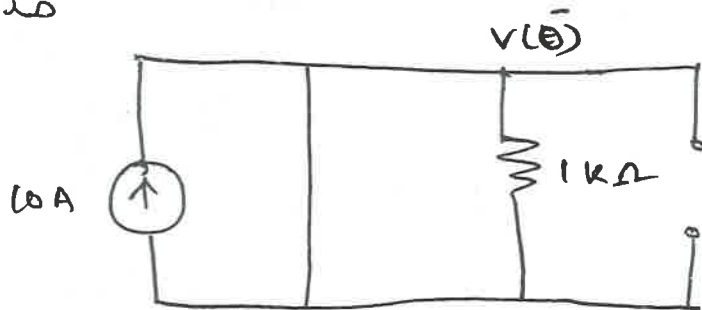


$$v(0^-) = v_c(0^-) = 0V \quad (1 \text{ Mark})$$

02


2

at $t = 0^+$, the equivalent circuit is

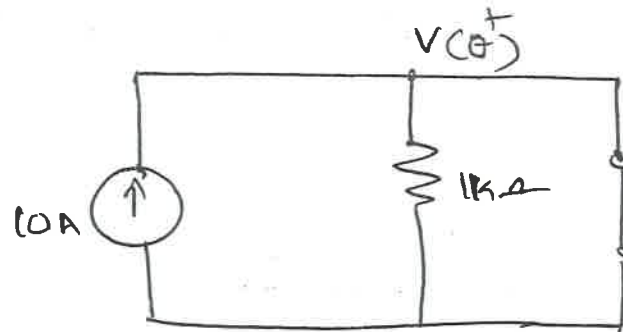

$$v(0^+) = v_c(0^+) = 0V. \quad (2 \text{ marks})$$

at $t > 0$, the equivalent circuit is

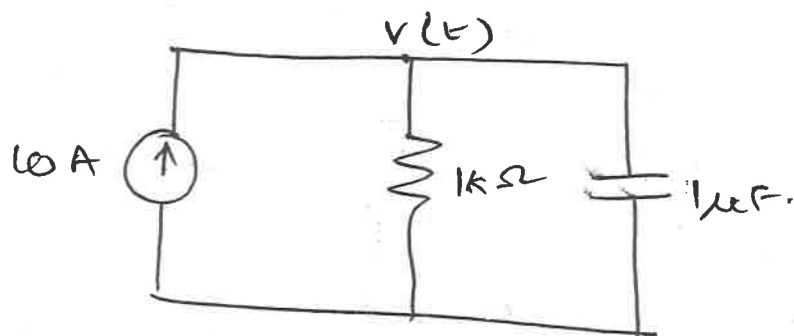

Applying KCL at the node

$$+10 - \left(\frac{v-0}{1k} \right) - C \frac{dv}{dt} = 0$$

$$\therefore 10 - \frac{v}{1000} - 1\mu \frac{dv}{dt} = 0 \quad (1 \text{ mark})$$

①

at $t = 0^+$, eqn ① becomes

$$10 - \frac{v(0^+)}{1000} - 1\mu \frac{dv(0^+)}{dt} = 0$$

$$\therefore 1\mu \frac{dv(0^+)}{dt} = 10$$

$$\therefore \frac{dv}{dt}(0^+) = \frac{10}{1\mu} = 10 \times 10^6 \text{ V/s.}$$

(1 mark)

1 c)

- 1) Application of source at i/p with o/p s.c. (1 mark)
Obtain ratio of i/p voltage to o/p current
- 2) Application of source to o/p with i/p s.c. Obtain ratio of o/p voltage to i/p current (2 marks)
- 3) Apply condition for reciprocity and obtain the desired result (2 marks)

1 D) Each definition carries (1 mark) 0

Q. 2

- A) 1) Analysis at $t = 0^-$ with circuit. (2 marks)
 $v_c(0^-) = 30V, i(0^-) = 0.$
- 2) Analysis at $t = 0^+$ with circuit (2 marks)
 $v_c(0^+) = 30V, i(0^+) = -1A.$
- 3) Analysis at $t > 0$ with circuit. (6 marks)
 $\frac{di(0^+)}{dt} = 0.33 \times 10^5 A/s$
 $\frac{d^2i(0^+)}{dt^2} = -1.1 \times 10^9 A/s^2.$

04

9

Q.2 B. Soln

① Application of KVL to obtain mesh equations (4 marks)

② Writing 2 parameters (2 marks)

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 4/5 & -4/5 \\ 2/5 & -12/5 \end{bmatrix}$$

③ Find Y-parameters using formula or otherwise. (2 marks)

④ Writing Y parameters (2 marks)

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 3/2 & -1/2 \\ 1/4 & -1/2 \end{bmatrix}$$

Q.3

A) 1) Application of KVL to write mesh equations for mesh ① - 3 marks.

2) Application of KVL to write mesh equation for mesh ② - 3 marks.

③ Mesh ② current $I_2 = -1A$. (2 marks)

④ Finding currents I_x and I_y and I_1 and I_2 by solving simultaneous equations.

$I_1 = 2A$ $I_2 = 0A$. (2 marks)

3 B)

05

(5)

$$R = 65 \Omega/\text{km} \quad L = 1.6 \text{ mH}/\text{km}$$

$$G = 2.25 \times 10^{-3} \text{ S}/\text{km} \quad C = 0.1 \mu\text{F}/\text{km}$$

Soln

$$\begin{aligned} Z &= R + j\omega L = 65 + j 2\pi \times 1000 \times 1.6 \times 10^{-3} \\ &= 65 + j 10.05 \Omega/\text{km} \\ &= 65.77 \angle 8.78^\circ \Omega/\text{km} \end{aligned}$$

(2 marks)

$$\begin{aligned} Y &= G + j\omega C = 2.25 \times 10^{-3} + j 2\pi \times 1000 \times 0.1 \times 10^{-6} \\ &= 2.25 \times 10^{-3} + j 6.28 \times 10^{-4} \text{ S} \\ &= 2.33 \times 10^{-3} \angle 15.59^\circ \text{ S}/\text{km} \end{aligned}$$

(2 marks)

$$\begin{aligned} \text{(Characteristic Impedance)} \quad Z_0 &= \sqrt{\frac{Z}{Y}} = \sqrt{\frac{65.77 \angle 8.78^\circ}{2.33 \times 10^{-3} \angle 15.59^\circ}} \\ &= 168.01 \angle 3.405^\circ \Omega \end{aligned}$$

(2 marks)

* Propagation constant

$$\gamma = \sqrt{ZY} = 0.391 \angle 12.19^\circ / \text{km}$$

(2 marks)

$$\text{Attenuation constant } \alpha = 0.382 + j 0.083 / \text{km}$$

$$0.382 \text{ nepers}/\text{km} \quad \text{(1 mark)}$$

$$\text{Phase constant } \beta = 0.083 \text{ rad}/\text{km}$$

(1 mark)

4 A)

i) $F(s) = \frac{N(s)}{D(s)}$
 ii) $\frac{N(s)}{D(s)}$

- a) Prove the Numerator is Hurwitz and denominator has to be factorized to show ~~the~~ no poles lie on RHS of s-plane. (2 marks) ~~Poles are not ~~any~~~~
- b) Since poles lie on the jw axis, carry out the residue test. (1 mark)
- c) Find $A(\omega^2)$ and show if $A(\omega^2) \geq 0$ for all ω , (1 mark)
- d) Final comment on PRF. (1 mark)

A

- B)
- 1) Calculation of V_{TH} (3 marks)
 $V_{TH} = 75V$
 - 2) Calculation of I_N (3 marks)
 $I_N = 2A$
 - 3) Calculation of R_{TH} (2 marks)
 $R_{TH} = 37.5 \Omega$
 - 4) Thevenin's equivalent n/w. (2 marks)

5) A)

07

7

soln

1) Break the network into two. (1 mark)

2) Write ~~KVL~~ KCL equations for network (1) (3 marks)

3) Write the Y-parameters for network (1).

$$\begin{bmatrix} Y'_{11} & Y'_{12} \\ Y'_{21} & Y'_{22} \end{bmatrix} = \begin{bmatrix} \frac{4s+1}{8s+4} & -\frac{1}{8s+4} \\ -\frac{1}{8s+4} & \frac{4s+1}{8s+4} \end{bmatrix} \quad (4 \text{ marks})$$

4) Write KCL equations for network (2)

(3 marks)

5) Write Y-parameters for network (2)

$$\begin{bmatrix} Y''_{11} & Y''_{12} \\ Y''_{21} & Y''_{22} \end{bmatrix} = \begin{bmatrix} \frac{s(s+1)}{2s+1} & -\left(\frac{s^2}{2s+1}\right) \\ -\left(\frac{s^2}{2s+1}\right) & \frac{s(s+1)}{2s+1} \end{bmatrix} \quad (1 \text{ mark})$$

6) Find Y-parameters of overall n/w. (1 mark)

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{4s^2+8s+1}{4(2s+1)} & -\frac{4s^2+1}{4(2s+1)} \\ -\frac{(4s^2+1)}{4(2s+1)} & \frac{4s^2+8s+1}{4(2s+1)} \end{bmatrix}$$

5 (B)

~~For Foster II~~Realization of $Y(s)$

a) Identification as LC function. (2 marks)

1) Foster II Realization

(08)


(8)

1) Partial Fraction expansion of $Y(s)$ (2 marks)

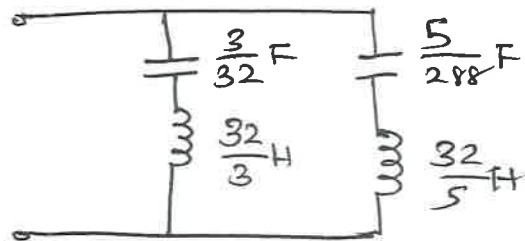2) Finding the component values and drawing the circuit (2 marks)

$$L_1 = \frac{32}{3} \text{ H} \quad C_1 = \frac{3}{32} \text{ F}$$


$$L_2 = \frac{32}{5} \text{ H} \quad C_2 = \frac{5}{288} \text{ F}$$



II Case I realization

1) Continued fraction expansion of $Z(s)$ (2 marks)

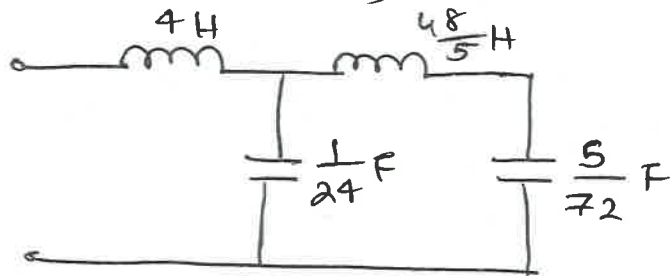2) Finding the component values and drawing the circuit (2 marks)



Q 6) A)

1) Find the normalized load impedance

$$\bar{Z}_L = \frac{25 + j50}{50} = 0.5 + j \Omega$$

(2 marks)

2) Mark the normalized load impedance point A at the intersection of $r = 0.5$ circle and $x = 1$ circle. (1 mark)

3) Draw the VSWR circle with centre O and radius equal to distance OA. The VSWR circle cuts the horizontal axis at

09

$x = 4.2$ on the right hand side

9

$\therefore VSWR = 4.2$ (2 marks)

- 4) Draw an arc with radius OA on the reflection coefficient line located at the lower side of the chart. This arc cuts the line at 0.62.

$\therefore |\Gamma| = 0.62$ (1 mark)

- 5) Extend line OA up to outer circumference of the chart to get point A'. The angle corresponding to A' is 83° .

$\therefore \phi = 83^\circ$

$\Gamma = |\Gamma| \angle \phi = 0.62 \angle 83^\circ$
(1 mark)

- 6) Find normalized input impedance

$\bar{Z}_s = 0.28 - j0.4$ (2 marks)

- 7) Actual input impedance is

$Z_s = Z_0 \bar{Z}_s = 50(0.28 - j0.4)$
 $= 14 - j20 \Omega$ (1 mark)

6) B) soln

10

(10)

1) Analysis at $t = 0^-$

(3 marks)

$$i(0^-) = 1A$$

$$v_2(0^-) = 0$$

2) Analysis at $t = 0^+$

(2 marks)

$$i(0^+) = 1A$$

$$v_2(0^+) = -0.5V$$

3) Analysis at $t > 0$

a) draw the equivalent circuit (1 mark)

b) Apply KCL to obtain node equation
(1 mark)

c) Obtain differential equation of the
form $\frac{dv}{dt} + Pv = 0$ (1 mark)

d) Find solution of the differential eqn.

$$v_2(t) = -0.5 e^{-\frac{3}{4}t} \quad \text{for } t > 0. \quad (2 \text{ marks})$$