

Q.1

(a) De Morgan's theorems

1)  $\overline{AB} = \bar{A} + \bar{B}$

Proof:

| A   | B   | $\overline{AB}$ | $\bar{A}$ | $\bar{B}$ | $\bar{A} + \bar{B}$ |
|-----|-----|-----------------|-----------|-----------|---------------------|
| (1) | (2) | (3)             | (4)       | (5)       | (6)                 |
| 0   | 0   | 1               | 1         | 1         | 1                   |
| 0   | 1   | 1               | 1         | 0         | 1                   |
| 1   | 0   | 1               | 0         | 1         | 1                   |
| 1   | 1   | 0               | 0         | 0         | 0                   |

column (3) = column (6)  
 $\overline{AB} = \bar{A} + \bar{B}$  Hence proved.


2)  $\overline{A+B} = \bar{A} \cdot \bar{B}$

| A   | B   | $\overline{A+B}$ | $\bar{A}$ | $\bar{B}$ | $\bar{A} \cdot \bar{B}$ |
|-----|-----|------------------|-----------|-----------|-------------------------|
| (1) | (2) | (3)              | (4)       | (5)       | (6)                     |
| 0   | 0   | 1                | 1         | 1         | 1                       |
| 0   | 1   | 0                | 1         | 0         | 0                       |
| 1   | 0   | 0                | 0         | 1         | 0                       |
| 1   | 1   | 0                | 0         | 0         | 0                       |

column (3) = column (6)  
 $\overline{A+B} = \bar{A} \cdot \bar{B}$

(b) Compare Combinational and sequential logic ckt.

|               |            |
|---------------|------------|
| Combinational | Sequential |
|---------------|------------|

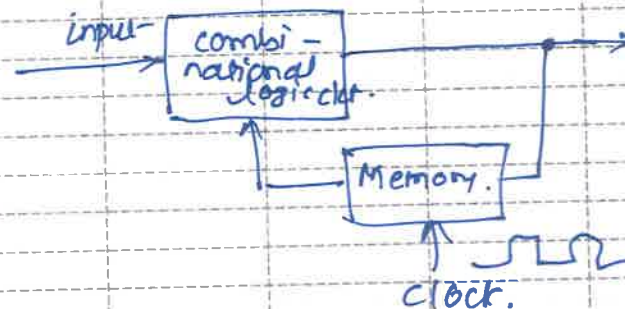

1) The output depends on present input.

2) No need of clock.

3) No need of memory

1) o/p depends on present inputs and past output.

2) clock required.

3) Memory required.

Q.1(c) Define

**Propagation delay:** The output of a logic gate does not change its state instantaneously in response to the change in the state of its input. There is a time delay in the two events. This time delay is known as the propagation delay.

Thus propagation delay is defined as the time delay between the instants of application of the input and the instant of occurrence of the corresponding output.


**Power Dissipation:** Due to applied voltage and the flow of the resultant current, some power is dissipated in the form of heat.

$$P_D = V_{CC} \cdot I_{CC}$$

**Fan Out:** Fan out is defined as the maximum number of ~~output~~ devices a gate can drive without change in its output voltage.

**Fan in:** Fan in is defined as the number of inputs a Gate has.

(d) Programmable Logic Array:

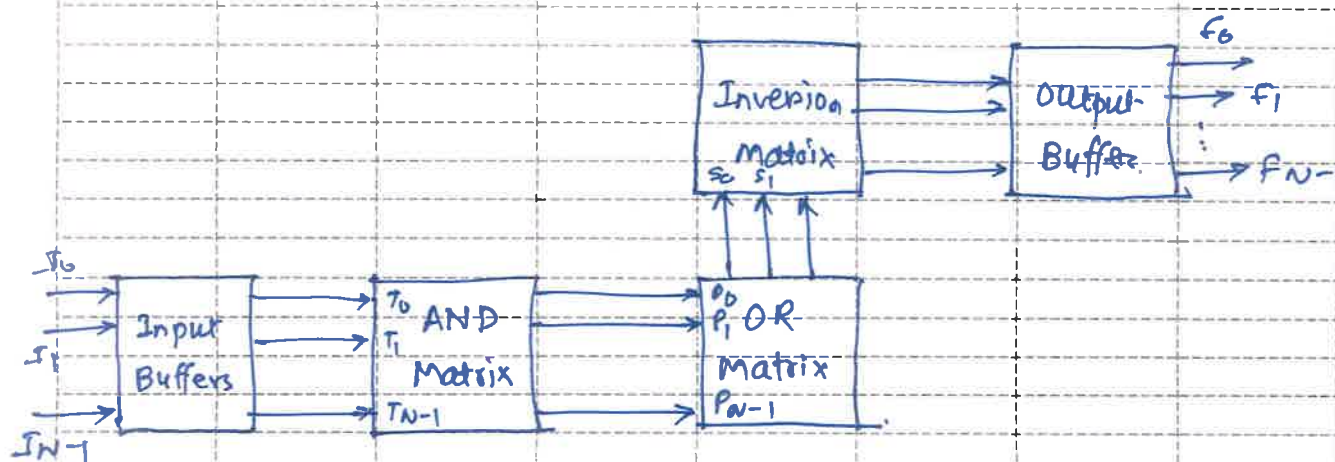



03


Q.2(a)

NAND


1) NOT Gate.




2) AND

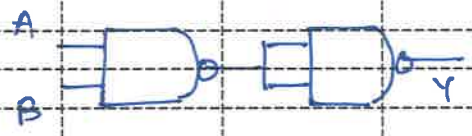


3) OR Gate

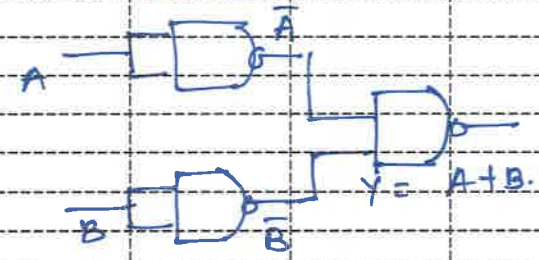

4) NOR:

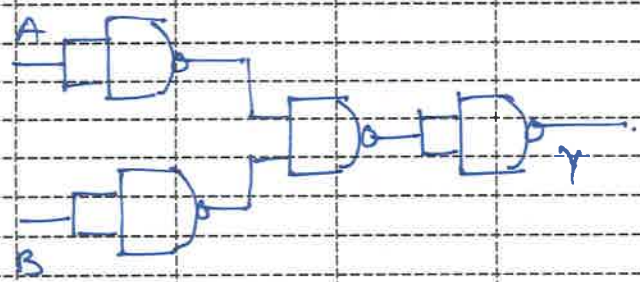


5) Ex-OR

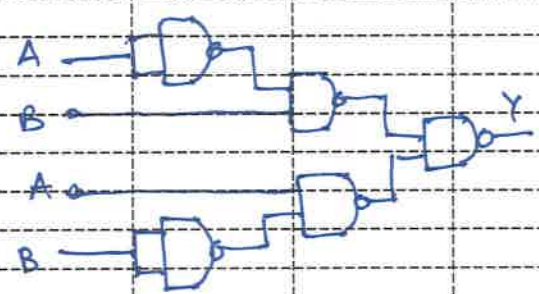


NOR


1) NOT

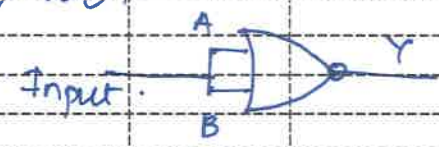


2) AND

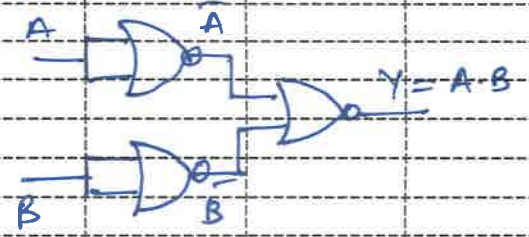


3) OR

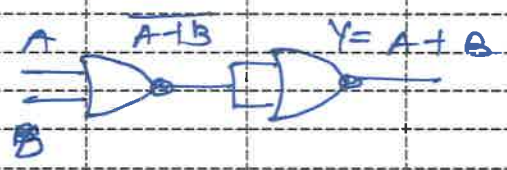

4) NAND

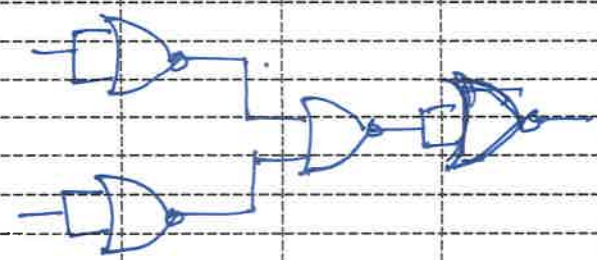

5) Ex-OR

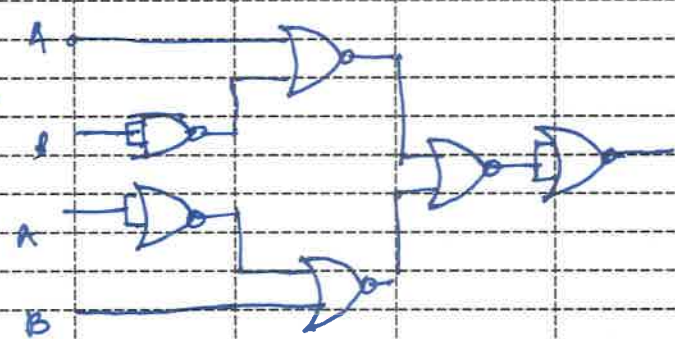



04

# Q.2(b) Two bit digital comparator

| S <sub>2</sub> | Inputs         |                |                |                | Output |       |       |
|----------------|----------------|----------------|----------------|----------------|--------|-------|-------|
|                | A <sub>1</sub> | A <sub>0</sub> | B <sub>1</sub> | B <sub>0</sub> | A < B  | A = B | A > B |
| 0              | 0              | 0              | 0              | 0              | 0      | 1     | 0     |
| 1              | 0              | 0              | 0              | 1              | 1      | 0     | 0     |
| 2              | 0              | 0              | 1              | 0              | 1      | 0     | 0     |
| 3              | 0              | 0              | 1              | 1              | 1      | 0     | 0     |
| 4              | 0              | 1              | 0              | 0              | 0      | 0     | 1     |
| 5              | 0              | 1              | 0              | 1              | 0      | 1     | 0     |
| 6              | 0              | 1              | 1              | 0              | 1      | 0     | 0     |
| 7              | 0              | 1              | 1              | 1              | 1      | 0     | 0     |
| 8              | 1              | 0              | 0              | 0              | 0      | 0     | 1     |
| 9              | 1              | 0              | 0              | 1              | 0      | 1     | 0     |
| 10             | 1              | 0              | 1              | 0              | 1      | 0     | 0     |
| 11             | 1              | 0              | 1              | 1              | 1      | 0     | 0     |
| 12             | 1              | 1              | 0              | 0              | 0      | 0     | 1     |
| 13             | 1              | 1              | 0              | 1              | 0      | 0     | 1     |
| 14             | 1              | 1              | 1              | 0              | 0      | 1     | 0     |
| 15             | 1              | 1              | 1              | 1              | 0      | 1     | 0     |

K-Map for A < B

| B <sub>1</sub> B <sub>0</sub> | A <sub>1</sub> A <sub>0</sub> |    |    |    |
|-------------------------------|-------------------------------|----|----|----|
|                               | 00                            | 01 | 11 | 10 |
| 00                            |                               |    |    |    |
| 01                            | 1                             |    |    |    |
| 11                            | 1                             |    |    | 1  |
| 10                            | 1                             | 1  |    |    |

$$(A < B) = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

K-Map for A = B


| B <sub>1</sub> B <sub>0</sub> | A <sub>1</sub> A <sub>0</sub> |    |    |    |
|-------------------------------|-------------------------------|----|----|----|
|                               | 00                            | 01 | 11 | 10 |
| 00                            | 1                             |    |    |    |
| 01                            |                               | 1  |    |    |
| 11                            |                               |    | 1  |    |
| 10                            |                               |    |    | 1  |

$$(A = B) = (A_1 \odot B_1) (A_0 \odot B_0)$$

K-Map for A > B


| B <sub>1</sub> B <sub>0</sub> | A <sub>1</sub> A <sub>0</sub> |    |    |    |
|-------------------------------|-------------------------------|----|----|----|
|                               | 00                            | 01 | 11 | 10 |
| 00                            |                               | 1  | 1  | 1  |
| 01                            |                               |    | 1  | 1  |
| 11                            |                               |    |    |    |
| 10                            |                               |    |    | 1  |
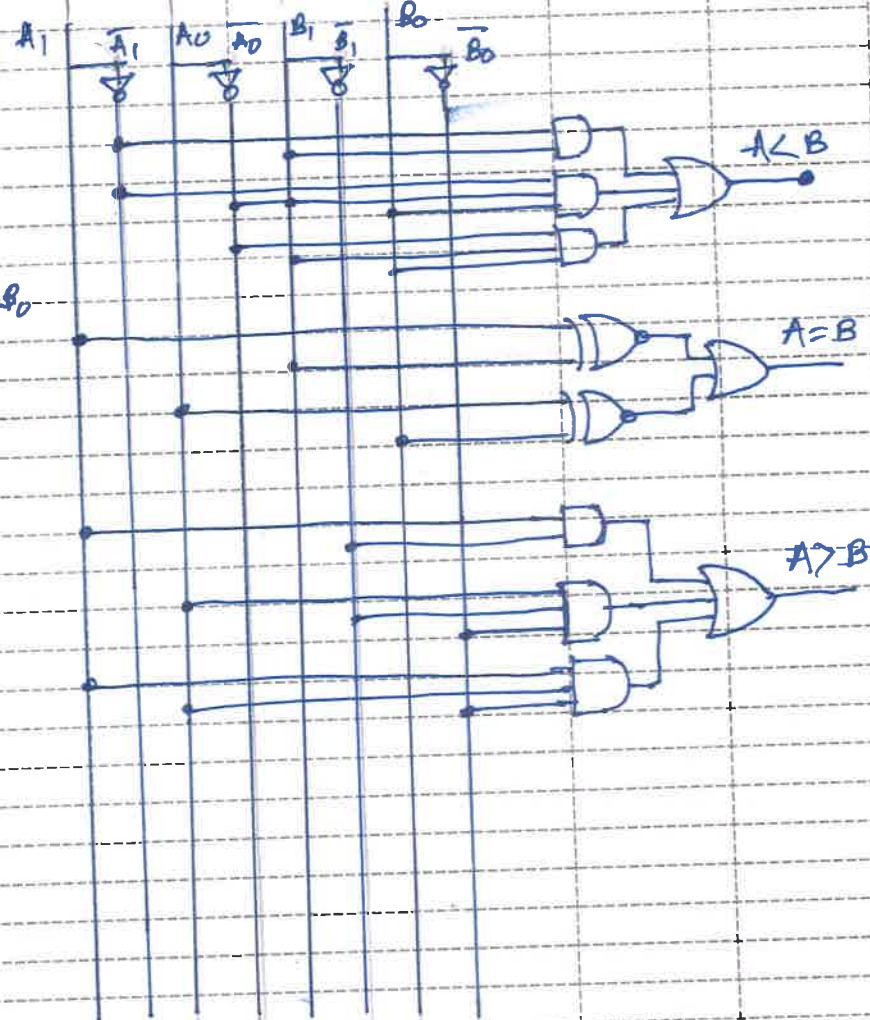
$$A > B = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_0$$




05
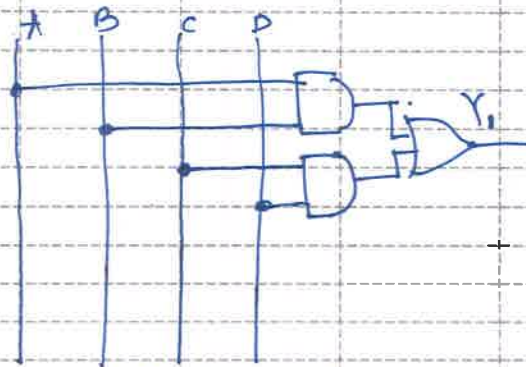
$$\begin{aligned}
 Q.3(a) \quad Y_1 &= (A+C)(A+D)(B+C)(B+D) \\
 &= (AA+AD+AC+CD)(B+C)(B+D) \\
 &= (A+AD+AC+CD)(B+C)(B+D) \\
 &= [A(1+C+D)+CD](B+C)(B+D) \\
 &= [A+CD](B+C)(B+D) \\
 &= [A+CD](BB+BD+BC+CD) \\
 &= [A+CD][B(1+C+D)+CD] \\
 &= [A+CD][B+CD] \\
 &= AB+ACD+BCD+CD \cdot CD \\
 &= AB+ACD+BCD+CD \\
 &= AB+CD(1+A+B) \\
 &= AB+CD
 \end{aligned}$$


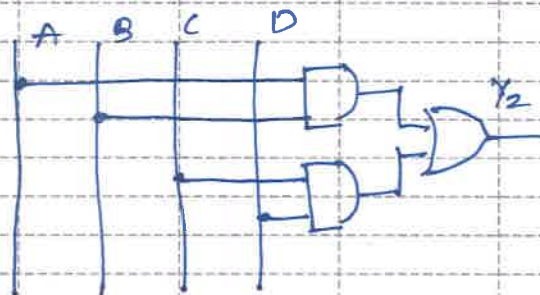
$$\begin{aligned}
 Y_2 &= (AB+C)(AB+D) \\
 &= (AB+ABD+AB(C+D)) \\
 &= AB(1+C+D)+CD \\
 &= AB+CD
 \end{aligned}$$






06

Q.3(b)  $F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 6, 8, 9, 10, 12, 13, 15)$

|           |   |   |    |           |    |    |           |    |
|-----------|---|---|----|-----------|----|----|-----------|----|
| $\bar{A}$ | 0 | 1 | 2  | 3         | 4  | 5  | 6         | 7  |
| A         | 8 | 9 | 10 | 11        | 12 | 13 | 14        | 15 |
| Input-    | 1 | 1 | 1  | $\bar{A}$ | 1  | 1  | $\bar{A}$ | A  |

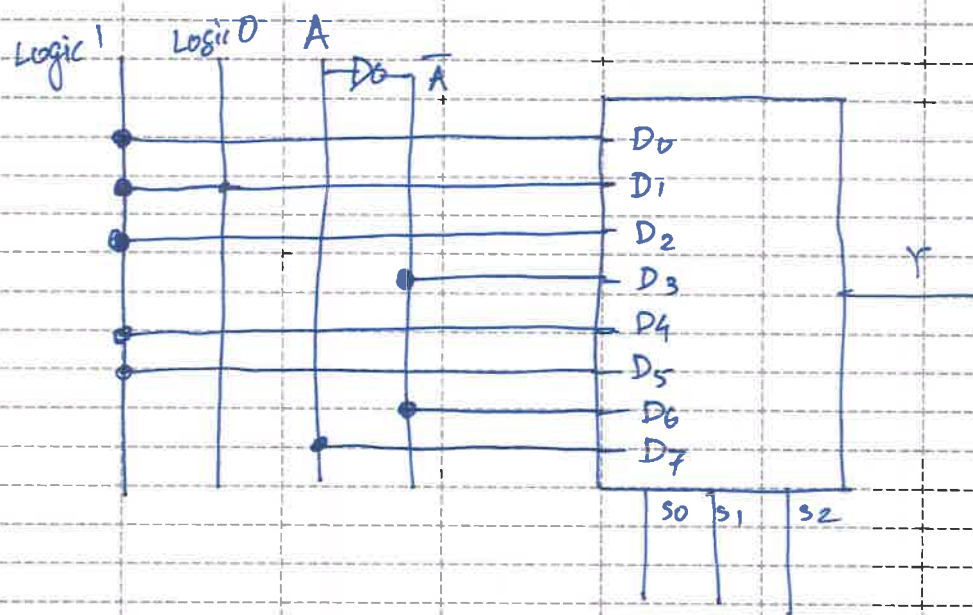

Q.5 a)  $f(A, B, C, D) = \sum m(1, 3, 7, 9, 10, 11, 13, 15)$

| Step 1 | Group | Minterm | A | B | C | D |
|--------|-------|---------|---|---|---|---|
|        | 0     | 1       | 0 | 0 | 0 | 1 |
|        |       | 3       | 0 | 0 | 1 | 1 |
|        | 1     | 9       | 1 | 0 | 0 | 1 |
|        |       | 10      | 1 | 0 | 1 | 0 |
|        |       | 7       | 0 | 1 | 1 | 1 |
|        | 2     | 11      | 1 | 0 | 1 | 1 |
|        |       | 13      | 1 | 1 | 0 | 1 |
|        | 3     | 15      | 1 | 1 | 1 | 1 |

07

| Step II | Group | Pair of Minterms | Binary |   |   |   | Prime Implicants |
|---------|-------|------------------|--------|---|---|---|------------------|
|         | 0     | 1-3              | 0      | 0 | - | 1 | ✓                |
|         |       | 1-9              | -      | 0 | 0 | 1 | ✓                |
|         |       | 3-7              | 0      | - | 1 | 1 | ✓                |
|         | 1     | 3-11             | -      | 0 | 1 | 1 | ✓                |
|         |       | 5-11             | 1      | 0 | - | 1 | ✓                |
|         |       | 9-13             | 1      | - | 0 | 1 | ✓                |
|         |       | 10-11            | 1      | 0 | 1 | - | ✓                |
|         |       |                  |        |   |   |   | $A\bar{B}C$      |
|         | 2     | 7-15             | -      | 1 | 1 | 1 | ✓                |
|         |       | 11-15            | 1      | - | 1 | 1 | ✓                |
|         |       | 13-15            | 1      | 1 | - | 1 | ✓                |

| Step III | Group | Minterms      | Binary |   |   |   |            |
|----------|-------|---------------|--------|---|---|---|------------|
|          | 0     | 1, 3, 9, 11   | -      | 0 | - | 1 | $\bar{B}D$ |
|          | 1     | 3, 7, 11, 15  | -      | - | 1 | 1 | $CD$       |
|          |       | 9, 11, 13, 15 | 1      | - | - | 1 | $AD$       |

Table of Prime Implicants.

| Prime Implicants. | Decimal numbers. | 1   | 3 | 7   | 9 | 10  | 11 | 13  | 15 |
|-------------------|------------------|-----|---|-----|---|-----|----|-----|----|
| $A\bar{B}C$       | 10, 11           |     |   |     |   | (X) | X  |     |    |
| $\bar{B}D$        | 1, 3, 9, 11      | (X) | X |     | X |     | X  |     |    |
| $CD$              | 3, 7, 11, 15     |     | X | (X) |   |     | X  |     | X  |
| $AD$              | 9, 11, 13, 15    |     |   |     | X |     | X  | (X) | X  |

$$\therefore f(A, B, C, D) = A\bar{B}C + \bar{B}D + CD + AD$$



## Q.6(b) JK FF to D FF Conversion

Truth Table

| Inputs |       | $Q_{n+1}$ | Outputs |       |
|--------|-------|-----------|---------|-------|
| D      | $Q_n$ |           | $J_n$   | $K_n$ |
| 0      | 0     | 0         | 0       | x     |
| 1      | 0     | 1         | 1       | x     |
| 0      | 1     | 0         | x       | 1     |
| 1      | 1     | 1         | x       | 0     |

K-Map for J


|                    |   |   |
|--------------------|---|---|
| $Q_n \backslash D$ | 0 | 1 |
| 0                  |   | 1 |
| 1                  | x | x |

$J = D$

K-Map for K

|                    |   |   |
|--------------------|---|---|
| $Q_n \backslash D$ | 0 | 1 |
| 0                  | x | x |
| 1                  | 1 |   |

$K = \bar{D}$

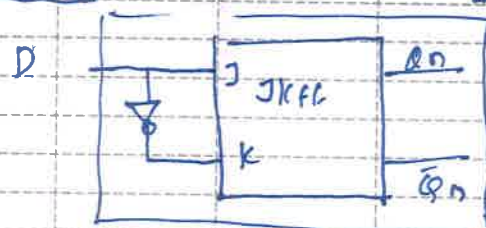


## T FF = D FF Conversion

| Inputs |       | $Q_{n+1}$ | Output |
|--------|-------|-----------|--------|
| D      | $Q_n$ |           | T      |
| 0      | 0     | 0         | 0      |
| 1      | 0     | 1         | 1      |
| 0      | 1     | 0         | 1      |
| 1      | 1     | 1         | 0      |

K-Map for T

|                    |   |   |
|--------------------|---|---|
| $Q_n \backslash D$ | 0 | 1 |
| 0                  |   | 1 |
| 1                  | 1 |   |

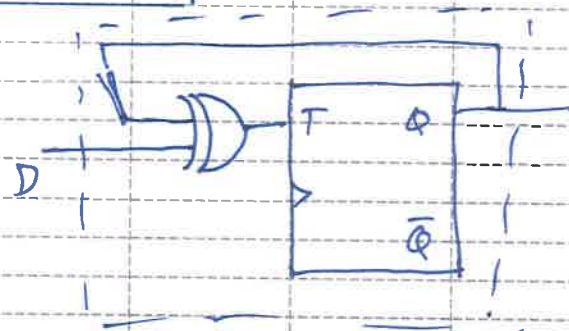

$$T = \bar{D}Q_n + D\bar{Q}_n$$

$$= D \oplus Q_n$$



09

