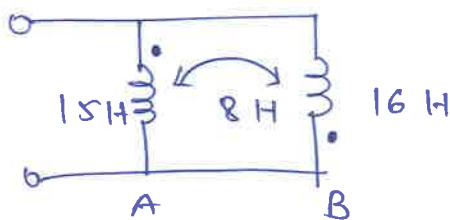


Solution set

Q p code. 22709

1 (a)



$$L_A = L_1 - m_{12} = 15 - 8 = 7 \text{ H}$$

$$L_B = L_2 - m_{12} = 16 - 8 = 8 \text{ H}$$

$$\frac{1}{L} = \frac{1}{L_A} + \frac{1}{L_B}$$

$$= \frac{1}{7} + \frac{1}{8} = \frac{15}{56}$$

$$L = \frac{56}{15} = 3.73 \text{ H}$$

(b)

$$m(s) = s^4 + 6s^2 + 8$$

$$n(s) = 7s^3 + 21s$$

$$7s^3 + 21s \overline{) s^4 + 6s^2 + 8} \left(\frac{1}{7}s \right.$$

$$\underline{s^4 + 3s^2}$$

$$3s^2 + 8 \overline{) 7s^3 + 21s} \left(\frac{7}{3}s \right.$$

$$\underline{7s^3 + \frac{56s}{3}}$$

$$\frac{7}{3}s \overline{) 3s^2 + 8} \left(\frac{19}{7}s \right.$$

$$\underline{3s^2}$$


$$8 \overline{) \frac{7}{3}s} \left(\frac{7}{24}s \right.$$

$$\underline{\frac{7}{3}s}$$


$$0$$

since all the quotient terms are positive, the polynomial $P(s)$ is Hurwitz.

(c)

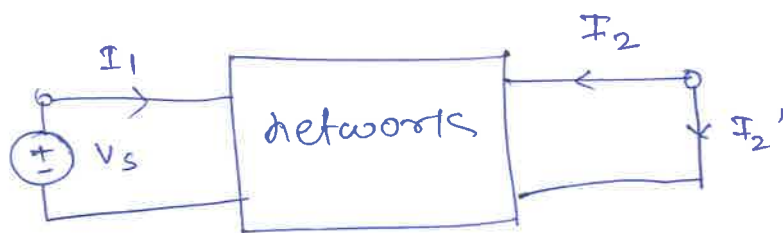
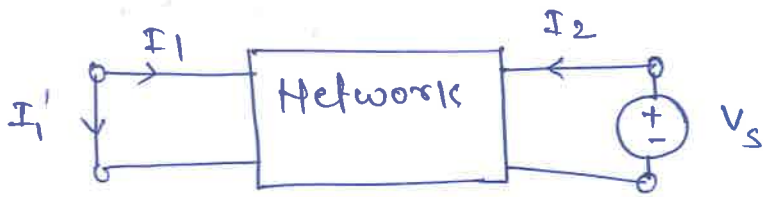
$$\frac{V_s}{I_2'} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}}$$




$$\frac{V_s}{I_1'} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{12}}$$

For the network to be reciprocal

$$\frac{V_s}{I_1'} = \frac{V_s}{I_2'}$$

$$Z_{12} = Z_{21}$$

(d)

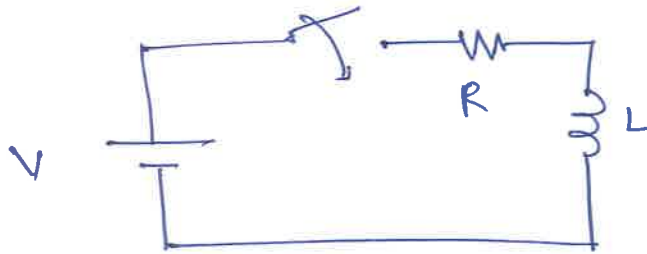

$$V - Ri - L \frac{di}{dt} = 0$$

$$\frac{L di}{V - Ri} = dt$$

Integrating both the sides

$$-\frac{L}{R} \ln(V - Ri) = t + K \quad \text{--- (1)}$$


setting $i = 0$ at $t = 0$

$$-\frac{L}{R} \ln V = K \quad \text{put in (1)}$$

$$-\frac{L}{R} [\ln(V - Ri)] = t - \frac{L}{R} \ln V$$

$$\frac{V - Ri}{V} = e^{-\frac{R}{L}t}$$
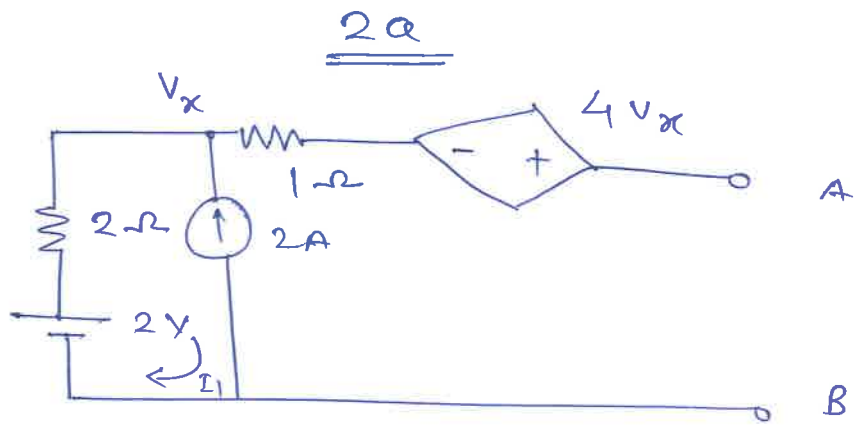
$$i = \frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L}t}$$



Step-I Calculation of V_{TH}

$$2 - 2I_1 - V_x = 0$$

$$V_x = 2 - 2I_1$$


For mesh I $I_1 = -2A$

$$V_x = 2 - 2(-2) = 6V$$

$$\therefore 2 - 2I_1 - 0 + 4V_x - V_{TH} = 0$$

$$V_{TH} = 30V$$

Step-II Calculation of I_N

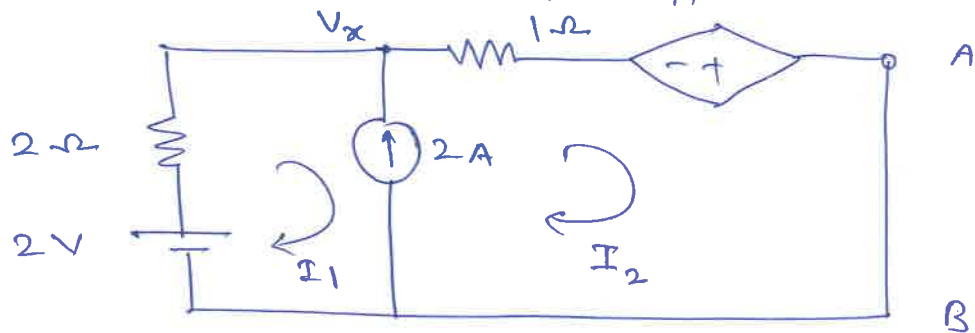

$$V_x = 2 - 2I_1$$

$$I_2 - I_1 = 2$$

Applying KVL


$$2 - 2I_1 - I_2 + 4V_x = 0$$

$$10I_1 + I_2 = 10$$

$$I_1 = 0.73 \quad I_2 = 2.73A$$

$$I_N = 2.73A$$
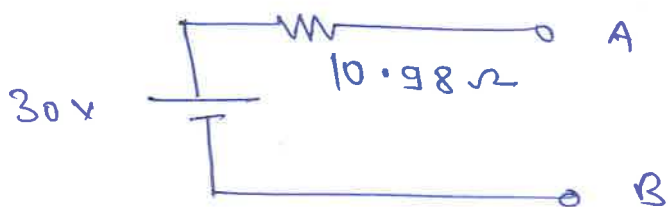
$$R_{TH} = \frac{V_{TH}}{I_N} = \frac{30}{2.73} = 10.98\Omega$$




2b

$$\text{At } t = 0^- \quad i(0^-) = \frac{100}{10+10} = 5 \text{ A}$$

$$\begin{aligned} V_c(0^-) &= 100 - 10(i(0^-)) - 5i(0^-) \\ &= 100 - 50 - 25 = 25 \text{ V} \end{aligned}$$

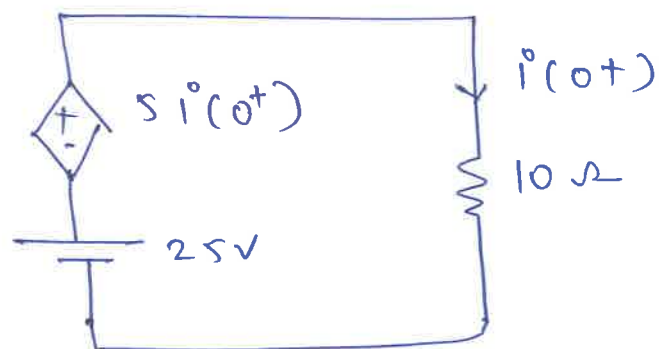At $t = 0^+$ the network is as shown below



$$\begin{aligned} 25 + 5i(0^+) - 10i(0^+) &= 0 \\ i(0^+) &= 5 \text{ A} \end{aligned}$$


For $t > 0$

$$25 - \frac{1}{4 \times 10^{-6}} \int_0^t i \, dt + 5i - 10i = 0$$

$$\frac{di}{dt} + 5000i = 0$$

$$i(t) = e^{-50000t} \quad \text{for } t > 0$$

3a

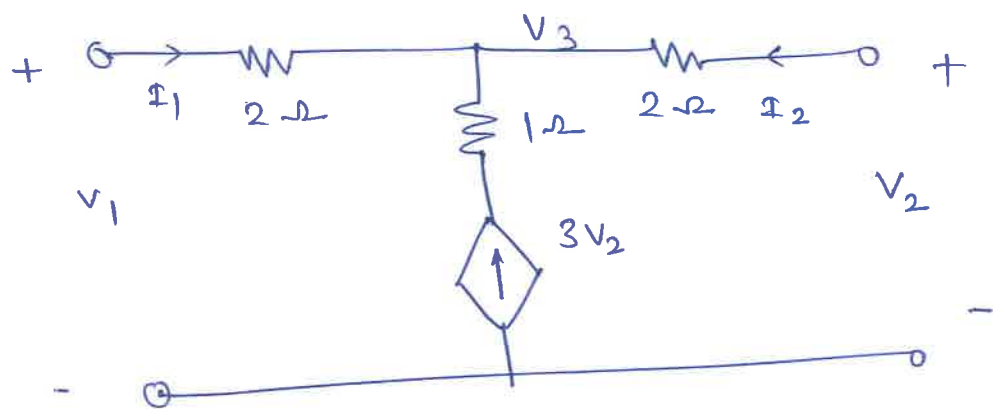

$$I_1 = \frac{V_1 - V_3}{2}$$

$$= \frac{V_1}{2} - \frac{V_3}{2}$$

$$I_2 = \frac{V_2 - V_3}{2}$$

$$= \frac{V_2}{2} - \frac{V_3}{2}$$

writing kcl at node

$$I_1 + I_2 + 3V_2 = 0$$

putting in above equation

$$\frac{V_1 - V_3}{2} + \frac{V_2 - V_3}{2} + 3V_2 = 0$$

$$V_3 = \frac{V_1}{2} + \frac{7}{2}V_2$$

$$I_1 = \frac{V_1}{4} - \frac{7}{4}V_2$$

$$I_2 = \frac{V_1}{4} - \frac{5}{4}V_2$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{4} & -\frac{7}{4} \\ -\frac{1}{4} & -\frac{5}{4} \end{bmatrix}$$

*

3b

Partial I form


$$Z(s) = \frac{s^2 + 4s + 3}{s^2 + 2s}$$

$$\begin{array}{r} s^2 + 2s \sqrt{s^2 + 4s + 3} \quad (1) \\ \underline{s^2 + 2s} \\ 2s + 3 \end{array}$$

$$Z(s) = 1 + \frac{2s + 3}{s^2 + 2s}$$

$$Z(s) = 1 + \frac{K_1}{s} + \frac{K_2}{s+2}$$
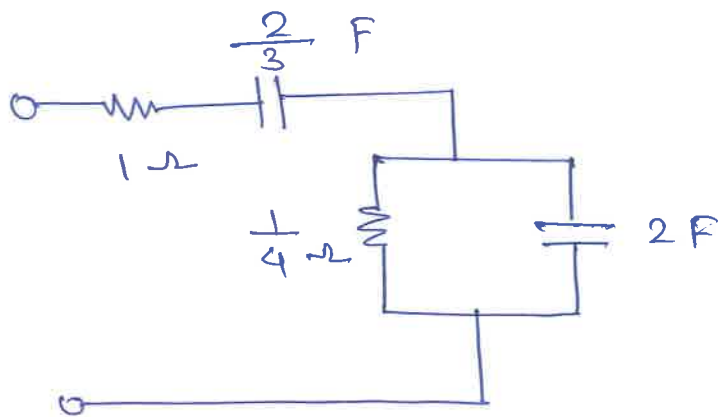
$$Z(s) = 1 + \frac{3/2}{s} + \frac{1}{s+2}$$



Case - II

$$Z(s) = \frac{3 + 4s + s^2}{2s + s^2}$$

By continued fraction method

$$2s + s^2 \overline{) 3 + 4s + s^2} \left(\frac{3}{2s} \right.$$

$$3 + \frac{3}{2}s$$

$$\frac{5}{2}s + s^2 \overline{) 2s + s^2} \left(\frac{4}{s} \right.$$


$$2s + \frac{4}{5}s^2$$

$$\frac{1}{5}s^2 \overline{) \frac{5}{2}s + s^2} \left(\frac{25}{2s} \right.$$

$$\frac{5}{2}s$$

$$s^2 \overline{) \frac{s^2}{5}} \left(\frac{1}{5} \right.$$

$$\frac{1}{5}s^2$$

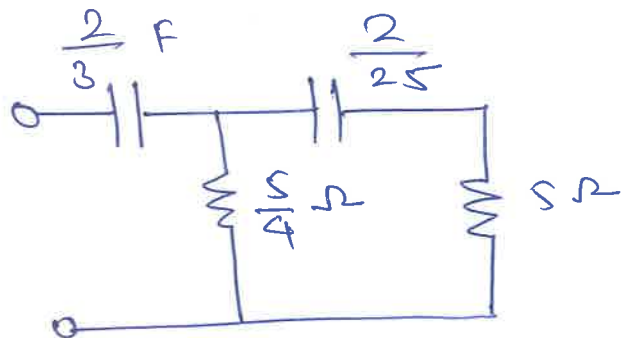

$$F(s) = \frac{4a}{s^3 + 8s^2 + 15s} \cdot \frac{1}{s^2 + 5s + 4}$$

The function has poles at $s = -1$ and $s = -4$ and zeros are at $s = 0$, $s = -3$ and $s = -5$

(b) There is no pole on $j\omega$ axis, hence residue test is not required


(c) $m_1 = 8s^2$ $n_1 = s^3 + 15s$
 $m_2 = s^2 + 4$ $n_2 = 5s$

$$A(\omega^2) = 3s^4 - 43s^2 \Big|_{s=j\omega}$$

$$= 3\omega^4 + 43\omega^2$$

$A(\omega^2)$ is positive for all $\omega \geq 0$

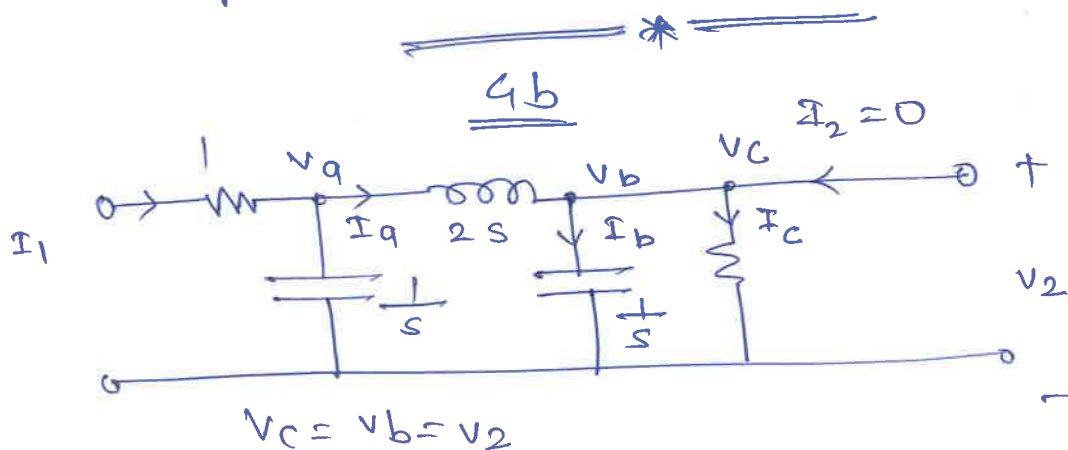All conditions are satisfied therefore the function is positive real.



$$I_a = sV_2 + V_2 = (s+1)V_2$$

$$V_a = 2sI_a + V_2$$


$$= (2s^2 + 2s + 1)V_2$$

$$I_1 = \frac{V_a}{\frac{1}{s}} + I_a = sV_a + I_a$$

$$= (2s^3 + 2s^2 + 2s + 1)V_2$$

$$V_1 = I_1 + V_a = (2s^3 + 2s^2 + 2s + 1)V_2 + (2s^2 + 2s + 1)V_2$$
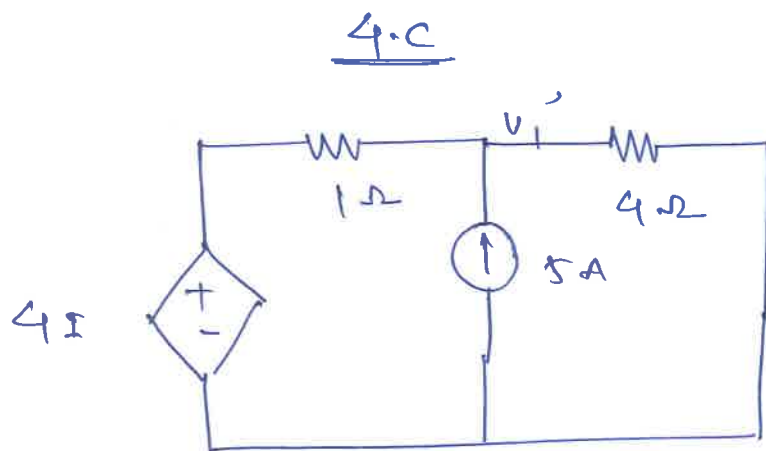
$$\frac{V_2}{V_1} = \frac{1}{2s^3 + 4s^2 + 4s + 2}$$




$$I = \frac{v_1'}{4}$$

$$\frac{v_1' - 4I}{1} + \frac{v_1'}{4} = 5 \quad (\text{KCL at node 1})$$

$$v_1' - 4\left(\frac{v_1'}{4}\right) + \frac{v_1'}{4} = 5$$

$$v_1' = 20\text{V}$$

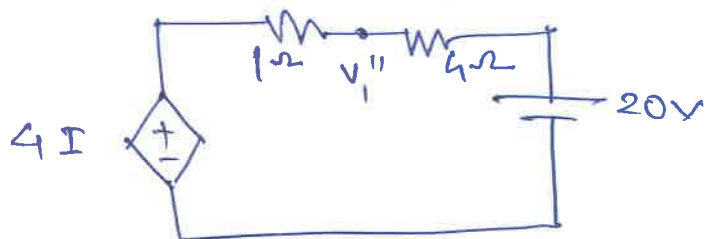Step - II when 20V source is acting alone



$$4I - I - 4I - 20 = 0$$

$$I = -20\text{A}$$

$$v_1'' = v_1' + v_1'' = 20 - 60 = -40\text{V}$$



So

At $t = 0^-$ no current flows the inductor and hence there is no voltage across the capacitor

$$i_L(0^-) = 0 \quad v_C(0^-) = 0$$

$$\text{At } t = 0^+, i_L(0^+) = 0 \quad v_C(0^+) = 0$$

for $t > 0$

$$\frac{V}{2} + \int_0^t v dt + 0.5 \times 10^{-6} \frac{dv}{dt} = 10 \quad \text{--- (1)}$$

At $t = 0^+$

$$\frac{v(0^+)}{2} + 0 + 0.5 \times 10^{-6} \frac{dv(0^+)}{dt} = 10$$

$$\frac{dv}{dt}(0^+) = 20 \times 10^6 \text{ V/s}$$

differentiating eqn (1)

$$\frac{1}{2} \frac{dv}{dt} + v + 0.5 \times 10^{-6} \frac{d^2v}{dt^2} = 0$$

At $t = 0^+$

$$\frac{1}{2} \frac{dv}{dt}(0^+) + v(0^+) + 0.5 \times 10^{-6} \frac{d^2v}{dt^2} v(0^+) = 0$$

$$\frac{d^2v}{dt^2}(0^+) = -20 \times 10^{12} \text{ V/s}^2$$



5b

$$Z = R + j\omega L = 15007 \angle 66.54^\circ \Omega/\text{km}$$

$$Y = G + j\omega C = 0.25 \times 10^{-6} + j2\pi \times 1000 \times 0.005 \times 10^{-6}$$

$$= 3.14 \times 10^{-5} \angle 89.54^\circ \text{ S/km}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = 692.77 \angle -11.5^\circ \Omega$$



$$\gamma = \sqrt{Z \cdot Y} = (4.55 \times 10^{-3} + j \cdot 0.022) / \text{km}$$

$$\alpha = 4.55 \times 10^{-3} \text{ nepers/km}$$

$$\beta = 0.022 \text{ rad/km}$$



5c

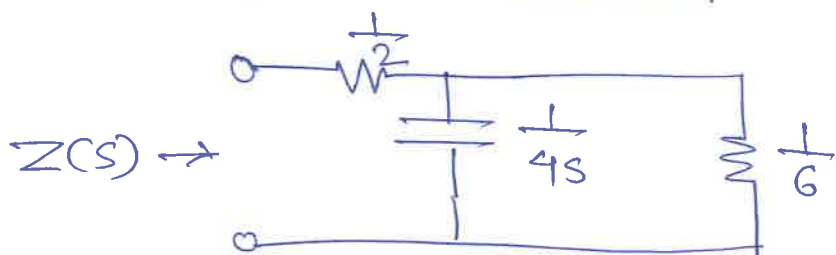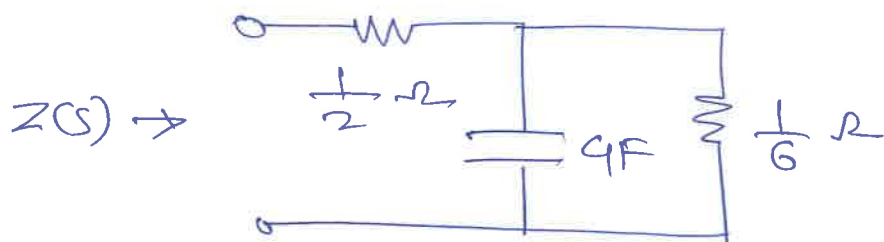

$$\begin{aligned}
 Z(s) &= \frac{1}{2} + \frac{\frac{1}{4s} \times \frac{1}{6}}{\frac{1}{4s} + \frac{1}{6}} \\
 &= \frac{4s+8}{2(4s+6)} = \frac{s+2}{2s+3} \\
 &= \frac{0.5(s+2)}{s+1.5}
 \end{aligned}$$

The function $Z(s)$ has zero at $s=-2$, and pole at $s=-1.5$

$$\underline{\underline{6a}}$$

$$Z_0 = 75 \Omega, \quad Z_L = 150 + j150 \Omega$$


$$\bar{Z}_L = \frac{150 + j150}{75} = 2 + j2$$

$$VSWR = 4.2$$

$$\Gamma = 0.62 \angle 30^\circ$$

6b

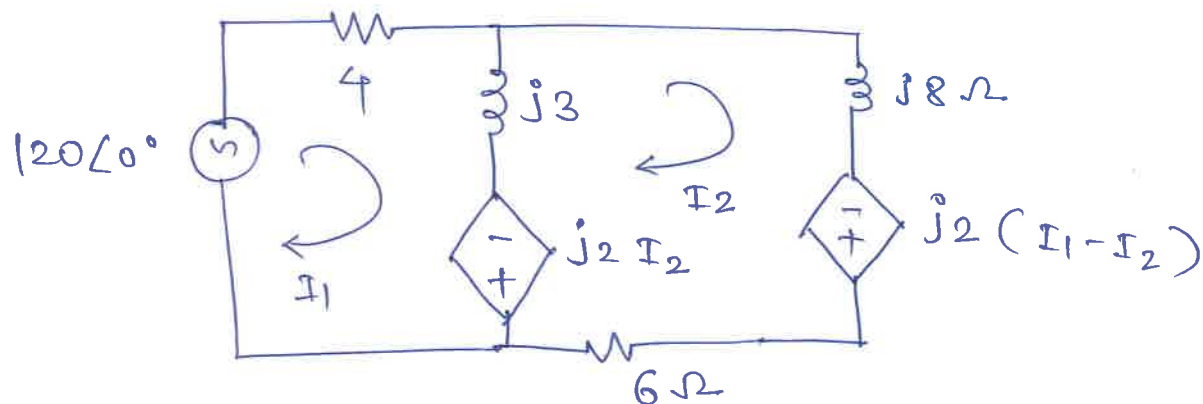The equivalent circuit in terms of dependent sources is shown below



Applying KVL to mesh - 1

$$120 \angle 0 - 4 I_1 - j3(I_1 - I_2) + j2 I_2 = 0$$

$$(4 + j3) I_1 - j5 I_2 = 120 \angle 0$$

Applying KVL to mesh 2

$$-j2 I_2 - j3 (I_2 - I_1) - j8 I_2 + j2 (I_1 - I_2) - 6 I_2 = 0$$

$$-j5 I_1 + (6 + j15) I_2 = 0$$

writing equations in matrix form

$$\begin{bmatrix} 4 + j3 & -j5 \\ -j5 & 6 + j15 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 120 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$I_2 = \frac{\begin{vmatrix} 4 + j3 & 120 \angle 0 \\ -j5 & 0 \end{vmatrix}}{\begin{vmatrix} 4 + j3 & -j5 \\ -j5 & 6 + j15 \end{vmatrix}} = 7.68 \angle 2.94^\circ \text{ A}$$





(c) Elements at initial conditions



circuit at $t = 0^+$



Elements with initial conditions

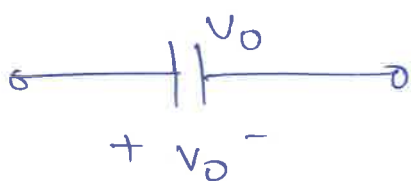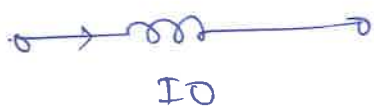

circuit at $t = \infty$

