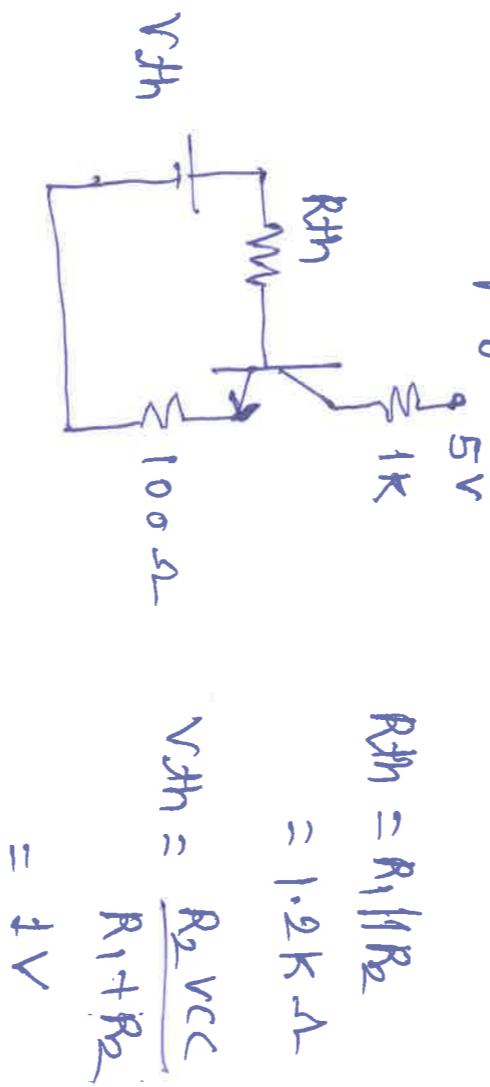


Solution . Q.P. Code : 36426

Que 2b :

①

Simplified circuit



KVL to input loop .

$$V_{BH} - I_B R_{BH} - V_{BE} - (1 + \beta) R_E = 0$$

Solving

$$I_B = \frac{1 - 0.7}{1.2 \times 10^3 + (101)(100)}$$

$$\therefore I_B = 26.54 \mu A$$

Let circuit is operating in Active region

$$\therefore I_C = \beta I_B$$
$$= 2.65 \text{ mA}$$

Applying KVL to O/P loop

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

Solving $V_{CE} = 2.14 \text{ V}$

02

Q.P. Code: 36426

Ques 3a:

$$K = \frac{I_{DQ}(ON)}{[V_{GS}(ON) - V_{GS}(TH)]^2}$$

$$\therefore K = \frac{3 \times 10^{-3}}{[10 - 5]^2}$$

$$K = 1.2 \times 10^{-4} \text{ A/V}^2$$

$$I_{DQ} = K [V_{GS} - V_{GS}(TH)]^2 \quad \text{--- (1)}$$

$$\begin{aligned} \text{but } V_{GS} &= V_G - I_D R_S \\ &= \frac{R_2 V_{DD}}{(R_1 + R_2)} - I_D R_S \end{aligned}$$

$$\therefore V_{GS} = 18 - 820 I_D \quad \text{--- (2)}$$

\therefore from eqnⁿ (1)

$$I_{DQ} = 1.2 \times 10^{-4} [18 - 820 I_D - 5]^2$$

$$\text{Solving } I_D = 6.69 \text{ mA} \quad \& \quad I_D = 37.4 \text{ mA}$$

\therefore selecting $I_D = 6.69 \text{ mA}$

from equation (2) $V_{GSQ} = 12.51 \text{ V}$

Apply KVL to o/p loop.

$$V_{DSQ} = V_{DD} - I_D (R_D + R_S)$$

$$V_{DSQ} = 14.44 \text{ V}$$