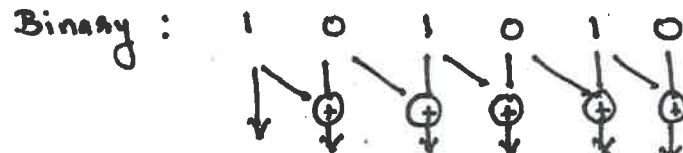


Solution
Digital Circuit Design.
Paper-1.

CP code: 27584

Q1 a) 1.

$$(42)_{10} = (101010)_2$$




Gray : 1 1 1 1 1 1

$$(42)_{10} = (111111)_{\text{Gray}}$$

----- 2½ marks

2. $(17)_{10} = (10001)_2$

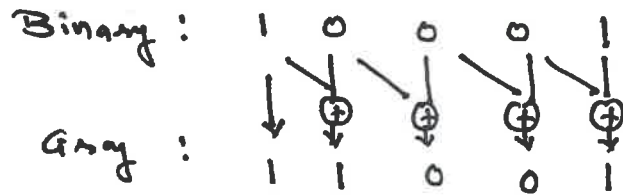

Gray : 1 1 0 0 1

$$(17)_{10} = (11001)_{\text{Gray}}$$

----- 2½ marks.

Q1 d)

Step 1) Write the truth table for conversion. The required truth table is obtained from excitation table is obtained from excitation table of JK & T flip flop.

Inputs				Outputs	
T	Present state Q_n	Next state Q_{n+1}	J	K	
0	0	0	0	X	
1	0	1	1	X	
1	1	0	X	1	
0	1	1	X	0	

← Excitation Table of TFF →

← Excitation Table of JK FF →

Step 2) K Map and simplification.

--- 2 marks

	Q_n	
T	0	1
0	0	X
1	1	X

J output

$$J = T$$


	Q_n	
T	0	1
0	X	0
1	X	1

K output

$$K = T$$

Step 3: Logic Diagram

--- 2 marks

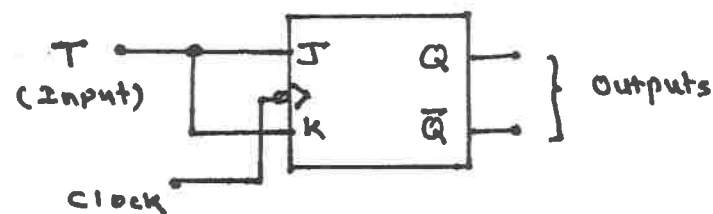


--- 1 mark.

Q 2 b)


$$F(A, B, C, D) = \sum m(0, 1, 4, 5, 6, 8, 10, 12, 13)$$

Design Table:

Inputs	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
Input Mux	1	\bar{A}	A	0	1	1	\bar{A}	0

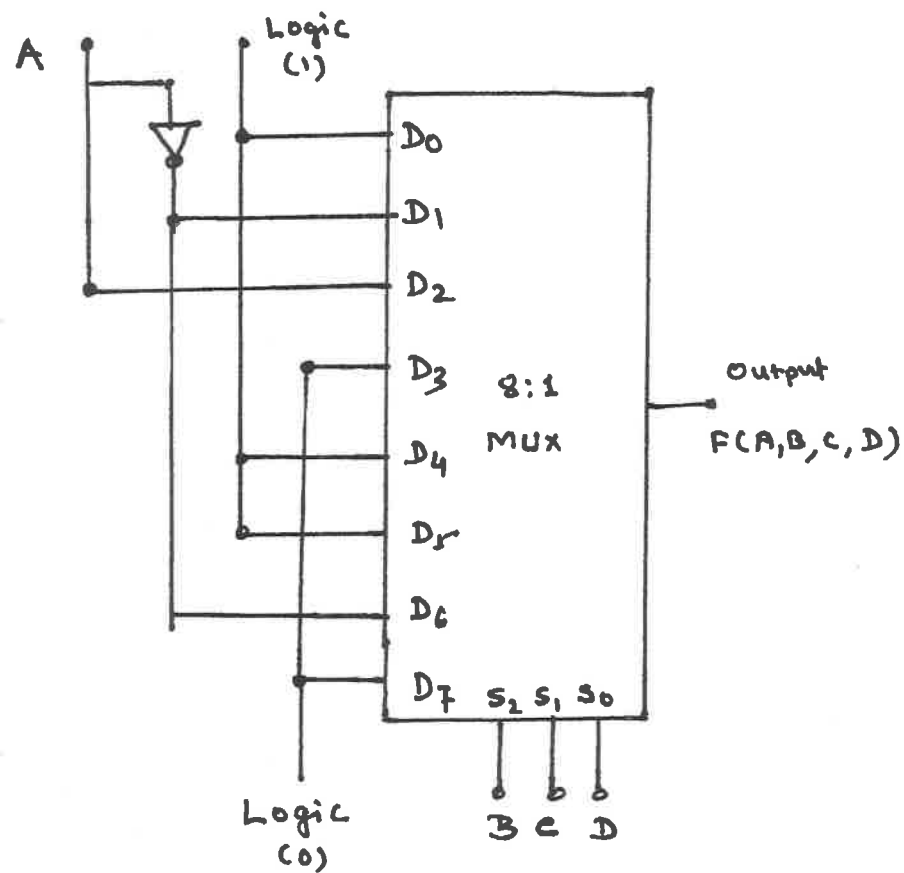

Q3 a) Johnson Counter :

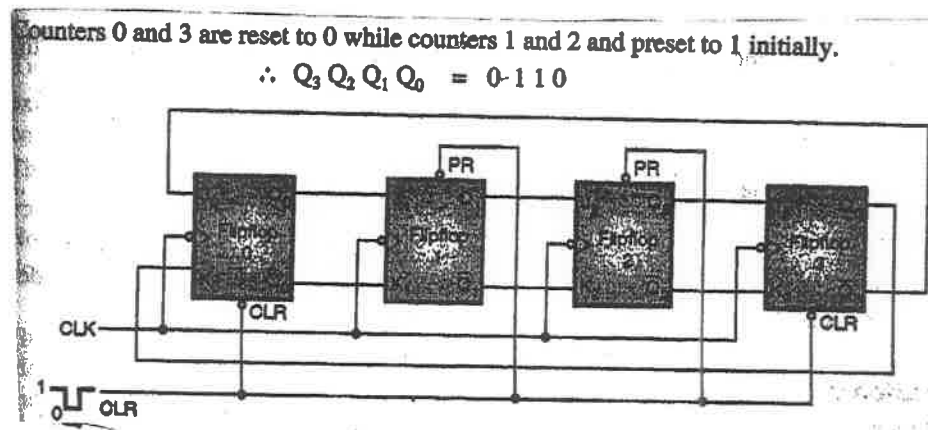

The other possible states of this Johnson's Counter are given below.

State	CLR	Q_3	Q_2	Q_1	Q_0
U	X	0	1	1	0
1	↓	1	1	0	1
1	↓	1	0	1	0
1	↓	0	1	0	0
1	↓	1	0	0	1

Q3 b)

Step 1) Group minterms --- number of 1's.

Group	Minterms	Binary Representation				
		A	B	C	D	
0	0	0	0	0	0	✓
1	1	0	0	0	1	
	2	0	0	1	0	✓
2	3	0	0	1	1	✓
	5	0	1	0	0	✓
	9	1	0	0	1	✓
3	7	0	1	1	1	✓
	11	1	0	1	1	✓

Step 2) Form Pairs

Group	Minterm Pairs	Binary Representation				
		A	B	C	D	
0	0, 1	0	0	0	-	✓
	0, 2	0	0	-	0	
1	1, 3	0	0	-	1	✓
	1, 5	0	-	0	1	
	1, 9	1	0	0	1	✓
	2, 3	0	0	1	-	
2	3, 7	0	-	1	1	✓
	3, 11	1	0	1	1	
		0	1	-	1	✓
		1	0	-	1	

Step 3) Group of four


Group	Minterms Quads	Binary Representation				
		A	B	C	D	
0	0, 1, 2, 3	0	0	-	-	} $\bar{A}\bar{B}$
	0, 2, 1, 3	0	0	-	-	
1	1, 3, 5, 7	0	-	-	1	} $\bar{A}D$
	1, 5, 3, 7	0	-	-	1	
	1, 3, 9, 11	-	0	-	1	} $\bar{B}D$
	1, 9, 3, 11	-	0	-	1	

(9)

Step 4) Prime implicants

Prime Implicants	Decimal Number	Given Minterms							
		0	1	2	3	5	7	9	11
$\bar{A}\bar{B}C$	2, 3			x	x				
$\bar{B}CD$	3, 11				x				x
$\bar{A}\bar{B}$	0, 1, 2, 3	(x)	x	x	x				
$\bar{A}D$	1, 3, 5, 7		x		x	(x)	(x)		
$\bar{B}D$	1, 3, 9, 11		x		x			(x)	x

Step 5) K Map. verification.

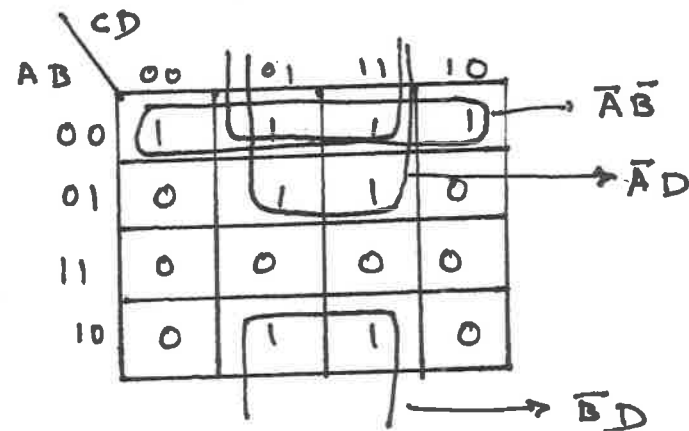

$$F(A, B, C, D) = \bar{A}\bar{B} + \bar{A}D + \bar{B}D$$

Q4 b).

1. Prove That.

$$\bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z} + \bar{W}XY\bar{Z} + WY\bar{Z} = Z$$

Solution:

$$\begin{aligned} \text{L.H.S.} &= \bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z} + \bar{W}XY\bar{Z} + WY\bar{Z} \\ &= \bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z}(1+Y) + \bar{W}XY\bar{Z} + WY\bar{Z} \\ &= \bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z} + \bar{W}\bar{X}Y\bar{Z} + \bar{W}XY\bar{Z} + WY\bar{Z} \\ &= \bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z} + \bar{W}Y\bar{Z}(\bar{X}+X) + WY\bar{Z} \\ &= \bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z} + \bar{W}Y\bar{Z} + WY\bar{Z} \\ &= \bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z} + Y\bar{Z}(\bar{W}+W) \\ &= \bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Z} + Y\bar{Z} \\ &= \bar{Y}\bar{Z} + Y\bar{Z} + \bar{W}\bar{X}\bar{Z} \\ &= \bar{Z}(\bar{Y}+Y) + \bar{W}\bar{X}\bar{Z} \\ &= \bar{Z} + \bar{W}\bar{X}\bar{Z} \\ &= \bar{Z} + (1+\bar{W}\bar{X}) \\ &= \bar{Z} \cdot 1 \\ &= \bar{Z} = \text{R.H.S.} \end{aligned}$$

2. Simplify equation

$$\begin{aligned} &[\bar{A}\bar{B}(C+BD) + \bar{A}\bar{B}]C \\ &(\bar{A}\bar{B}C + \bar{A}\bar{B}BD + \bar{A}\bar{B})C \\ &(\bar{A}\bar{B}C + 0 + \bar{A}\bar{B})C \\ &(\bar{A}\bar{B}C + \bar{A}\bar{B})C \\ &\bar{A}\bar{B}CC + \bar{A}\bar{B}C \\ &\bar{A}\bar{B}C + \bar{A}\bar{B}C \\ &\bar{B}C(A + \bar{A}) \\ &\bar{B}C \cdot 1 \\ &\bar{B}C \end{aligned}$$

Q.5. b) BCD Adder using 4bit binary adder.

