

Q.1 a) $I_x = I_1 - I_2$ — (1)

For loop (1)

$$50I_1 - 40I_2 - 10I_3 = 100$$
 — (2)

For loop (2)

$$60I_2 - 40I_1 - 20I_3 = -50I_x$$
 — (3)

$$= 10I_1 + 10I_2 - 20I_3 = 0$$
 — (3)

For loop (3)


$$60I_3 - 10I_1 - 20I_2 = 0$$
 — (4)

Solving eq^{ns} we get

$$I_1 = 0.74, I_2 = -1.48, I_3 = -0.37$$

$$I_{20} = I_3 - I_2 = \boxed{1.11 \text{ A}}$$

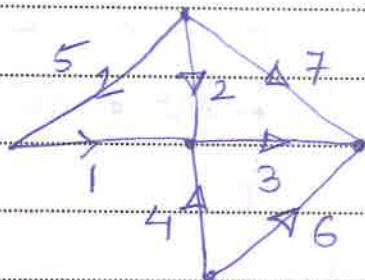- c) cutset 1: {1, 5}
 2: {2, 5, 7}
 3: {3, 6, 7}
 4: {4, 6}



e) $I_1 = \frac{V_1 - V_3}{1} = V_1 - V_3$ — (1)

KCL at node (3) $\Rightarrow I_1 = \frac{V_3}{2} + \frac{V_3 - V_2}{2} = V_3 - \frac{V_2}{2}$ — (2)

KCL at node (2) $I_2 = \frac{V_2}{4} + \frac{V_2 - V_3}{2} = \frac{3}{4}V_2 - \frac{V_3}{2}$ — (3)

\therefore eqⁿ (1) & (2) \Rightarrow

$$V_3 = \frac{V_1}{2} + \frac{V_2}{4}$$
 — (4)


Using eqⁿ (4) in eqⁿ (2) $I_1 = \frac{V_1}{2} - \frac{V_2}{4}$ — (5)

Using eqⁿ (4) in eqⁿ (3) $I_2 = -\frac{V_1}{4} + \frac{5}{8}V_2$ — (6)

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 1/2 & -1/4 \\ -1/4 & 5/8 \end{bmatrix}$$

Q.2 a) For V_{th}


a)

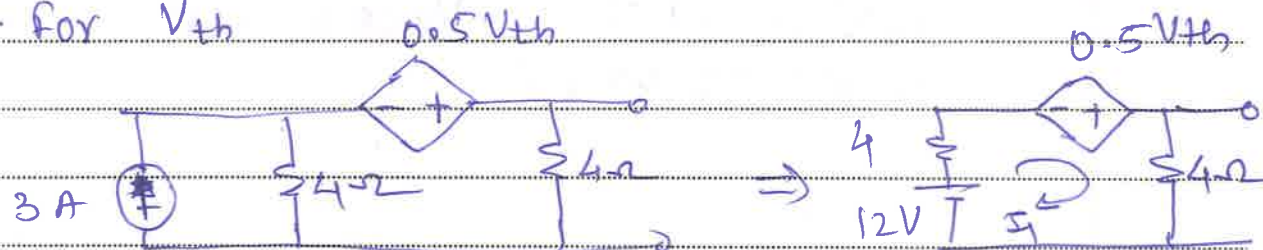

$$\therefore V_{th} = 4I$$

$$I = 2$$


$$\therefore \boxed{V_{th} = 8 \text{ V}}$$

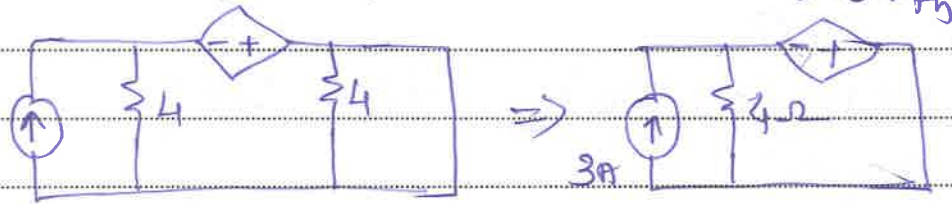For I_{sc} $0.5V_{th}$ 

$$\therefore V_{th} = 0 \quad \therefore I_{sc} = 3A$$


$$\therefore R_{th} = \frac{V_{th}}{I_{sc}} = \frac{0}{3} = 0 \Omega$$

$$\therefore R_L = R_{th} = 0 \Omega$$

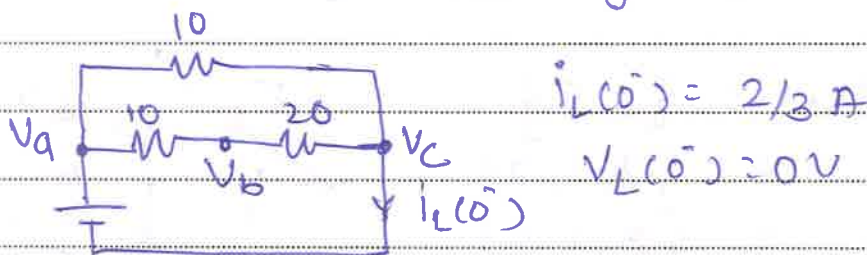(b) at $t=0$ \therefore ckt is already stable

$$V_a = 5V, \quad V_b = 3.33V, \quad V_c = 0$$

$$\therefore V_a(0^-) = 5V, \quad V_b(0^-) = 3.33V$$

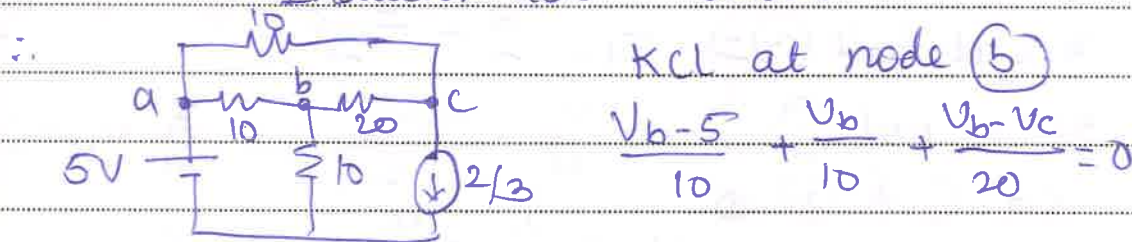at $t=0^+$ Inductor acts as current source.

$$\text{KCL at node (b)}$$

$$\frac{V_b - 5}{10} + \frac{V_b}{10} + \frac{V_b - V_c}{20} = 0$$

$$\therefore \text{at } t=0^+ \quad 2V_b(0^+) - 10 + 2V_b(0^+) + V_b(0^+) = 0$$

KCL at node (c)

$$\frac{V_c(0^+) - V_b(0^+)}{20} + \frac{V_c(0^+) - 5}{10} + \frac{2}{3} = 0 \quad \text{--- (2)}$$


 \therefore Solving eqⁿ

$$V_b(0^+) = 1.9V \quad V_a(0^+) = 5V$$

$$V_c(0^+) = -0.476V$$


03

Q.3 a) To find I_{sc}

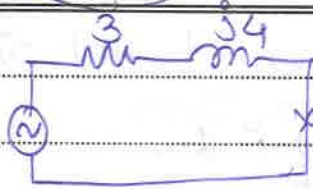

$I_{sc} \therefore I_{sc} = 5 \angle -53.13^\circ$

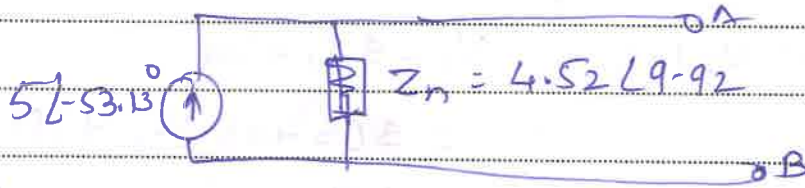$Z_n = 4.46 + j0.78 = 4.52 \angle 9.92^\circ \Omega$



(b)

$I(-j5) = 13.41 \angle 26.56^\circ \text{ A}$ using CDR

$\therefore V_{th} = -j5 \times I$

$= 67.08 \angle -63.43^\circ \text{ V}$

$\therefore Z_{th} = (5 + j15) \parallel (-j5)$


$= 7.07 \angle -81.86^\circ \Omega$



(c)


at $t=0^-$ $i_L(0^-) = 0$ $V_C(0^-) = 0$

at $t=0^+$

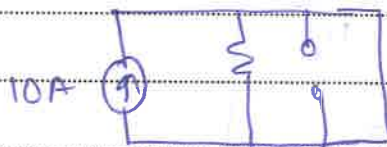

$\therefore i_L(0^+) = 0$
 $V_C(0^+) = 0$

at $t > 0$

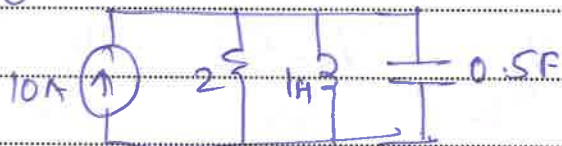

\therefore Applying KCL $10 = \frac{V_A}{2} + \int_{-\infty}^t v dt + 0.5 \mu F \frac{dv}{dt}$ (1)

\therefore at $t=0^+$

$10 = \frac{V(0^+)}{2} + \int_{-\infty}^t v(0^+) dt + 0.5 \times 10^{-6} \frac{dV(0^+)}{dt}$

$\therefore \boxed{\frac{dV(0^+)}{dt} = 20 \times 10^6 \text{ V/s}}$


diff. eqⁿ

(1) $\Rightarrow 0 = \frac{1}{2} \frac{dV}{dt} + V + 0.5 \mu F \frac{d^2V}{dt^2}$

$\therefore \boxed{\frac{d^2V}{dt^2} = -20 \times 10^{12} \text{ V/s}^2}$

04

Q.4 (a) The transformed network is.

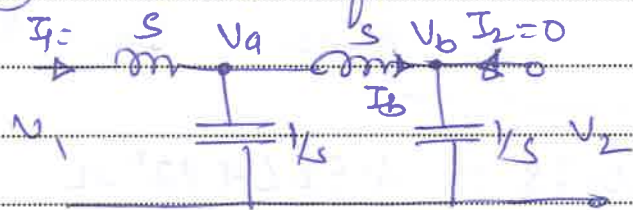

$$V_b = V_2$$

$$I_b = sV_2 \quad \because V_2 / 1/s$$

$$V_a = I_b + V_2$$

$$= s(sV_2) + V_2$$

$$= s^2 V_2 + V_2$$

$$= (s^2 + 1)V_2$$

$$I_1 = \frac{V_a}{1/s} + I_b$$

$$= sV_a + I_b$$

$$= (s^3 + 2s)V_2$$

$$V_1 = sI_1 + V_a$$

$$= s(s^3 + 2s)V_2 + (s^2 + 1)V_2$$

$$= (s^4 + 3s^2 + 1)V_2$$

$$\therefore \frac{V_1}{I_1} = \frac{s^4 + 3s^2 + 1}{s^3 + 2s}$$


$$\frac{V_2}{V_1} = \frac{1}{s^4 + 3s^2 + 1}$$

$$\frac{V_2}{I_1} = \frac{1}{s^3 + 2s}$$

Q.4 (b) at $t=0^-$

$$V_c(0^-) = 5V$$

at $t \geq 0$ the transformed ckt is

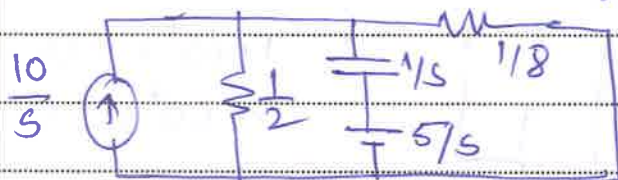

Using KCL

$$\frac{10}{s} = \frac{V_s}{1/2} + \frac{V_s - 5/s}{1/s} + \frac{V_s}{1/8}$$

$$\therefore 10 = s(s+5)V_s \quad \text{--- (1)}$$

$$\therefore V_s = \frac{10}{s(s+5)} = \frac{A}{s} + \frac{B}{s+5}$$

$$\therefore A|_{s=0} = \frac{10 \cdot s}{s+5} = 2$$

$$B|_{s=-5} = -2$$

$$\therefore V_s = \frac{2}{s} - \frac{2}{s+5}$$

$\therefore L^{-1}$ is


$$V(t) = 2 - 2e^{-5t}$$

Q. 5(a) $A_a = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & -1 & -1 & -1 & -1 \end{bmatrix}$

Q. $\begin{bmatrix} 1 & -1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & -1 & 1 & 1 & 0 & 0 \\ 0 & -1 & 0 & 0 & 0 & 0 & 1 & 1 \end{bmatrix}$

$B = \begin{bmatrix} 1 & 1 & 0 & 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 & -1 & 0 \\ 1 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & -1 & 0 \end{bmatrix}$

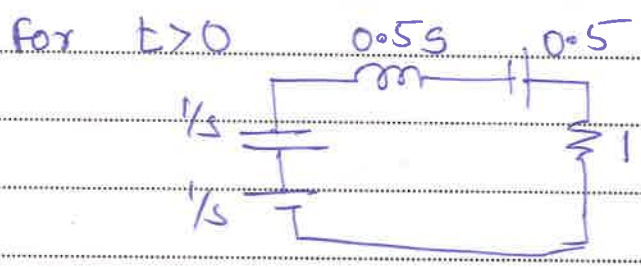(b) at $t=0^-$ $V_C(0^-) = 1V$ $i(0^-) = 1A$
 \therefore $V_C(0^+) = 1V$ $i(0^+) = 1A$



\therefore Applying KVL we get $\frac{1}{s} - \frac{1}{s} I(s) - 0.5s I(s) + 0.5 + I(s) = 0$

$$I(s) = \frac{s+2}{s^2+2s+2} = \frac{(s+1)+1}{(s+1)^2+1} = \frac{s+1}{(s+1)^2+1} + \frac{1}{(s+1)^2+1}$$

$L^{-1} \Rightarrow i(t) = e^{-t} \cos t + e^{-t} \sin t \text{ A}$

