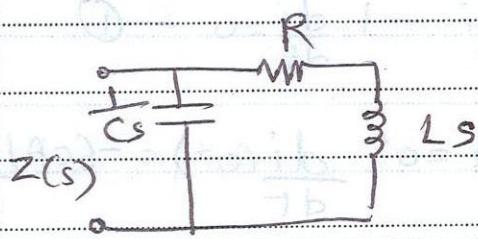


Q.P. code: 27433



The transformed network
is shown.


$$Z(s) = \frac{(R + Ls) \frac{1}{Cs}}{\frac{1}{Cs} + (R + Ls)}$$

$$Z(s) = \frac{1}{C} \frac{s + \frac{R}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

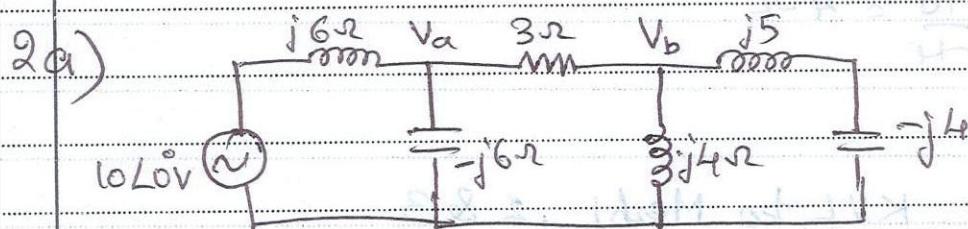c) By continued fraction expansion

quotients are:- $\frac{s}{7}, \frac{1}{3}, \frac{9}{7}, \frac{1}{24}$

Since all quotients are positive, $P(s)$ is Hurwitz.



KCL at node a :-



$$0.33V_a - 0.33V_b = 1.67 \angle -90^\circ \quad \text{--- (1)}$$

KCL at node b :-


$$-0.33V_a + (0.33 - j1.25)V_b = 0 \quad \text{--- (2)}$$

$$\therefore V_a = 5.24 \angle -75.17^\circ \text{ V}$$

2b) At $t=0^-$

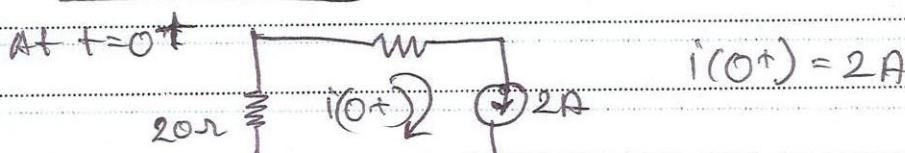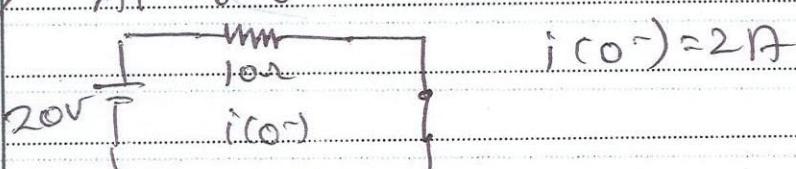

For $t > 0$ KVL

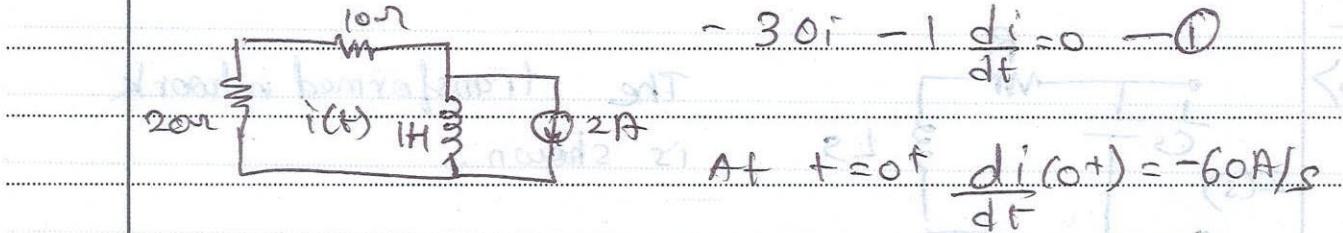

Differentiating eqⁿ(1) :- & at $t=0^+$

$$\frac{d^2i}{dt^2}(0^+) = 1800 \text{ A/s}^2$$

$$Q3a) V_x = 4V$$

$$V_{TH} = V_x - 5V_x = -4V_x = -16V$$

I_{SC}:- Applying KCL at node

$$V_x = -4V$$

$$I_{SC} = \frac{V_x - 5V_x}{R_{TH}} = -4$$

$$R_{TH} = \frac{16}{4} = 4\Omega$$

Q3b) Applying KVL to Mesh 1, 2 & 3

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 5 & 1 \\ -1 & 3 \end{bmatrix}$$

h parameters :-

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{16}{3} & \frac{1}{3} \\ \frac{1}{3} & \frac{1}{3} \end{bmatrix}$$

Q4
a) 30V source alone:-

$$I_x' = -\frac{V_1}{5}$$

KCL at node:-

$$I_x' = 3A (\rightarrow)$$

20V source is alone:-

KVL to mesh:- $I_x'' = 2A (\rightarrow)$

By Superposition theorem:-


$$I_x = I_x' + I_x''$$

$$I_x = 3 + 2 = 5A (\rightarrow)$$

Q4b) $Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$

Foster I:- By partial fraction exp.

$$Z(s) = \frac{\left(\frac{3}{8}\right)}{s} + \frac{\left(\frac{1}{4}\right)}{s+2} + \frac{\left(\frac{3}{8}\right)}{s+4}$$

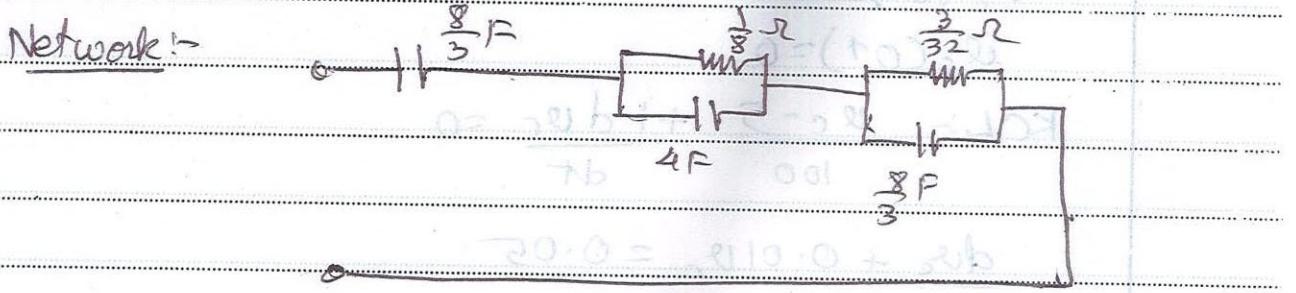


Foster II:- $\frac{Y(s)}{s} = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$

By division. $\frac{Y(s)}{s} = 1 + \frac{2s + 5}{(s+1)(s+3)}$

By partial fraction exp.
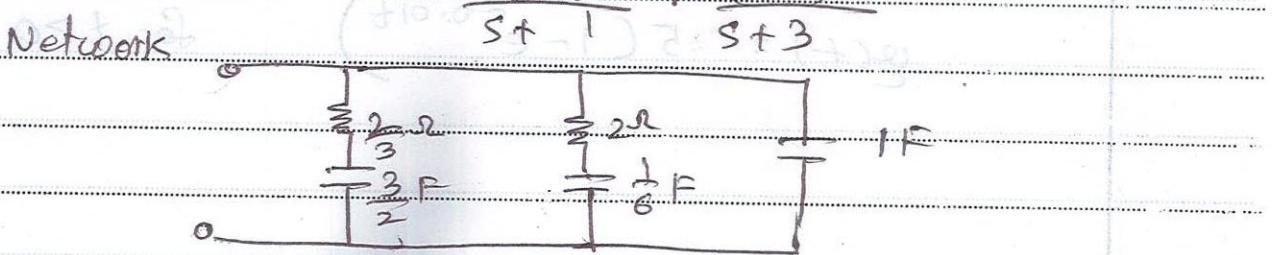
$$Y(s) = s + \frac{\left(\frac{3}{2}\right)s}{s+1} + \frac{\left(\frac{1}{2}\right)s}{s+3}$$



$$Q5b) i) I_1 = V_1 - V_3 \quad \text{--- (1)}$$

$$I_2 = \frac{V_2 - V_3}{3} \quad \text{--- (2)}$$

$$\text{KCL} : I_1 + I_2 = \frac{V_3}{2} \quad \text{--- (3)}$$

Substituting eqn (1) & (2) in (3).

$$V_3 = \frac{6V_1 + 2V_2}{11} \quad \text{--- (4)}$$

eqn (4) in (1).

$$I_1 = \frac{5V_1 - 2V_2}{11}$$

Substitution (4) in (2)

$$I_2 = \frac{-2V_1 + 3V_2}{11}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{5}{11} & -\frac{2}{11} \\ -\frac{2}{11} & \frac{3}{11} \end{bmatrix}$$

5b ii)

$$v_c(0^-) = 0$$

$$v_c(0^+) = 0$$

$$\text{KCL} : \frac{v_c - 5}{100} + \frac{1}{1} \frac{dv_c}{dt} = 0$$

$$\frac{dv_c}{dt} + 0.01v_c = 0.05$$

Solution of this differential equation :-

$$v_c(t) = \frac{Q}{P} + K e^{-Pt}$$

$$= 5 + K e^{-0.01t}$$

$$\text{At } t=0, v_c(0)=0 \quad \therefore K = -5$$

$$v_c(t) = 5(1 - e^{-0.01t}) \quad \text{for } t > 0$$

$$26) F(s) = \frac{s^2 + 1}{s^3 + 4s} = \frac{(s+j1)(s-j1)}{s(s+j2)(s-j2)}$$

poles at $s=0, -j2, j2$

zeros at $s=-j1, j1$

Residue test :-

$$F(s) = \frac{K_1}{s} + \frac{K_2}{s+j2} + \frac{K_2^*}{s-j2}$$

$$K_1 = \frac{1}{4}, \quad K_2 = \frac{3}{8}, \quad K_2^* = \frac{3}{8}$$

Residues are real & positive

$$\cdot A(\omega^2) = m_1 m_2 - n_1 n_2 \Big|_{s=j\omega} \\ = 0.$$

$A(\omega^2)$ is zero for all $\omega \geq 0$

Since all 3 test conditions are satisfied, function
is positive real.

(472) (442) = 14² - 2 · (2) 7

(27-3)(37+2)2 = 24+22

51.5' S 132° E along

W. Bank of R. to 1055

at bridge

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924

104 + 19 = 924