

01

Q.P. 25858

T.E. Biomedical Engineering.
Sem -V (CBSGS)
Analog and Digital Circuit Design (*Solution*)


Q1 Attempt any **Four** of following. [20]

- MOSFET structure – 01 mark, working – 02 marks, characteristics -02 marks
- Block diagram – 02 marks and Explanation of block diagram – 03 marks.
- Types of analog switches – 05marks
- Any 4 points with examples – 01 mark each.- 05 marks
- GIC explanation – 03 marks and Examples – 02 marks
- PLL block diagram – 02 marks, Explanation of block diagram -02 marks and list applications – 01 marks.

Q2 a. Functional Block diagram of IC8038 –02 mark, Explanation – 03 marks. [05]

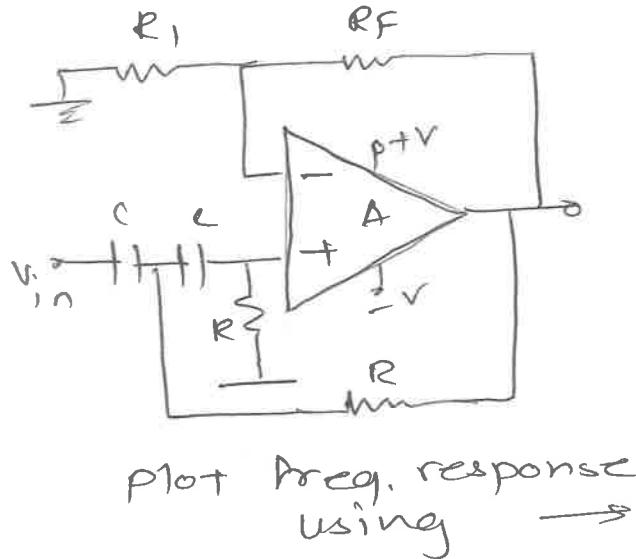b. A 2nd order Butterworth high pass filter for $f = 1.5 \text{ KHz}$ and also plot its frequency response. [05]

Circuit Diagram –01 mark, Solution – 02 marks, Plotting frequency response – 02 marks.



$$A_F = 1.586 = \text{passband gain}$$

for 2nd order Butterworth response

$$A_F = 1 + \frac{RF}{R_1}$$

$$f = \frac{1}{2\pi RC} = 1.5k$$

Assume, C then find R

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (f_L/f)^4}}$$

c. Functional Block Diagram –04 mark, Explanation – 03 marks. [10]
Explanation for pin 2 and 5 – 03 marks

Q3 a. SCR Diagram –02 mark, equivalent model – 02 marks, Explanation – 04 marks. [08]

b. Design an Instrumentation Amplifier using AD620 for gain of 650 and explain its applications. [06]


Circuit Diagram –02 mark, Design for gain – 02 marks, application – 02 marks.

(Q2)

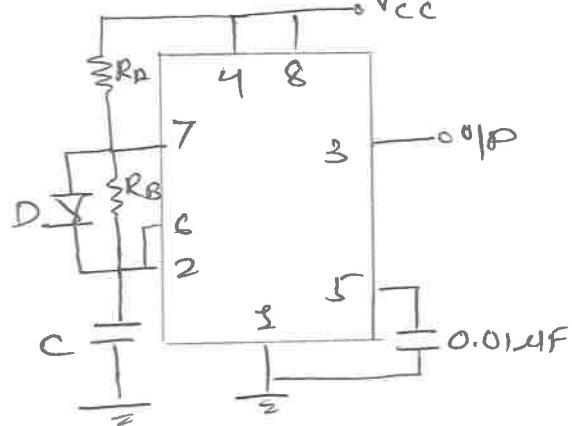c. Design a timer for Duty cycle 40% for $T_{on} = 0.8\text{ms}$. Draw corresponding waveforms. [06]

Circuit Diagram -01 mark, Solution for RA, RB, C - 03 marks.

Waveforms for V_o (showing T_{on} and T_{off}) and capacitor - 02 marks



As Duty cycle is less than 50%, diode is used to bypass R_B during charging of capacitor i.e. during T_{on} .

$$T = T_{on} + T_{off}$$

$$D = \frac{T_{on} \times 100}{T} = 40$$

$$\text{As } T_{on} = 0.8\text{ms} \Rightarrow T = 2\text{ms}$$

$$T_{off} = 1.2\text{ms}$$

$$T_{on} = 0.693 R_A C$$

$$T_{on} = 0.693 R_B C$$

$$\text{Assume, } C = 0.1\mu\text{F}$$

$$\therefore R_A = 17.32\text{k}\Omega \approx 18\text{k}$$

$$R_B = 11.54\text{k}\Omega \approx 12\text{k}$$

Q4 a. Comparison between active and passive (3 points) -02 marks [10]
KRC filter circuit – 2 marks, Explanation – 02 marks, Derivation of Q – 04 marks

b. Lock Range – 02 marks, Capture range – 02 marks [05]
Pull in time – 01 marks.

c. Missing pulse circuit diagram -01 mark, working – 02 marks, waveforms– 02 marks [05]

Q5 a. Equation for $V_o = 01$ mark and $I_{sc} - 01$ mark and solution – 03 marks

[05]

$$I_{sc} = \frac{V_{source}}{R_{sc}}$$

$$V_o = V_{N3} = V_{ref} \frac{R_2}{R_1 + R_2}$$

$$R_3 = R_1 // R_2$$

$$V^+ = V_{cc} = V_{in} = 15 \pm 20V$$

b. UJT Relaxation oscillator circuit diagram – 02 mark, working – 02 marks,
Derivation for Frequency – 03 marks

[07]

c. Stepper motor diagram – 03 mark, working – 05 marks.

[08]

Q6. Attempt any **Four** of following:-

[20]

a) Explain FSK using IC 555

Diagram – 02 marks ,Explanation- 03 marks

b) Short note on :Switching Mode Power Supply

Diagram – 02 marks ,Explanation- 03 marks

c) Short note on :Opto –Isolators and Opto -Couplers

Diagram – 02 marks ,Explanation- 03 marks

d) Draw Symbol, structure and characteristics of DIAC and TRIAC.

symbol – 01 mark ,structure -02 marks, Characteristicsn- 02 marks

e) Draw Frequency response of Butterworth, Chebyshev and Elliptical filters and compare them.
frequency response – 02 marks , Comparison- 03 marks