

Q1-1 (a)

$$1) Q(s) = s^5 + s^3 + s$$

Solution:- Since the given polynomial contains odd functions only, it is not possible to perform CFE

$$Q'(s) = \frac{d}{ds} Q(s) = 5s^4 + 3s^2 + 1$$

By CFE

$$5s^4 + 3s^2 + 1 \bigg) s^5 + s^3 + s \left(\frac{1}{5}s \right.$$

$$s^5 + \frac{3}{5}s^3 + \frac{1}{5}s$$

$$\hline \frac{2}{5}s^3 + \frac{4}{5}s \bigg) 5s^4 + 3s^2 + 1 \left(\frac{2s}{5} \right.$$

$$5s^4 + 10s^2$$

$$\hline -7s^2 + 1 \bigg) \frac{2}{5}s^3 + \frac{4}{5}s \left(-\frac{2}{35}s \right.$$

Since quotient term is negative, $Q(s)$ is not Hurwitz

$$2) Q(s) = s^4 + 6s^3 + 8s^2 + 10$$

In the given polynomial, the term s is missing and it is neither an even nor an odd polynomial. Hence, it is not Hurwitz

d Y-Parameter in terms of Z-Parameter

we know that,

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

By Cramer's Rule,

$$I_1 = \frac{\begin{vmatrix} V_1 & Z_{12} \\ V_2 & Z_{22} \end{vmatrix}}{\begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}}} = \frac{Z_{22} V_1 - Z_{12} V_2}{Z_{11} Z_{22} - Z_{12} Z_{21}} = \frac{Z_{22}}{\Delta Z} V_1 - \frac{Z_{12}}{\Delta Z} V_2$$

$$\text{Where } \Delta Z = Z_{11} Z_{22} - Z_{12} Z_{21}$$

$$\text{Comparing with } I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$Y_{11} = \frac{Z_{22}}{\Delta Z} \quad \& \quad Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

$$\text{Also, } I_2 = \frac{\begin{vmatrix} Z_{11} & V_1 \\ Z_{21} & V_2 \end{vmatrix}}{\Delta Z} = \frac{Z_{11} V_2 - Z_{12} V_1}{\Delta Z} = -\frac{Z_{12}}{\Delta Z} V_1 + \frac{Z_{11}}{\Delta Z} V_2$$

$$\text{Comparing with } I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{21} = -\frac{Z_{12}}{\Delta Z} \quad Y_{22} = \frac{Z_{11}}{\Delta Z}$$

Q1-2

(2)

$$(a) \quad Z(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

$$Z(s) = \frac{3[s^2 + 6s + 8]}{s^2 + 3s} = \frac{3s^2 + 18s + 24}{s^2 + 3s}$$

$$\begin{array}{r} s^2 + 3s \overline{) 3s^2 + 18s + 24} \quad (3) \\ \underline{3s^2 + 9s} \\ 9s + 24 \end{array}$$

$$Z(s) = 3 + \frac{9s + 24}{s(s+3)}$$

$$\begin{array}{ccc} \downarrow & & \downarrow \\ Z_1(s) & & Z_2(s) \end{array}$$

$$Z_2(s) = \frac{9s + 24}{s(s+3)}$$

$$\frac{9s + 24}{s(s+3)} = \frac{A}{s} + \frac{B}{s+3}$$

$$9s + 24 = A(s+3) + Bs$$

$$\text{Put } s = 0$$

$$24 = A(3)$$

$$\boxed{A = 8}$$

$$\text{Put } s = -3$$

$$-27 + 24 = -3B$$

$$-3 = -3B$$

$$\boxed{B = 1}$$

$$Z_2(s) = \frac{8}{s} + \frac{1}{s+3}$$


$$Z(s) = 3 + \frac{8}{s} + \frac{1}{s+3}$$

$$\begin{array}{ccc} \downarrow & \downarrow & \downarrow \\ z_1 & z_2 & z_3 \end{array}$$

$$z_1 = 3 \rightarrow R = 3\Omega$$

$$z_2 = \frac{8}{s} \rightarrow \frac{1}{Cs} \Rightarrow C = \frac{1}{8} F$$
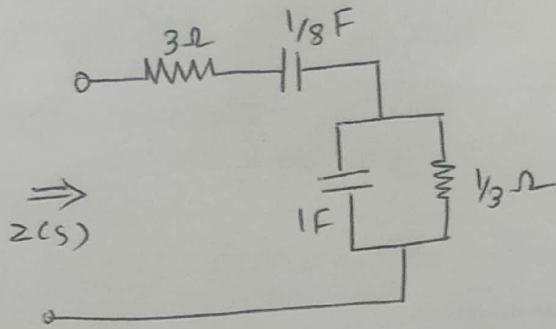
$$z_3 = \frac{1}{s+3} \Rightarrow Y_3 = \frac{s+3}{s} \begin{matrix} \downarrow \\ CS \\ C=1F \end{matrix} \quad \begin{matrix} \downarrow \\ R = \frac{1}{3}\Omega \end{matrix}$$



Foster! - II

$$Y(s) = \frac{s^2 + 3s}{3s^2 + 18s + 24}$$

$$\begin{array}{r} 3s^2 + 18s + 24 \) \ s^2 + 3s \ (1/3) \\ \underline{-(s^2 + 6s + 8)} \\ -3s - 8 \end{array}$$

$$\frac{Y(s)}{s} = \frac{s(s+3)}{3s(s+2)(s+4)}$$

$$\frac{Y(s)}{s} = \frac{1}{3} \left[\frac{A}{s+2} + \frac{B}{s+4} \right]$$

$$\frac{s(s+3)}{s(s+2)(s+4)} = \frac{1}{3} \left[\frac{A}{s+2} + \frac{B}{s+4} \right]$$

$$\frac{s+3}{(s+2)(s+4)} = \frac{A}{s+2} + \frac{B}{s+4}$$

$$s+3 = A(s+4) + B(s+2)$$

$$\text{Put } s = -4$$

$$-1 = B(-2)$$

$$\boxed{B = 1/2}$$

$$\text{Put } s = -2$$

$$1 = A(2)$$

$$\boxed{A = 1/2}$$

$$\frac{Y(s)}{s} = \frac{1}{3} \left[\frac{1/2}{s+2} + \frac{1/2}{s+4} \right]$$

$$\frac{Y(s)}{s} = \frac{1}{6} \left[\frac{1}{s+2} + \frac{1}{s+4} \right]$$

$$Y(s) = \frac{s}{6(s+2)} + \frac{s}{6(s+4)}$$

\downarrow \downarrow
 Y_1 Y_2

$$Y_1 = \frac{s}{6s+12} \Rightarrow Z_1 = \frac{6s+12}{s} = 6 + \frac{12}{s}$$

$$\downarrow \quad \downarrow$$


$$R=6\Omega \quad \frac{1}{Cs} = C \Rightarrow \frac{1}{12} F$$

$$Y_2 = \frac{s}{6s+24} \Rightarrow Z_2 = \frac{6s+24}{s} \Rightarrow 6 + \frac{24}{s}$$

$$\downarrow \quad \downarrow$$

$$R=6\Omega \quad \frac{1}{Cs} = C = \frac{1}{24} F$$

Foster II:-

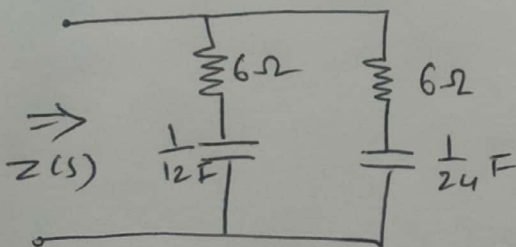

$$(b) Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

Cauer - I

$$Z(s) = \frac{s^2 + 4s + 3}{s^2 + 2s}$$

By CFE


$$(s^2 + 2s) \overline{s^2 + 4s + 3} \quad (1 \rightarrow Z = 1\Omega)$$

$$\begin{array}{r} \underline{s^2 + 2s} \\ 2s + 3 \end{array} \overline{s^2 + 2s} \left(\frac{s}{2} \rightarrow Y = Cs \Rightarrow C = \frac{1}{2}F \right)$$

$$\begin{array}{r} \underline{s^2 + \frac{3}{2}s} \\ \frac{1}{2}s \end{array} \overline{2s + 3} \quad (4 \rightarrow Z = 4\Omega)$$

$$\begin{array}{r} \underline{2s} \\ 3 \end{array} \overline{\frac{1}{2}s} \left(\frac{s}{6} \rightarrow Y = Cs = C = \frac{1}{6}F \right)$$

$$\begin{array}{r} \underline{\frac{1}{2}s} \\ 0 \end{array}$$

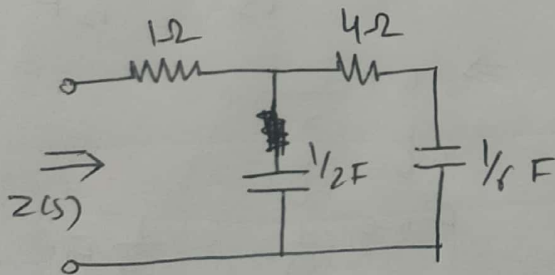

Case II -

(4)

$$Z(s) = \frac{3 + 4s + s^2}{2s + s^2}$$

$$2s + s^2 \overline{) 3 + 4s + s^2} \left(\frac{3}{2s} \rightarrow Z \Rightarrow \frac{1}{Cs} \Rightarrow C = \frac{2}{3} F \right)$$

$$\underline{3 + \frac{3}{2}s}$$

$$\frac{5}{2}s + s^2 \overline{) 2s + s^2} \left(\frac{4}{5} \rightarrow Y = \frac{1}{R} \Rightarrow R = \frac{5}{4} \Omega \right)$$

$$\underline{2s + \frac{4}{5}s^2}$$


$$\frac{1}{5}s^2 \overline{) \frac{5}{2}s + s^2} \left(\frac{2s}{2s} \rightarrow Z \Rightarrow \frac{1}{Cs} \Rightarrow C = \frac{2}{25} F \right)$$

$$\underline{\frac{5}{2}s}$$

$$s^2 \overline{) \frac{1}{5}s^2} \left(\frac{1}{5} \rightarrow Y = \frac{1}{R} \Rightarrow R = 5 \Omega \right)$$


$$\underline{\frac{1}{5}s^2}$$

$$\underline{0}$$

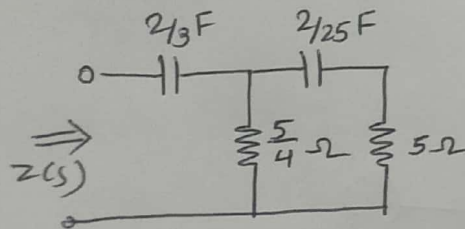

Q.3

(a) For N_1

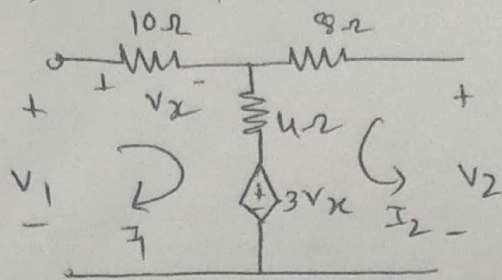

$$V_x = 10 I_1$$

KVL to loop 1

$$V_1 - 10 I_1 - 4 (I_1 + I_2) - 3 V_x = 0$$

$$V_1 = 44 I_1 + 4 I_2 \quad \text{--- (1)}$$

KVL to loop 2

$$V_2 - 8 I_2 - 4 (I_2 + I_1) - 3 V_x = 0$$

$$V_2 = 34 I_1 + 12 I_2 \quad \text{--- (2)}$$

$$12 I_2 = -34 I_1 + V_2$$

$$I_2 = -\frac{34}{12} I_1 + \frac{1}{12} V_2$$

$$I_2 = -2.83 I_1 + 0.0833 V_2 \quad \text{--- (i)}$$

$$\boxed{h_{21} = -2.83 \quad h_{22} = 0.0833}$$


$$V_1 = 44 I_1 + 4 [-2.83 I_1 + 0.0833 V_2]$$

$$V_1 = 32.68 I_1 + 0.33 V_2$$

$$\boxed{h_{11} = 32.68 \quad h_{12} = 0.33}$$

$$h_i = \begin{bmatrix} 32.68 & 0.33 \\ -2.83 & 0.0833 \end{bmatrix}$$

For N_2

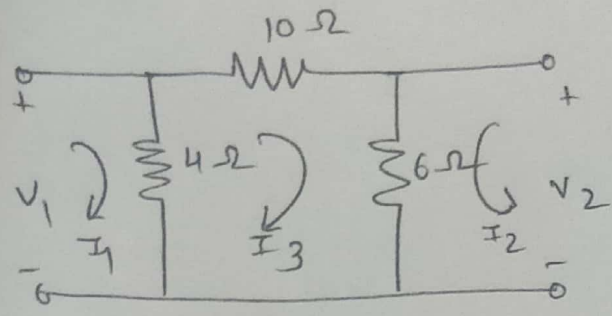

loop 1

$$V_1 - 4(I_1 - I_3) = 0$$

$$V_1 = 4I_1 - 4I_3 \quad \text{--- (i)}$$

loop 2

$$V_2 - 6(I_2 + I_3) = 0$$

$$V_2 = 6I_2 + 6I_3 \quad \text{--- (ii)}$$

loop 3

$$-10I_3 - 6(I_3 + I_2) - 4(I_3 - I_1) = 0$$

$$-10I_3 - 6I_3 - 6I_2 - 4I_3 + 4I_1 = 0$$

$$4I_1 - 6I_2 - 20I_3 = 0$$

$$20I_3 = 4I_1 - 6I_2$$

$$I_3 = \frac{I_1}{5} - \frac{3}{10} I_2$$

$$V_1 = 4I_1 - 4 \left[\frac{I_1}{5} - \frac{3}{10} I_2 \right]$$

$$V_1 = \frac{16}{5} I_1 + \frac{6}{5} I_2 \quad \text{--- (1)}$$

$$V_2 = 6I_2 + 6 \left[\frac{I_1}{5} - \frac{3}{10} I_2 \right]$$

$$V_2 = \frac{6}{5} I_1 + \frac{21}{5} I_2 \quad \text{--- (2)}$$

Rearrange eqn (2)

$$\frac{21}{5} I_2 = V_2 - \frac{6}{5} I_1$$

$$I_2 = -\frac{2}{7} I_1 + \frac{5}{21} V_2$$

$$h_{21} = -\frac{2}{7} \quad h_{22} = \frac{5}{21}$$

$$V_1 = \frac{16}{5} I_1 + \frac{6}{5} \left(-\frac{2}{7} I_1 + \frac{5}{21} V_2 \right)$$

$$V_1 = \frac{20}{7} I_1 + \frac{2}{7} V_2$$

$$h_{11} = \frac{20}{7} \quad h_{12} = \frac{2}{7}$$


N_1

$$\begin{bmatrix} 32.68 & 0.33 \\ -2.83 & 0.0833 \end{bmatrix} + \begin{bmatrix} \frac{20}{7} & \frac{2}{7} \\ -\frac{2}{7} & \frac{5}{21} \end{bmatrix} = \begin{bmatrix} 35.532 & 0.616 \\ -3.116 & 0.3212 \end{bmatrix}$$

(b) At $t=0^-$, No current flowing thro the inductor


$$i(0^-) = 0$$

At $t=0^+$

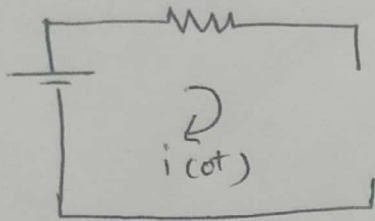

$$i(0^+) = 0$$

For $t > 0$, the network is shown.

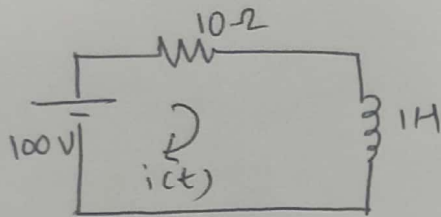

$$100 - 10i(t) - 1 \frac{di}{dt} = 0 \quad \text{--- (1)}$$

$$\frac{di}{dt} = 100 - 10i(t) \quad \text{--- (2)}$$

At $t=0^+$

$$\boxed{\frac{di}{dt}(0^+) = 100 \text{ A/s}}$$


Differentiating equation 2

$$\frac{d^2i}{dt^2} = -10 \frac{di}{dt}$$

$$\boxed{\frac{d^2i}{dt^2} = -10(100) = -1000 \text{ A/s}^2}$$

Q1-4

(a)

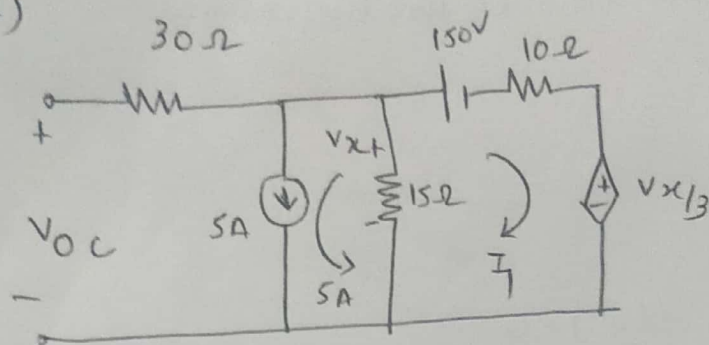Step :- I


$$V_x = -15(5 + I_1)$$

$$-150 + 10I_1 - \frac{V_x}{3} - 15(I_1 + 5) = 0$$

$$I_1 = -10 \text{ Amp}$$

$$V_{OC} = V_x = -15(5 - 10)$$

$$\boxed{V_{OC} = 75 \text{ V}}$$

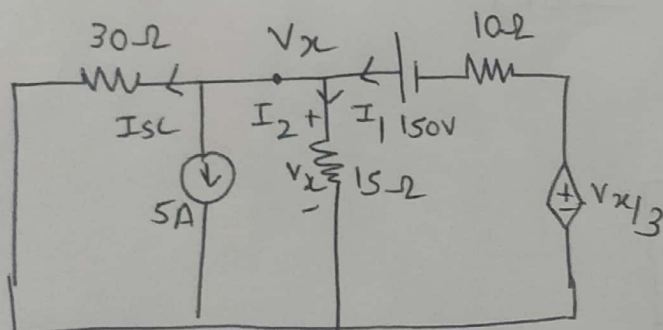Step :- II Find I_{SC} Applying KCL at node V_x

$$I_1 = I_2 + 5 + I_{SC}$$

$$\frac{V_x}{3} + 150 - V_x = \frac{V_x}{15} + 5 + \frac{V_x}{30}$$


$$\boxed{V_x = 60 \text{ V}}$$

$$I_{SC} = \frac{V_x}{30} = 2 \text{ Amp}$$

Step III:-


$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{75}{2} = 37.5 \Omega$$

Step IV:-

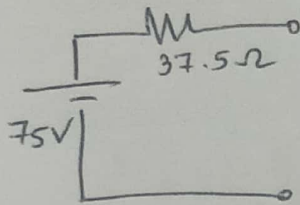

(b) solution:-

In s-domain

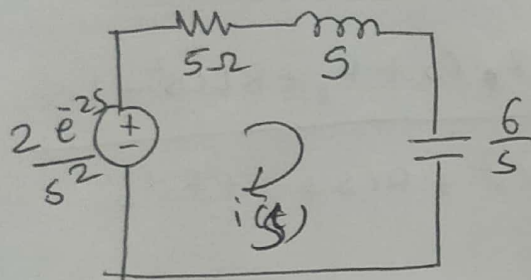

$$\frac{2e^{-2s}}{s^2} - 5I(s) - sI(s) - \frac{6}{s}I(s) = 0$$

$$\frac{2e^{-2s}}{s^2} = I(s) \left[5 + s + \frac{6}{s} \right]$$

$$I(s) = \frac{2e^{-2s}}{s(s^2 + 5s + 6)} = \frac{2e^{-2s}}{s(s+3)(s+2)}$$

By P.F

$$\frac{1}{s(s+3)(s+2)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+2}$$

$$I(s) = 2e^{-2s} \left[\frac{1}{6s} + \frac{1}{3(s+3)} - \frac{1}{2(s+2)} \right]$$

$$I(s) = \frac{1}{3} \frac{e^{-2s}}{s} - \frac{e^{-2s}}{s+2} + \frac{2}{3} \frac{e^{-2s}}{s+3}$$

$$i(t) = \frac{1}{3} u(t-2) - e^{-2(t-2)} u(t-2) + \frac{2}{3} e^{-3(t-2)} u(t-2)$$

Q15
(a)

$$Z(s) = \frac{(R_1 + Ls) \cdot (R + 1/s)}{R_1 + Ls + R + \frac{1}{Cs}} = \frac{R_1 R + \frac{R_1}{Cs} + R L s + \frac{L}{C}}{R_1 Cs + L C s^2 + R C s + 1}$$

$$= \frac{R_1 R C s + R_1 + R L C s^2 + L}{L C s^2 + R C s + 1 + R_1 C s}$$

$$= \frac{R L C s^2 + s [R_1 R C + L] + R_1}{L C s^2 + s [R C + R_1 C] + 1}$$

$$Z(s) = H \cdot \frac{(s+1)(s+3)}{(s+1+\sqrt{5}j)(s+1-\sqrt{5}j)}$$

$$= \frac{H (s+1)(s+3)}{(s+1)^2 - (j\sqrt{5})^2}$$

$$= \frac{H [s^2 + 4s + 3]}{s^2 + 2s + 6} = \frac{H [s^2 + 4s + 3]}{s^2 + 2s + 6}$$

$$Z(0) = H \left[\frac{3}{6} \right] \quad \therefore H = 2$$

$$1 = \frac{H}{2}$$

$$Z(s) = 2 \frac{[s^2 + 4s + 3]}{s^2 + 2s + 6}$$

$$= \frac{RLC \left[s^2 + s \left[\frac{R_1 RC + L}{RLC} \right] + \frac{R_1}{RLC} \right]}{LC \left[s^2 + s \left[\frac{RC + R_1 C}{LC} \right] + \frac{1}{LC} \right]}$$

$$= \frac{R \left[s^2 + s \left[\frac{R_1}{L} + \frac{1}{RC} \right] + \frac{R_1}{RLC} \right]}{s^2 + s \left[\frac{R}{L} + \frac{R_1}{L} \right] + \frac{1}{LC}}$$

$$\boxed{R = 2 \Omega}$$

$$\frac{R_1}{L} + \frac{1}{2C} = 4$$

$$\frac{R_1}{L} + \frac{1}{RC} = 4$$

$$\frac{R_1}{2LC} = 3$$

$$\boxed{L = \frac{3}{2} H}$$

$$\frac{R_1}{RLC} = 3$$

$$\boxed{\frac{R_1}{LC} = 6}$$

$$\frac{1}{\frac{3}{2}} + \frac{1}{2C} = 4$$

$$\frac{R + R_1}{L} = 2$$

$$\frac{2 + R_1}{L} = 2$$

$$\frac{2}{3} + \frac{1}{2C} = 4$$

$$\frac{1}{LC} = 6$$

$$2 + R_1 = 2L$$

$$\frac{1}{2C} = 4 - \frac{2}{3}$$

$$R_1 \cdot 6 = 6$$

$$\frac{1}{2C} = \frac{10}{3}$$

$$\frac{1}{2} = \frac{10}{3} C$$

$$\boxed{\begin{array}{l} R = 2 \Omega \\ R_1 = 1 \Omega \\ L = \frac{3}{2} H \\ C = \frac{3}{20} F \end{array}}$$

$$\boxed{R_1 = 1 \Omega}$$

$$\boxed{\frac{3}{20} = C}$$

$$\frac{1}{L} + \frac{1}{2C} = 4$$


$$\boxed{C = \frac{3}{20} F}$$

$$\frac{2 + 1}{L} = 2$$

$$\frac{3}{L} = 2$$

(b)

Step I:- considering only 20V

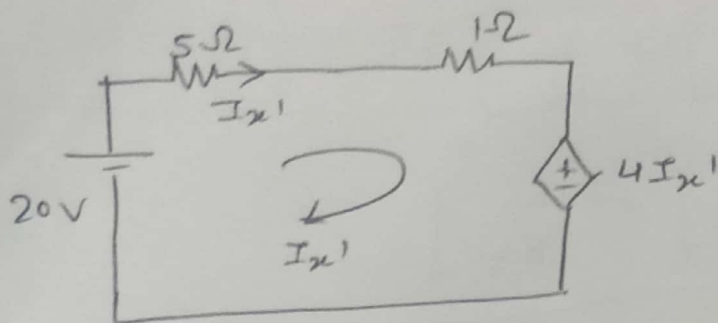


$$20 - 5I_x' - I_x' - 4I_x' = 0$$

$$20 = 10I_x'$$

$$I_x' = 2A$$

Step II:- considering only 30A

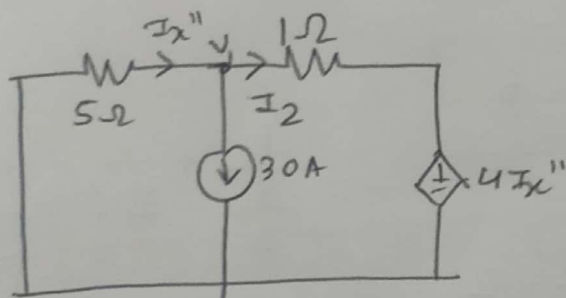

$$I_x'' = 30 + I_2$$

$$I_x'' - \frac{V_1}{5} = 30 + \frac{V_1 - 4I_x''}{1}$$

$$I_x'' = 30 + V_1 - 4I_x''$$

$$5I_x'' = 30 + V_1$$

$$5 \left[-\frac{V_1}{5} \right] = 30 + V_1$$

$$-30 = 2V_1$$

$$V_1 = -15V$$

$$I_x'' = -\frac{V_1}{5} = 3A$$

$$I_x = I_2' + I_x''$$

$$= 2 + 3$$

$$I_x = 5A$$

Q1-6

$$(a) \quad F(s) = \frac{2s^4 + 7s^3 + 11s^2 + 12s + 4}{s^4 + 5s^3 + 9s^2 + 11s + 6}$$

Step I:-

$$Z(s) = 2s^4 + 7s^3 + 11s^2 + 12s + 4$$

$$\begin{array}{r|rrrr} s^4 & 2 & 11 & 4 & \\ s^3 & 7 & 12 & 0 & \\ s^2 & \underline{53} & 4 & 0 & \\ s & \underline{440} & 0 & & \\ s^0 & 4 & & & \end{array}$$

$$Z(s) = s^4 + 5s^3 + 9s^2 + 11s + 6$$

$$\begin{array}{r|rrrr} s^4 & 1 & 9 & 6 & \\ s^3 & 5 & 11 & 0 & \\ s^2 & \underline{34/5} & 6 & 0 & \\ s & \underline{112/17} & 0 & & \\ s^0 & 6 & & & \end{array}$$

1st condition is satisfied.

step II:-

$$N(s) = 2s^4 + 7s^3 + 11s^2 + 12s + 4$$

$$(s+2)(s+0.5)(s+0.5+j1.323)(s+0.5-j1.323)$$

$$D(s) = s^4 + 5s^3 + 9s^2 + 11s + 6$$

$$(s-3)(s+1)(s+0.5-j1.323)(s+0.5+j1.323)$$

No poles on jw axis
residue test not require

2nd condition satisfied.

Step 3:-

$$A(\omega^2) = m_1 m_2 - n_1 n_2 \Big|_{s=j\omega}$$

$$m_1 = 2s^4 + 11s^2 + 4 \quad n_1 = 7s^3 + 12s$$

$$m_2 = s^4 + 9s^2 + 6 \quad n_2 = 5s^3 + 11s$$

$$A(\omega^2) = (2s^4 + 11s^2 + 4)(s^4 + 9s^2 + 6) - (7s^3 + 12s)(5s^3 + 11s)$$

$$= 2s^8 + 18s^6 + 12s^4 + 11s^6 + 99s^4 + 66s^2 + 4s^4 + 36s^2 + 24$$

$$- [35s^6 + 77s^4 + 60s^4 + 23s^2]$$

$$= \text{for all values of } \omega \geq 0$$


$$A(\omega^2) \geq 0$$

\therefore Third condition satisfied

\therefore given function is PPF

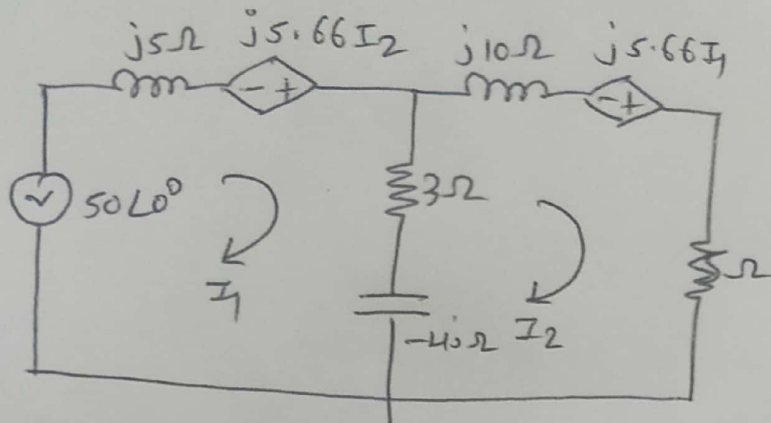(b) For magnetically coupled circuit

$$\begin{aligned}
 X_m &= K \sqrt{X_{L1} X_{L2}} \\
 &= 0.8 \sqrt{(5)(10)} \\
 &= 5.66 \Omega
 \end{aligned}$$



KVL to mesh 1

$$50 \angle 0^\circ - j5I_1 + j5.66I_2 + (3 - 4j)(I_1 - I_2) = 0$$

$$(3 + j)I_1 - (3 + j1.66)I_2 = 50 \angle 0^\circ \quad \text{--- (1)}$$

KVL to mesh 2

$$-(3 - 4j)(I_1 - I_2) - j10I_2 + j5.66I_1 - 5I_2 = 0$$

$$-(3 + j1.66)I_1 + (8 + 6j)I_2 = 0$$

$$\begin{bmatrix} 3+j & -(3+j1.66) \\ -(3+j1.66) & 8+6j \end{bmatrix}
 \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} =
 \begin{bmatrix} 50 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$I_2 = \frac{\begin{vmatrix} 3+j & 50 \angle 0^\circ \\ -(3+j1.66) & 0 \end{vmatrix}}{\begin{vmatrix} 3+j & -(3+j1.66) \\ -(3+j1.66) & 8+6j \end{vmatrix}} = 8.62 \angle -24.7^\circ$$

$$V_{5\Omega} = 5I_2 = 43.1 \angle -24.79^\circ \text{ A}$$