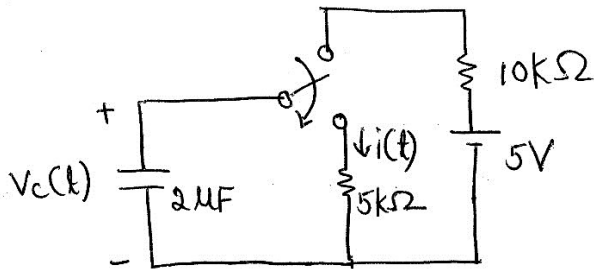


Please check whether you have got the right question paper.


- N.B:
1. Question.No.1 is compulsory.
 2. Attempt any three from remaining.
 3. Assume suitable data if necessary.

- Q.1 a) Determine $V_c(0^+)$, $V_c(0^-)$, $i(0^+)$, $i(0^-)$, Obtain time constant for $t > 0$ and current $i(t)$ for $t > 0$. 10




05

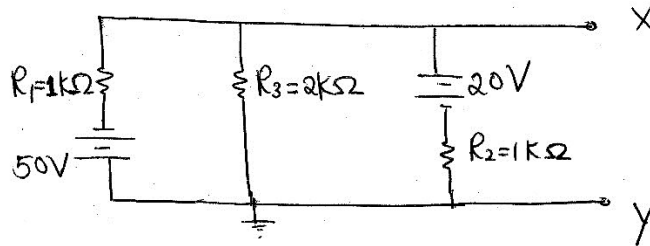- i. In the figure blow apply Millman's theorem to solve for the voltage V_{xy} .




05

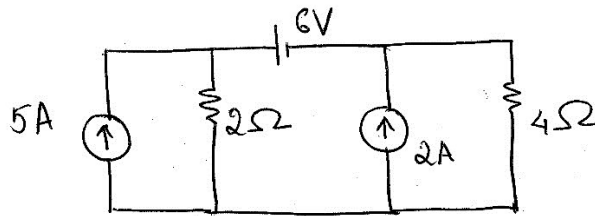- ii. Find current I using source transformation through. 4Ω Resistor.



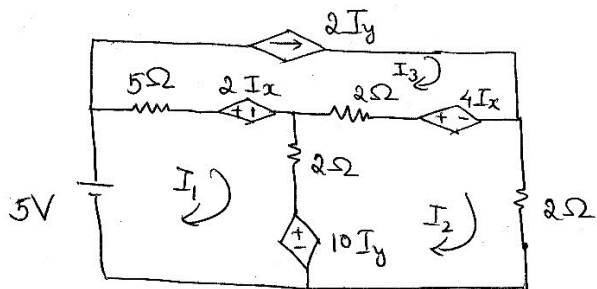
- Q.2 a) Using mesh analysis find the currents I_x and I_y . 10




- i. Draw the oriented graph from the incidence matrix given below. 05

$$\begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 0 \end{bmatrix}$$

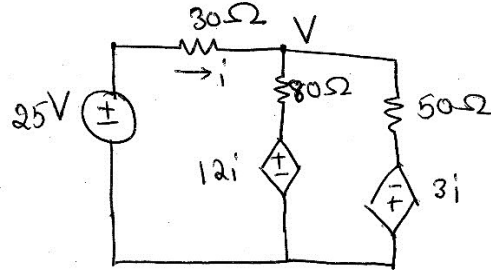- ii. Using source transformation find the voltage V. 05



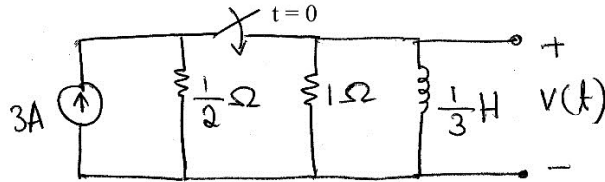- Q.3 a) In the network shown, the switch is closed at $t = 0$. Find $v(t)$ for $t > 0$. 10



- b) Explain the difference between dependent and independent sources, also write down the various types of dependent sources with relevant examples. 10

- Q.4 a) Test the three polynomials $K_1(s)$, $K_2(s)$ and $K_3(s)$ for Hurwitz criteria 10

- i) $K_1(s) = 2s^4 + s^3 + 7s^2 + s + 1$
 ii) $K_2(s) = s^4 + 2s^3 + 2s^2 + 2s + 1$
 iii) $K_3(s) = s^3 + s^2 + s + 2$


- b) Realise the network for the following functions using specified method. 10

i. $Z(s) = \frac{s^4 + 4s^2 + 3}{s(s^2 + 2)}$ (Foster I)

ii. $Y(s) = \frac{6s^4 + 42s^2 + 48}{s^5 + 18s^3 + 48s}$ (Cauer I)


- Q.5 a) Derive the condition of reciprocity and symmetry for transmission parameters/ chain parameters. 10

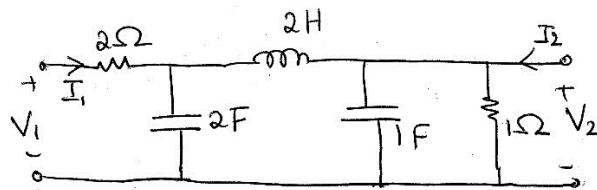- b) Determine ABCD parameter of the given network. 10



- Q.6 a) Find the voltage across 5Ω resistor using mesh analysis

10

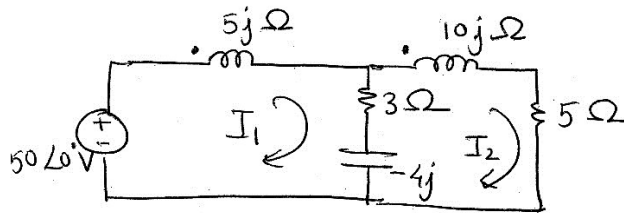

- b) Find 'i' current in the given circuit using superposition theorem.

10

