

Q.P. Code :25130

[Time: Three Hours]


[Marks:80]

Please check whether you have got the right question paper.

- N.B:
1. Question.No.1 is compulsory.
 2. Attempt any three questions from the remaining.
 3. Assume suitable data if required. Justify your assumptions.

- Q.1
- a) Differentiate between JFET and MOSFET. 05
 - b) Derive torque Equation of DC Motor. 05
 - c) State applications of BLDC motor. 05
 - d) Forced and natural response of RLC network 05

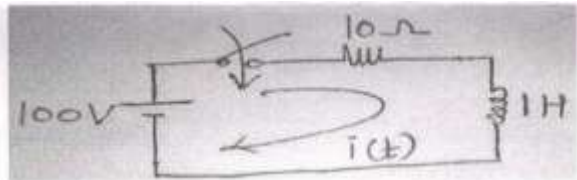- Q.2
- a) In the network, switch is closed. Assuming all initial conditions as zero. Find $i(t)$, $di(t)/dt$, $d^2i(t)/dt^2$ at $t=0+$ 10




- b) Explain working of BJT CE amplifier with neat circuit diagram and necessary equations. 10

- Q.3
- a) Using the pole-zero plot, find magnitude and phase of the function. 10
 $F(s) = \frac{(s+1)(s+3)}{s(s+2)}$ at $s = j4$.

- b) Explain characteristics for DC shunt and Series motor. 10

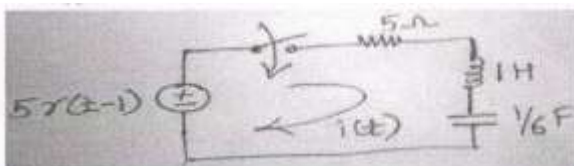- Q.4
- a) Determine the current $i(t)$ in the network, when the switch is closed at $t=0$ 10



- b) Explain different methods of speed control for three phases Induction Motor. 10

Q.P. Code :25130

- Q.5 a) A 250 V, 4 Pole, DC shunt motor has armature resistance of 0.12Ω and field resistance of 125Ω . It has 960 lap connected conductors and flux of 20mWb per pole. If the input current is 30A , estimate speed and torque developed. 10
- b) Explain construction and working of squirrel cage induction motor. 10
- Q.6 Write short notes on **any three**. 20
- a) Equivalent circuit for induction motor
 - b) Capacitor start capacitor run IM
 - c) 3-point starter
 - d) Working of BJT as a Switch.
