

(3 HOURS)

Total Marks : 80

1. Question no. 1 is compulsory.
2. Solve any three from remaining five questions.
3. Assume suitable additional data if necessary

- Q1 (a) Write short note on virtual ground (5 marks)
- (b) Define the following (5 marks)
- a) Input offset voltage b) CMRR c) PSRR d) Slew Rate
- (c) Explain a non inverting comparator with diagram. (5 marks)
- (d) If the time constant of an integrator is 1ms and the input is a square wave of frequency 1kHz, $V_{pp} = 2V$. Draw the output waveforms. Assume $V_0 = 0V$ at $t = 0$. (5 marks)
- Q2 (a) Design a second order KRC low pass filter with a cut off frequency $f_o = 1kHz$ and pass band gain of 1.586. (10 marks)
- (b) Design an RC phase shift oscillator to oscillate at 100Hz. (10 marks)
- Q3 (a) Discuss (any one) (10 marks)
- a) square wave generator b) triangular wave generator
- (b) Draw the circuit diagram for a peak detector and explain the working. (10 marks)
- Q4 (a) Design an astable multivibrator using IC555 for a frequency of 2kHz and a duty cycle of 70%. what modification you suggest to obtain 50% duty cycle. (10 marks)
- (b) Discuss in detail R-2R ladder D/A converter. (10 marks)
- Q5 (a) Explain function of each block of PLL. (10 marks)
- (b) Discuss classification of IC voltage regulators. Explain the functional block diagram of a three terminal fixed voltage regulator. (10 marks)

Q6 (a) Write short note on (any two)

(20 marks)

a) Instrumentation amplifier

b) Logarithmic amplifiers.

c) Precision rectifiers

d) Schmitt trigger