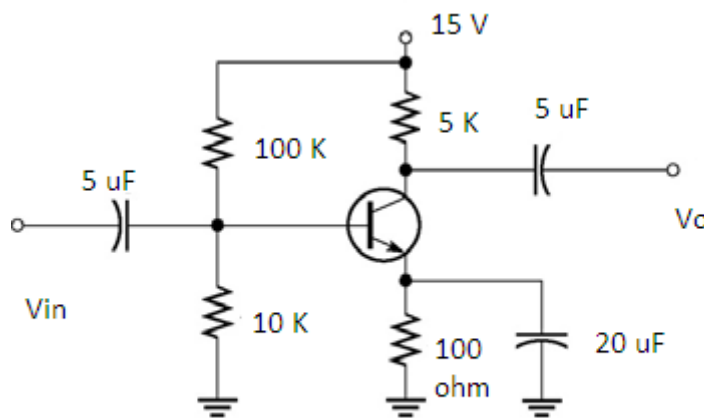


Time: 3 Hours

Max. Marks: 80

- N.B. (1) Question No. 1 is compulsory.  
 (2) Answer any three from remaining five questions.  
 (3) Figures to the right indicate full marks  
 (4) Assume the data if it is necessary.

Que-1	Solve <b>any four</b>	Marks
a	Explain the working of Photodiode.	5
b	How BJT amplifies weak signal, explain.	5
c	Compare depletion and enhancement type nMOSFET	5
d	Explain the different types of coupling.	5
e	Compare Differential amplifier with normal CE amplifier.	5
f	State the condition of sustained oscillations in oscillator circuit.	5
Que-2a	What is the need of Filters in power supply, explain LC filter with neat diagram, waveform and ripple factor equation.	10
Que-2b	Determine $A_v$ , $A_i$ , $R_i$ and $R_o$ for given BJT amplifier circuit using hybrid model	10




Given :  $h_{ie} = 1 \text{ k ohm}$ ,  $h_{fe} = 50$ , Neglect  $h_{re}$  and  $h_{oe}$

Que-3a	Draw Voltage divider bias circuit for JFET and derive equation of $I_{DQ}$ and $V_{DSQ}$	10
Que-3b	State the advantages of Negative feedback in amplifier, Prove that Input resistance increases in voltage series negative feedback amplifier.	10
Que-4a	Derive equation of $A_{dm}$ , $A_{cm}$ and CMRR for Dual input Balanced output Differential amplifier	10
Que-4b	Explain working of Wien Bridge oscillator with the help of diagram.	10

Que-5a For the given circuit find  $I_{Bq}$ ,  $I_{Cq}$ ,  $V_{CEq}$ ,  $V_C$  and  $V_E$ , given  $\beta = 75$

10

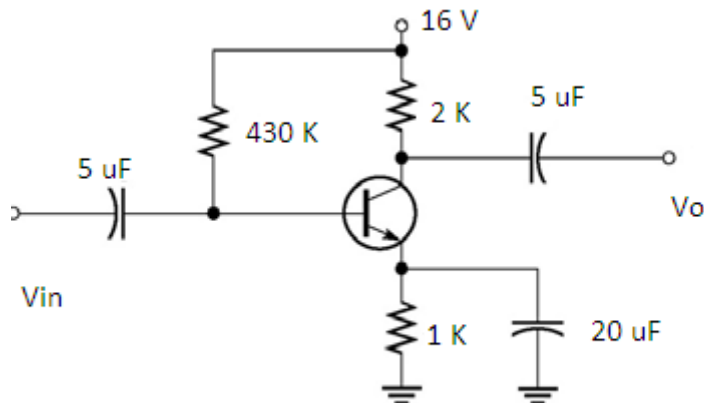

Que-5b Explain in brief different amplifier coupling techniques.

10

Que-6 Write short notes

- |   |   |   |
|---|---|---|
| a | Frequency response of BJT amplifier       | 5 |
| b | Small signal model of CS (JFET) Amplifier | 5 |
| c | Thermal Runaway                           | 5 |
| d | UJT Relaxation oscillator                 | 5 |
-