


Solution of Linear Integrated Circuits
 S.E. - Sem-IV - (CBCGS) - Biomedical Engineering.
 Subject Code - 40103 57409

Page No. 01 of 05

Q. No.

Q-2(a)

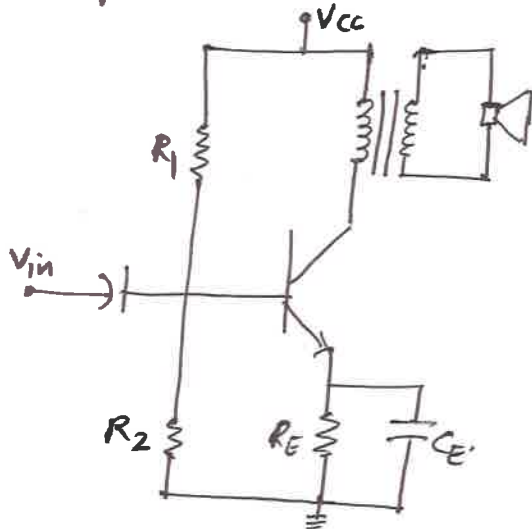Class A transformer coupled power amplifier to $8\text{-}\Omega$ load -



$$P_L = 10\text{W}, R_L = 8\text{-}\Omega$$

$$\text{Assume } \eta_T = 0.9$$

$$\therefore P_L' = \frac{P_L}{\eta_T}$$

$$P_d(\text{max}) \geq 2 P_L'$$

$$\text{Select } V_{CC} \left(V_{CC} \leq \frac{V_{CE0}}{2} \right)$$

$$V_{RE} = 10\% V_{CC}$$

$$R_L' = \frac{V_{CC} - V_{RE} - V_{CE(\text{sat})}}{2 P_L'}$$

$$S \leq 10 = \frac{(1 + \beta_{\text{max}})(1 + k)}{1 + \beta_{\text{max}} + k}$$

$$k = \frac{R_{Th}}{R_E}$$

$$\frac{N_1}{N_2} = \sqrt{\frac{R_L'}{R_L}}$$

Marks

Questions should be —
 WRITTEN IN LEGIBLE HANDWRITING IN BLACK INK.
 SIGNS, SKETCHES OR FIGURES IF ANY BE DRAWN IN NEAT BLACK INK,
 so as to avoid mistakes in the printed question papers.

Duration Hours.


Total Marks assigned to the paper

Q. No.

Marks

N.B.: Any other valid design approach can also be considered while assessment.

Q-3 - (a)

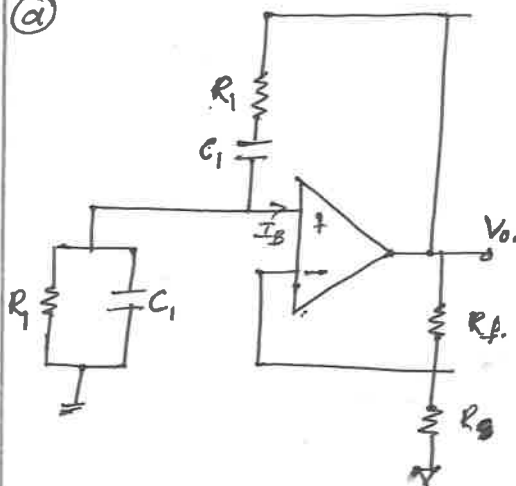

$f = 10\text{KHz}$ - Wein Bridge Osc^r.

$$R_f = 2R_1$$

$$f = \frac{1}{2\pi RC}$$

$$I_i = I_f + I_B \quad \& \quad I_B(\text{max}) = 100 \times 500 \text{ nA} = 50 \mu\text{A}$$

$$\text{Let } V_{cc} = 15\text{V} \Rightarrow V_o = V_{cc} - 1 = 14\text{V}$$

$$A_v = \frac{V_o}{V_{in}} \Rightarrow \text{gain} = \frac{R_f}{R_1} = 2$$

$$\therefore V_{in} = \frac{V_o}{A_v} = \frac{14}{2} = 7$$

$$R_1 = \frac{V_{in}}{I_i} = \frac{7\text{V}}{50 \mu\text{A}} = 0.14 \text{ M}\Omega = 140\text{K}\Omega$$

$$R_f = 2R_1 = 2 \times 140\text{K} = 280\text{K}$$


$$R = \frac{R_1}{10} = \frac{140}{10} = 14\text{K} \approx 15\text{K (Std)}$$

$$C = \frac{1}{2\pi f R} = 0.001 \mu\text{F}$$

Q. No.

Marks

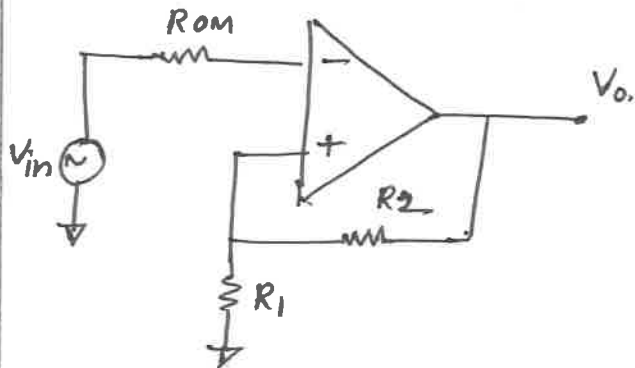Q-3-(b) $V_{ut} = 4V$, $V_{lt} = -4V$ $V_{CC} = V_{EE} = \pm 15V$.



$$V_{ut} = \frac{R_1}{R_1 + R_2} (+V_{sat})$$

$$V_{lt} = \frac{R_1}{R_1 + R_2} (-V_{sat})$$

$$V_{hy} = V_{ut} - V_{lt}$$

As $|V_{cd}| = |V_{EE}| = 15V$, $V_{sat} \& -V_{sat} = \pm 14V$

$$V_{ut} = \frac{R_1}{R_1 + R_2} \times 14V$$

Let $R_1 + R_2 = 10K$


$$\therefore R_1 = V_{ut} \times \frac{R_1 + R_2}{14}$$

$$= 4 \times \frac{10}{14}$$

$$= 2.85K$$

$$\therefore R_2 = 7.15K$$

(c) $V_o = 3V_a - 5V_b - 6V_c$

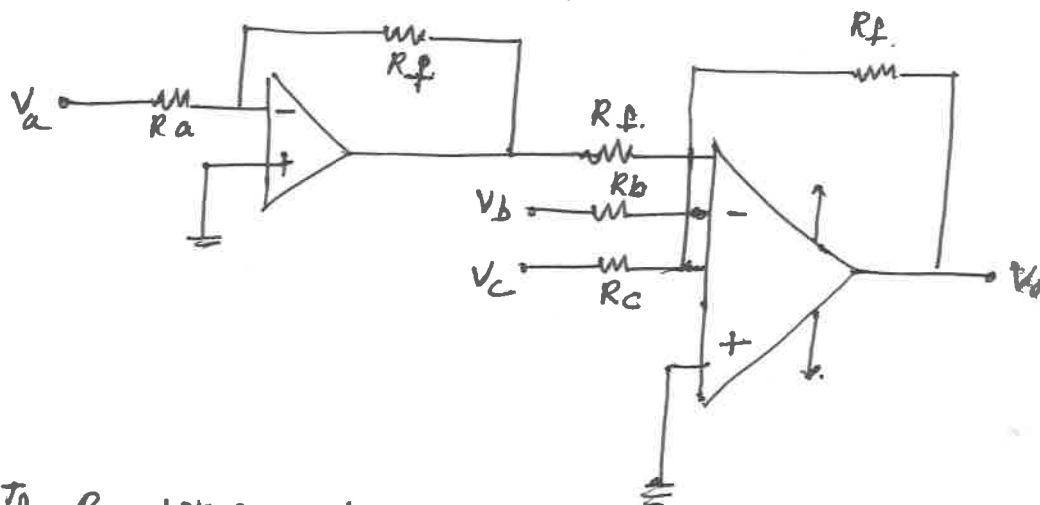

If $R_f = 10K\Omega$, $R_a = 3.33K$, $R_b = 2K$, $R_c = 1.67K$.


Q. No.

Marks

$$V_{0a} = -V_a \cdot \frac{R_f}{R_a}$$

$$V_o = - \left(V_a \frac{R_f}{R_a} \right) - V_b \cdot \frac{R_f}{R_b} - V_c \cdot \frac{R_f}{R_c}$$

(d)

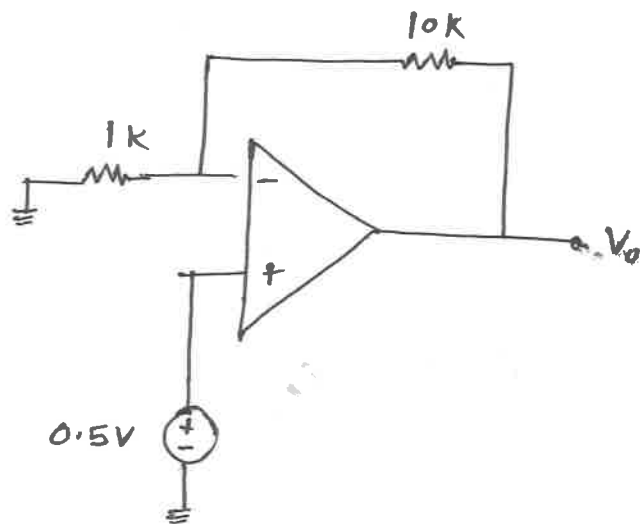

$$I_L = \frac{V_o - V_i}{R_L}$$

$V_i = 0.5V$ by
Virtual short.

$$\begin{aligned} V_o &= \left(1 + \frac{R_f}{R_i} \right) \cdot V_i \\ &= \left(1 + \frac{10}{1} \right) V_i \\ &= 5.5V \end{aligned}$$

$$\therefore I_L = \frac{5.5 - 0.5}{10} = 0.5 \text{ mA}$$

$$\text{If } R_L = 20k \quad I_L = \frac{10.5 - 0.5}{20} = 0.5 \text{ mA}$$

Q. No.

Q-5 (a)

D.C analysis -

$$I_E = \frac{V_{EE} - V_{BE}}{\frac{R_{in}}{\beta} + 2R_E} \quad \text{or} \quad \frac{V_{EE}}{2R_E}$$

$$V_{CE} = (V_{CC} - I_C R_C) - (-V_{BE}) = V_{CC} + V_{BE} - I_C R_C$$

$$= -11.79$$

a.c analysis -

$$r_e = \frac{26 \text{ mV}}{I_{CQ}} = 2.7 \Omega$$

$$A_d = \frac{R_C}{r_e} = 1.2 \text{ k}$$

$$A_c = \frac{-R_C}{r_e + 2R_E} = \frac{3.3}{2.7 \Omega + 2 \times 1 \text{ k}}$$

$$= 1.65$$

$$R_{id} = 2\beta a_c r_e$$

$$= 2 \times 100 \times 2.7 \Omega$$

$$= 540 \Omega$$


$$CMRR = \frac{r_e + 2R_E}{r_e} \quad \text{or} \quad \frac{A_d}{A_c}$$

$$\approx 740$$

$$R_o = R_C = 3.3 \text{ k}$$

Marks

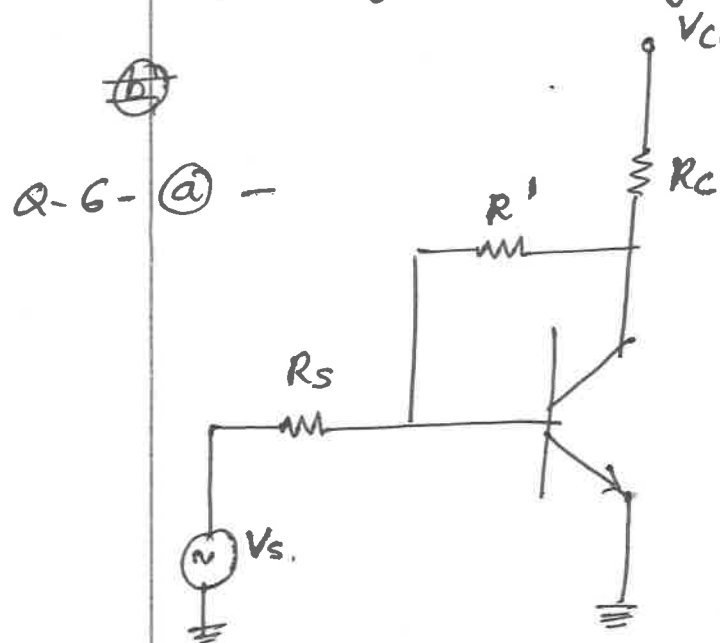Q. No. ~~Q-3~~ (a) Design a wein bridge oscillator for ~~10 kHz~~ frequency.



Type of feedback -
Shunt Shunt f/b.

$$i) \beta = \frac{-I_f}{V_o}$$

$$ii) R_M = \frac{V_o}{I_s}$$

$$iii) D = 1 + \beta \cdot R_M$$

$$iv) A_{vf} = \frac{R_{MF}}{R_S}$$

$$v) R_{if} = \frac{R_i}{D}$$

$$vi) R_{of} = \frac{R_o \parallel R_c}{D}$$

Marks