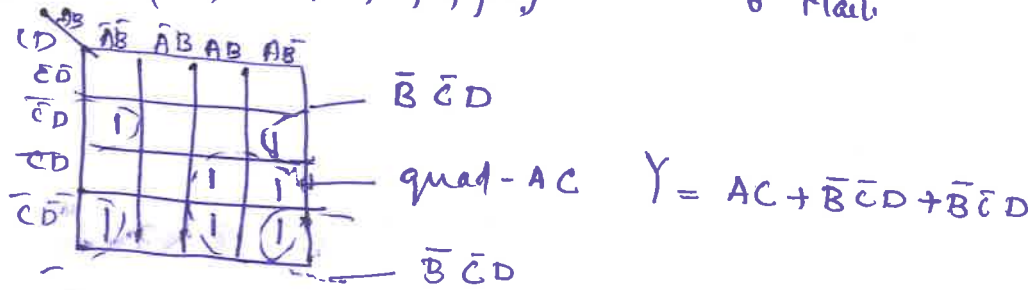


3 (b) $Y = \sum m(1, 2, 9, 10, 11, 14, 15)$

6 Marks




Implementation using gates - 4 Marks.

4 (b)

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 10, 11, 14, 15)$$



	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	\bar{A}	\bar{A}	1	1	\bar{A}	0	A	A

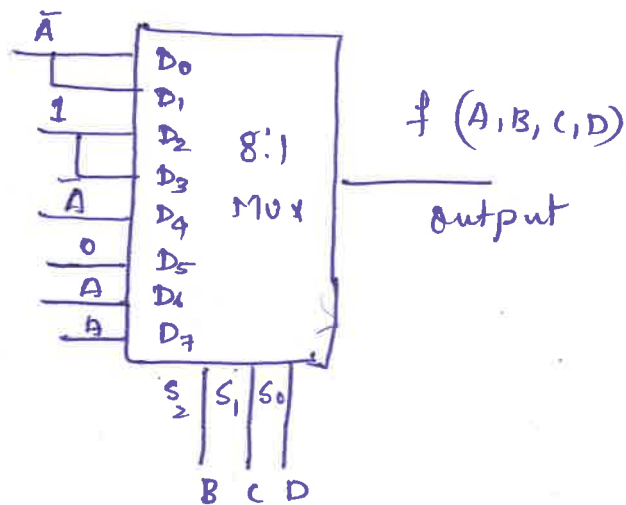

5 (a)

Binary input			Gray output		
B ₂	B ₁	B ₀	G ₂	G ₁	G ₀
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

4 Marks

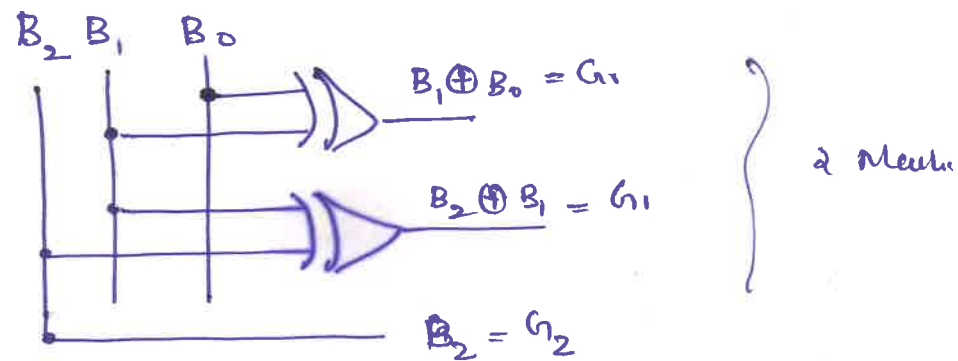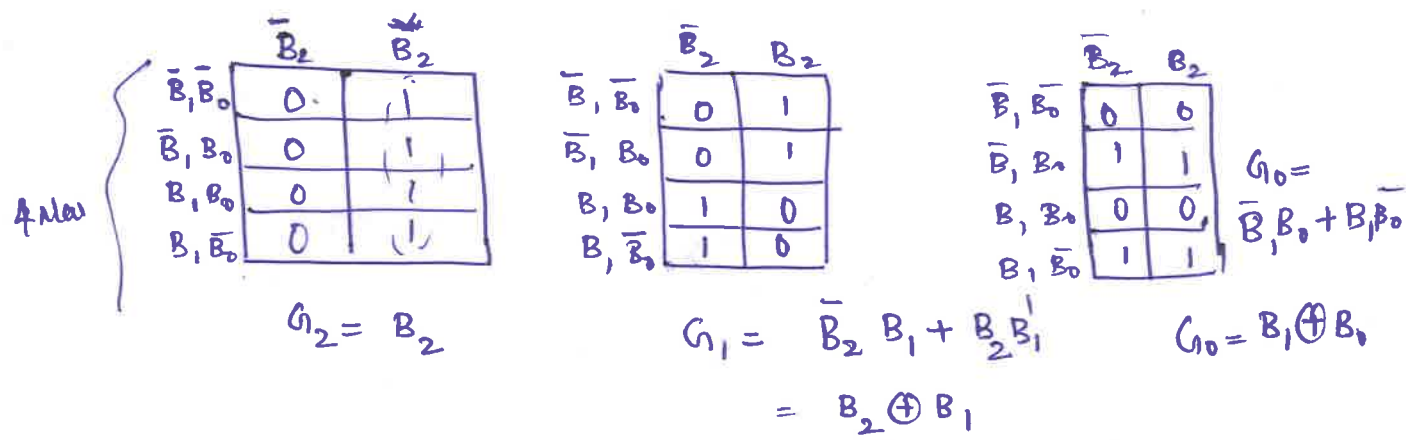

5 (b)

Q_C	Q_B	Q_A
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Q_C	Q_B	Q_A	Q_C^+	Q_B^+	Q_A^+	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	0	0	0	1	x	x	1	x	1
1	0	0	0	0	0	x	1	0	x	0	x
1	0	1	0	0	0	x	1	0	x	x	1
1	1	0	0	0	0	x	1	x	1	0	x
1	1	1	0	0	0	x	1	x	1	x	1

$$J_C = Q_B, Q_A, K_C = 1, J_B = \bar{Q}_C Q_A, K_B = Q_C + Q_A, J_A = \bar{Q}_C, K_A = 1$$

Implementasi using JK - 3 Meulu



Timing diagram - 1 Meul