

Model Question paper for online examination
F.Y.B.Sc. CS PHYSICS PAPER-II

Q1. The time constant of a circuit consisting of a 15 mH inductor and a 470 K Ω resistor is

- (a) **32 Ns
- (b) 7 Ns
- (c) 31.9 Ns
- (d) 70 Ns

Q2. The capacitance C is charged through a resistor R. The time constant of the charging circuit is given by

- (a) C/R
- (b) 1/RC
- (c) **RC
- (d) R/C

Q.3 In AC circuit, peak value of sine wave is 220 V. Its average value will be

- (a) 120.1 V
- (b) **140.1 V
- (c) 180.5 V
- (d) 200 V

Q4. The net impedance in series LCR circuit connected with AC source at resonance will be ,

- (a) **Z = R
- (b) Z = ωC
- (c) Z = ωL
- (d) Z = $\omega L - 1/\omega C$

Q5. The kinetic energy of electron in an orbit of radius r in hydrogen atom is proportional to

- (a) $\frac{e^2}{r}$
- (b) ** $\frac{e^2}{2r}$
- (c) $\frac{e^2}{r^2}$
- (d) $\frac{e^2}{2r^2}$

Q6. The ratio of minimum to maximum wavelength in Balmer series is

- (a) **5 : 9
- (b) 5 : 36
- (c) 1 : 4

(d) 3 : 4

Q7. The wavelength of de-Broglie wave is $3 \mu\text{m}$, then its momentum ($h = 6.63 \times 10^{-34} \text{ Js}$) is

- (a) $2.21 \times 10^{-28} \text{ Js}$
- (b) $3.31 \times 10^{-28} \text{ Js}$
- (c) $4.45 \times 10^{-28} \text{ Js}$
- (d) $1.65 \times 10^{-28} \text{ Js}$

Q8. The potential difference applied to an X-ray tube increased. As a result in the emitted radiation

- (a) the Intensity increases
- (b) the minimum wavelength increases
- (c) the intensity remains unchanged
- (d) the minimum wavelength decreases

Q9. Moseley's law for characteristics of X-rays is $\nu = b (Z - a)^2$. In this formula

- (a) both a and b are independent on the material.
- (b) a is independent but b depends on the material.
- (c) b is independent but a depends on the material.
- (d) both a and b depend on the material.

Q10. The minimum inter planer space required for Bragg's diffraction

- (a) $\lambda/4$
- (b) $\lambda/2$
- (c) λ
- (d) 2λ

Q11. Average value of full wave rectified voltage with peak voltage of 60 volt is equal to

- (a) 23 V
- (b) 32.14 V
- (c) 38.16 V
- (d) 12.45 V

Q12. A voltage regulator has no load output of 20 V and full load output of 19.3 V. The percentage load regulation is

- (a) 0.7%
- (b) 3.5%
- (c) 21.4%
- (d) 67.9%

Q13. The phase difference between the output and input voltages of a CE amplifier is

- (a) 0°

- (b) 90°
- (c) **180°**
- (d) 270°

Q14. A transistor has $\alpha_{d.c.} = 0.995$, then $\beta_{d.c.}$ will be

- (a) 19.9
- (b) **199**
- (c) 0.99
- (d) 99

Q15. In PNP transistor working as a common – base amplifier, the current gain is 0.95 and emitter current is 8.3 mA. The base current is

- (a) **0.41 mA**
- (b) 0.34 mA
- (c) 0.29 mA
- (d) 0.20 mA

Note: Option marked with asterisk () is correct option.**