

**Model Question paper for online examination**  
**F.Y.B.Sc. CS PHYSICS PAPER-II**

Q1. The time constant of a circuit consisting of a 15 mH inductor and a 470 K $\Omega$  resistor is

- (a) \*\*32 Ns
- (b) 7 Ns
- (c) 31.9 Ns
- (d) 70 Ns

Q2. The capacitance C is charged through a resistor R. The time constant of the charging circuit is given by

- (a) C/R
- (b) 1/RC
- (c) \*\*RC
- (d) R/C

Q.3 In AC circuit, peak value of sine wave is 220 V. Its average value will be

- (a) 120.1 V
- (b) \*\*140.1 V
- (c) 180.5 V
- (d) 200 V

Q4. The net impedance in series LCR circuit connected with AC source at resonance will be ,

- (a) \*\*Z = R
- (b) Z =  $\omega C$
- (c) Z =  $\omega L$
- (d) Z =  $\omega L - 1/\omega C$

Q5. The kinetic energy of electron in an orbit of radius r in hydrogen atom is proportional to

- (a)  $\frac{e^2}{r}$
- (b) \*\* $\frac{e^2}{2r}$
- (c)  $\frac{e^2}{r^2}$
- (d)  $\frac{e^2}{2r^2}$

Q6. The ratio of minimum to maximum wavelength in Balmer series is

- (a) \*\*5 : 9
- (b) 5 : 36
- (c) 1 : 4

(d) 3 : 4

Q7. The wavelength of de-Broglie wave is  $3\text{ }\mu\text{m}$ , then its momentum ( $h = 6.63 \times 10^{-34}\text{ Js}$ ) is

- (a)  $2.21 \times 10^{-28}\text{ Js}$
- (b)  $3.31 \times 10^{-28}\text{ Js}$
- (c)  $4.45 \times 10^{-28}\text{ Js}$
- (d)  $1.65 \times 10^{-28}\text{ Js}$

Q8. The potential difference applied to an X-ray tube increased. As a result in the emitted radiation

- (a) the Intensity increases
- (b) the minimum wavelength increases
- (c) the intensity remains unchanged
- (d) the minimum wavelength decreases

Q9. Moseley's law for characteristics of X-rays is  $\nu = b(Z-a)^2$ . In this formula

- (a) both  $a$  and  $b$  are independent on the material.
- (b)  $a$  is independent but  $b$  depends on the material.
- (c)  $b$  is independent but  $a$  depends on the material.
- (d) both  $a$  and  $b$  depend on the material.

Q10. The minimum inter planer space required for Bragg's diffraction

- (a)  $\lambda/4$
- (b)  $\lambda/2$
- (c)  $\lambda$
- (d)  $2\lambda$

Q11. Average value of full wave rectified voltage with peak voltage of 60 volt is equal to

- (a) 23 V
- (b) 32.14 V
- (c) 38.16 V
- (d) 12.45 V

Q12. A voltage regulator has no load output of 20 V and full load output of 19.3 V. The percentage load regulation is

- (a) 0.7%
- (b) 3.5 %
- (c) 21.4%
- (d) 67.9 %

Q13. The phase difference between the output and input voltages of a CE amplifier is

- (a)  $0^\circ$

- (b)  $90^\circ$
- (c)  **$180^\circ$**
- (d)  $270^\circ$

Q14. A transistor has  $\alpha_{d.c.} = 0.995$ , then  $\beta_{d.c.}$  will be

- (a) 19.9
- (b) **199**
- (c) 0.99
- (d) 99

Q15. In PNP transistor working as a common – base amplifier, the current gain is 0.95 and emitter current is 8.3 mA. The base current is

- (a) **0.41 mA**
- (b) 0.34 mA
- (c) 0.29 mA
- (d) 0.20 mA

**Note: Option marked with asterisk (\*\*) is correct option.**